

Roll No. ....

Printed Pages : 3

1220

**BCA / D-18**  
**LOGICAL ORG.**  
**Paper-BCA-114**

**Logical Organisation of Computer-I**

*Time allowed : 3 hours]*

*[Maximum marks : 80*

*Note : Attempt five questions. Select one from each unit.*

*Question No. 1 is compulsory.*

1. (a) Make T.T. for self complimenting code. 2
- (b) Prove that NOR is universal gate. 2
- (c) State Duality Principle. 2
- (d) What is parity bit ? Define odd and even parity. 2
- (e) Prove using Induction (T.T.)  $a \oplus (b \oplus c) = (a \oplus b) \oplus c$ . 4
- (f) Draw and label 3 variable K – map. 4

**Unit-I**

2. Perform conversions as :

(a) (i)  $(17.3)_{10} \rightarrow ( )_2$  2

$( )_{16} \rightarrow ( )_{10}$  2

(ii)  $(X)_5 = (234)_{10}$

(iii) A register stores High, low, low, High. Find number in Decimal, Octal, Binary and Hexadecimal. 4

(b) Write note on Cyclic and 8421 code. 4

(c) Make Half Adder for adding Two numbers. 4

1220

[Turn over

(2)

3. (a) Explain floating point representation. 10  
(b) Solve using 2's Complement : 6
- |           |            |           |
|-----------|------------|-----------|
| -9        | -32        | -6        |
| <u>-7</u> | <u>+10</u> | <u>-9</u> |

### Unit-II

4. (a) Define Boolean algebra, its postulates, how it differs from ordinary algebra. 8  
(b) Solve using Boolean Algebra. 8
- (i)  $(a + b)(ac + c) \overline{(b + ac)} = \overline{abc}$   
(ii)  $ab + bc + ca$
5. (a) Draw and label 4 variable K - Map. 4  
(b) Solve using K- Map.  
 $z = \pi 0, 2, 4, 6$   
 $z = \sum 0, 1, 9, 10, 11 + \sum_{\phi} 2, 3, 8, 12$  8  
(c) Solve using T.T.  
 $\overline{a + b + c} = \overline{a} \cdot \overline{b} \cdot \overline{c}$  4

### Unit-III

6. (a) Make T.T. and explain :  
NAND, XOR, NOT 6  
(b) Make T.T. for 3 variables and explain :  
OR, AND, NOR 6  
(c) Make circuit diagram :  
 $ab(\overline{c}d + c\overline{d}) + \overline{a}bc$  4

1220

( 3 )

7. What is combinational logic ? Explain analysis and design procedures. 16

**Unit-IV**

8. (a) Make 4 to 10 Line Decoder  
(b) Make code convertor from 8421 to cyclic. 16
9. (a) Design Comparator for 2 bits  
(b) Make full-adder 16

