

Roll No. ....

Total Pages : 03

**BT-3/D-20**

**43138**

ELECTRONIC DEVICES

EC-201

Time : Three Hours]

[Maximum Marks : 75

**Note :** All questions in Part A and Part B are compulsory.  
Attempt any *Four* questions from Part C, selecting *one*  
question from each Unit.

**Part A**

**15**

1. Explain the following in brief :
  - (i) Diffusion and drift current
  - (ii) Base width modulation
  - (iii) Drain and Transfer characteristics
  - (iv) Opamp Series regulator
  - (v) Stability Factor.

**Part B**

**15**

2. Enumerate the concept of Zener breakdown in PN junction with its VI characteristics. **5**
3. Draw and explain the practical transistor CB amplifier. Also explain the function of each component. **5**

(2)L-43138

4. What is MOSFET ? Explain the construction and characteristics of N channel MOSFET with suitable diagram. 5
5. What do you understand by Voltage Regulation ? With neat sketch explain the working of Zener diode shunt voltage regulator. 5

**Part C**

**40**

**Unit I**

6. Explain the current flow in a forward biased PN junction with relevant expression for minority carrier concentration and diagram to illustrate the carrier density close to depletion layer. 10
7. Explain hole electron pair generation and recombination with diagrams in details. 10

**Unit II**

8. Draw and explain the practical transistor CE amplifier. Also explain the function of each component. 10
9. Draw and explain 11 parameters and PI model of CE Transistor. 10

### Unit III

10. Explain the following terms in details :
- (a) Pinch off voltage
  - (b) Channel length modulation
  - (c) Velocity saturation
  - (d) AC drain resistance
  - (e) Amplification factor. 10
11. With help of neat sketches explain the operation and characteristics of junction FET. 10

### Unit IV

12. Outline the construction of Zener voltage regulator with neat circuit diagram. 10
13. Write short notes on the following : 10
- (i) Transistor shunt voltage Regulator
  - (ii) DC Regulated power supply.