



# DIGITAL ELECTRONICS AND LOGIC DESIGN

**B.Tech (IT)**

**Notes**

**Prepared By:**



## UNIT - 1

### NUMBER SYSTEMS & BOOLEAN ALGEBRA

- Introduction about digital system
- Philosophy of number systems
- Complement representation of negative numbers
- Binary arithmetic
- Binary codes
- Error detecting & error correcting codes
- Hamming codes

#### INTRODUCTION ABOUT DIGITAL SYSTEM

A Digital system is an interconnection of digital modules and it is a system that manipulates discrete elements of information that is represented internally in the binary form.

Now a day's digital systems are used in wide variety of industrial and consumer products such as automated industrial machinery, pocket calculators, microprocessors, digital computers, digital watches, TV games and signal processing and so on.



#### Characteristics of Digital systems

- Digital systems manipulate discrete elements of information.
- Discrete elements are nothing but the digits such as 10 decimal digits or 26 letters of alphabets and so on.
- Digital systems use physical quantities called signals to represent discrete elements.
- In digital systems, the signals have two discrete values and are therefore said to be binary.
- A signal in digital system represents one binary digit called a bit. The bit has a value either 0 or 1.
  
#### Analog systems vs Digital systems

Analog system process information that varies continuously i.e; they process time varying signals that can take on any values across a continuous range of voltage, current or any physical parameter.

Digital systems use digital circuits that can process digital signals which can take either 0 or 1 for binary system.



Abrupt amplitude variations

## Advantages of Digital system over Analog system

### 1. Ease of programmability

The digital systems can be used for different applications by simply changing the program without additional changes in hardware.

### 2. Reduction in cost of hardware

The cost of hardware gets reduced by use of digital components and this has been possible due to advances in IC technology. With ICs the number of components that can be placed in a given area of Silicon are increased which helps in cost reduction.

### 3. High speed

Digital processing of data ensures high speed of operation which is possible due to advances in Digital Signal Processing.

### 4. High Reliability

Digital systems are highly reliable one of the reasons for that is use of error correction codes.

### 5. Design is easy

The design of digital systems which require use of Boolean algebra and other digital techniques is easier compared to analog designing.

### 6. Result can be reproduced easily

Since the output of digital systems unlike analog systems is independent of temperature, noise, humidity and other characteristics of components the reproducibility of results is higher in digital systems than in analog systems.

## Disadvantages of Digital Systems

- Use more energy than analog circuits to accomplish the same tasks, thus producing more heat as well.
- Digital circuits are often fragile, in that if a single piece of digital data is lost or misinterpreted the meaning of large blocks of related data can completely change.
- Digital computer manipulates discrete elements of information by means of a binary code.
- Quantization error during analog signal sampling.

## NUMBER SYSTEM

Number system is a basis for counting various items. Modern computers communicate and operate with binary numbers which use only the digits 0 & 1. Basic number system used by humans is Decimal number system.

For Ex: Let us consider decimal number 18. This number is represented in binary as 10010.

We observe that binary number system takes more digits to represent the decimal number. For large numbers we have to deal with very large binary strings. So this fact gave rise to three new number systems.

- i) Octal number systems
- ii) Hexa Decimal number system
- iii) Binary Coded Decimal number (BCD) system


To define any number system we have to specify

- Base of the number system such as 2, 8, 10 or 16.
- The base decides the total number of digits available in that number system.
- First digit in the number system is always zero and last digit in the number system is always base-1.

### Binary number system:

The binary number has a radix of 2. As  $r = 2$ , only two digits are needed, and these are 0 and 1. In binary system weight is expressed as power of 2.

#### • Example:

 

The left most bit, which has the greatest weight is called the Most Significant Bit (MSB). And the right most bit which has the least weight is called Least Significant Bit (LSB).

For Ex:  $1001.01_2 = [(1) \times 2^3] + [(0) \times 2^2] + [(0) \times 2^1] + [(1) \times 2^0] + [(0) \times 2^{-1}] + [(1) \times 2^{-2}]$

$$1001.01_2 = [1 \times 8] + [0 \times 4] + [0 \times 2] + [1 \times 1] + [0 \times 0.5] + [1 \times 0.25]$$

$$1001.01_2 = 9.25_{10}$$

### Decimal Number system

The decimal system has ten symbols: 0,1,2,3,4,5,6,7,8,9. In other words, it has a base of 10.

### Octal Number System

Digital systems operate only on binary numbers. Since binary numbers are often very long, two shorthand notations, octal and hexadecimal, are used for representing large binary numbers. Octal systems use a base or radix of 8. It uses first eight digits of decimal number system. Thus it has digits from 0 to 7.

### Hexa Decimal Number System

The hexadecimal numbering system has a base of 16. There are 16 symbols. The decimal digits 0 to 9 are used as the first ten digits as in the decimal system, followed by the letters A, B, C, D, E and F, which represent the values 10, 11,12,13,14 and 15 respectively.

Decima	Binar	Octal	Hexadeci
l	y		mal
0	0000	0	0
1	0001	1	1
2	0010	2	2
3	0011	3	3
4	0100	4	4
5	0101	5	5
6	0110	6	6
7	0111	7	7
8	1000	10	8
9	1001	11	9
10	1010	12	A
11	1011	13	B
12	1100	14	C
13	1101	15	D
14	1110	16	E
15	1111	17	F

## Number Base conversions

The human beings use decimal number system while computer uses binary number system. Therefore it is necessary to convert decimal number system into its equivalent binary.

- i) Binary to octal number conversion
- ii) Binary to hexa decimal number conversion

The binary number: 001 010 011 000 100 101 110 111  
 The octal number: 1 2 3 0 4 5 6 7

The binary number: 0001 0010 0100 1000 1001 1010 1101 1111  
 The hexadecimal number: 1 2 5 8 9 A D F

- iii) Octal to binary Conversion

Each octal number converts to 3 binary digits

Code
0 - 000
1 - 001
2 - 010
3 - 011
4 - 100
5 - 101
6 - 110
7 - 111

To convert  $653_8$  to binary, just substitute code:

6 5 3  
 ↓ ↓ ↓  
 110 101 011

iv) **0100 1111 1101 0111**

- v) Octal to Decimal conversion

Ex: convert  $4057.06_8$  to octal

$$=4 \times 8^3 + 0 \times 8^2 + 5 \times 8^1 + 7 \times 8^0 + 0 \times 8^{-1} + 6 \times 8^{-2}$$

$$=2048 + 0 + 40 + 7 + 0 + 0.0937$$

$$=2095.0937_{10}$$

vi) Decimal to Octal Conversion

Ex: convert  $378.93_{10}$  to octal

**378<sub>10</sub> to octal:** Successive division:

$$\begin{array}{r}
 8 \mid 378 \\
 \hline
 8 \mid 47 \text{ --- } 2 \\
 \hline
 8 \mid 5 \text{ --- } 7 \quad \uparrow \\
 \hline
 0 \text{ --- } 5
 \end{array}$$

$$=572_8$$

0.93<sub>10</sub> to octal :

$$0.93 \times 8 = 7.44$$

$$0.44 \times 8 = 3.52$$

$$0.53 \times 8 = 4.16$$

$$0.16 \times 8 = 1.28$$

$$=0.7341_8$$

$$378.93_{10} = 572.7341_8$$

vii) Hexadecimal to Decimal Conversion

Ex:  $5C7_{16}$  to decimal

$$= (5 \times 16^2) + (C \times 16^1) + (7 \times 16^0)$$

$$= 1280 + 192 + 7$$

$$= 147_{10}$$

viii) Decimal to Hexadecimal Conversion

Ex: 2598.67510

$$\begin{array}{r}
 16 \overline{)2598} \\
 \underline{16 \ 162} \quad -6 \\
 10 \quad \quad -2
 \end{array}$$

$$= A26_{(16)}$$

$$0.675_{10} = 0.675 \times 16 \rightarrow 10.8$$

$$= 0.800 \times 16 \rightarrow 12.8 \quad \downarrow$$

$$= 0.800 \times 16 \rightarrow 12.8$$

$$= 0.800 \times 16 \rightarrow 12.8$$

$$= 0.ACCC_{16}$$

$$2598.675_{10} = A26.ACCC_{16}$$

ix) Octal to hexadecimal conversion:

The simplest way is to first convert the given octal no. to binary & then the binary no. to hexadecimal.

Ex:  $756.603_8$

7	5	6	.	6	0	3
111	101	110	.	110	000	011
0001	1110	1110	.	1100	0001	1000
1	E	E	.	C	1	8

x) Hexadecimal to octal conversion:

First convert the given hexadecimal no. to binary & then the binary no. to octal.

Ex:  $B9F.AE_{16}$

B	9	F	.	A	E		
1011	1001	1111	.	1010	1110		
101	110	011	111	.	101	011	100
5	6	3	7	.	5	3	4

$$= 5637.534$$

### Complements:

In digital computers to simplify the subtraction operation & for logical manipulation complements are used. There are two types of complements used in each radix system.

- i) The radix complement or  $r$ 's complement
- ii) The diminished radix complement or  $(r-1)$ 's complement




## Representation of signed no.s binary arithmetic in computers:

- Two ways of rep signed no.s
  1. Sign Magnitude form
  2. Complemented form
- Two complimented forms
  1. 1's compliment form
  2. 2's compliment form

Advantage of performing subtraction by the compliment method is reduction in the hardware.( instead of addition & subtraction only adding ckt's are needed.)  
i.e, subtraction is also performed by adders only.

Instead of subtracting one no. from other the compliment of the subtrahend is added to minuend. In sign magnitude form, an additional bit called the sign bit is placed in front of the no. If the sign bit is 0, the no. is +ve, If it is a 1, the no is \_ve.

Ex:

 

Note: manipulation is necessary to add a +ve no to a -ve no

## Representation of signed no.s using 2's or 1's complement method:

If the no. is +ve, the magnitude is rep in its true binary form & a sign bit 0 is placed in front of the MSB. If the no is \_ve , the magnitude is rep in its 2's or 1's compliment form & a sign bit 1 is placed in front of the MSB.

Ex:

Given no.	Sign mag form	2's comp form	1's comp form
01101	+13	+13	+13
010111	+23	+23	+23
10111	-7	-7	-8
1101010	-42	-22	-21

### Special case in 2's comp representation:

Whenever a signed no. has a 1 in the sign bit & all 0's for the magnitude bits, the decimal equivalent is  $-2^n$ , where n is the no of bits in the magnitude .

Ex: 1000= -8 & 10000=-16

### Characteristics of 2's compliment no.s:

Properties:

1. There is one unique zero
2. 2's comp of 0 is 0
3. The leftmost bit can't be used to express a quantity . it is a 0 no. is +ve.
4. For an n-bit word which includes the sign bit there are  $(2^{n-1}-1)$  +ve integers,  $2^{n-1}$  -ve integers & one 0 , for a total of  $2^n$  unquestates.
5. Significant information is contained in the 1's of the +ve no.s & 0's of the \_ve no.s
6. A \_ve no. may be converted into a +ve no. by finding its 2's comp.

### Signed binary numbers:

Decimal	Sign 2's comp form	Sign 1's comp form	Sign mag form
+7	0111	0111	0111
+6	0110	0110	0110
+5	0101	0101	0101
+4	0100	0100	0100
+3	0011	0011	0011
+2	0010	0010	0010
+1	0011	0011	0011
+0	0000	0000	0000

-0	--	1111	1000
-1	1111	1110	1001
-2	1110	1101	1010
-3	1101	1100	1011
-4	1100	1011	1100
-5	1011	1010	1101
-6	1010	1001	1110
-7	1001	1000	1111
8	1000	--	--

## Methods of obtaining 2's comp of a no:

- In 3 ways
  1. By obtaining the 1's comp of the given no. (by changing all 0's to 1's & 1's to 0's) & then adding 1.
  2. By subtracting the given n bit no N from  $2^n$
  3. Starting at the LSB , copying down each bit upto & including the first 1 bit encountered , and complimenting the remaining bits.Ex: Express -45 in 8 bit 2's comp form

+45 in 8 bit form is 00101101

### I method:

1's comp of 00101101 & the add 1

00101101

11010010

+1

11010011

is 2's comp form

### II method:

Subtract the given no. N from  $2^n$

$2^n = 100000000$

Subtract 45 = -00101101

+1

11010011

is 2's comp

### III method:

Original no: 00101101

Copy up to First 1 bit 1

Compliment remaining : 1101001

bits

11010011

Ex:



-73.75 in 12 bit 2's complement

I method

$$\begin{array}{r}
 01001001.1100 \\
 10110110.0011 \\
 \hline
 \phantom{01001001.1100} +1 \\
 \hline
 \end{array}$$

10110110.0100 is 2's

II method:

$2^8 = 100000000.0000$

Sub 73.75 = -01001001.1100

10110110.0100 is 2's comp

III method :

Originalno : 01001001.1100

Copy up to 1'st bit 100

Comp the remaining bits: 10110110.0

$$\begin{array}{r}
 \phantom{01001001.1100} \\
 \phantom{10110110.0} \\
 \hline
 10110110.0100
 \end{array}$$

### 2's complement Arithmetic:

- The 2's comp system is used to rep -ve no.s using modulus arithmetic . The word length of a computer is fixed. i.e, if a 4 bit no. is added to another 4 bit no . the result will be only of 4 bits. Carry if any , from the fourth bit will overflow called the Modulus arithmetic.  
Ex:  $1100 + 1111 = 1011$
- In the 2's compl subtraction, add the 2's comp of the subtrahend to the minuend . If there is a carry out , ignore it , look at the sign bit I.e, MSB of the sum term .If the MSB is a 0, the result is positive.& it is in true binary form. If the MSB is a 1 ( carry in or no carry at all) the result is negative.& is in its 2's comp form. Take its 2's comp to find its magnitude in binary.

**Ex:** Subtract 14 from 46 using 8 bit 2's comp arithmetic:

$$\begin{array}{r}
 +14 = 00001110 \\
 -14 = 11110010 \quad \text{2's comp} \\
 \hline
 +46 = 00101110 \\
 -14 = +11110010 \quad \text{2's comp form of -14} \\
 \hline
 \hline
 \end{array}$$

$$\begin{array}{r} \hline -32 \quad (1)00100000 \quad \text{ignore carry} \\ \hline \end{array}$$

Ignore carry, The MSB is 0. so the result is +ve. & is in normal binary form. So the result is +00100000=+32.

**EX:** Add -75 to +26 using 8 bit 2's comp arithmetic

$$\begin{array}{r} +75 = 01001011 \\ -75 = 10110101 \quad \text{2's comp} \\ +26 = 00011010 \\ -75 = +10110101 \quad \text{2's comp form of -75} \end{array}$$

$$\begin{array}{r} \hline -49 \quad 11001111 \quad \text{No carry} \\ \hline \end{array}$$

No carry, MSB is a 1, result is -ve & is in 2's comp. The magnitude is 2's comp of 11001111. i.e, 00110001 = 49. so result is -49

**Ex:** add -45.75 to +87.5 using 12 bit arithmetic

$$\begin{array}{r} +87.5 = 01010111.1000 \\ -45.75 = +11010010.0100 \end{array}$$

$$\begin{array}{r} \hline -41.75 \quad (1)00101001.1100 \quad \text{ignore carry} \\ \hline \text{MSB is 0, result is +ve.} = +41.75 \end{array}$$

### 1's compliment of n number:

- It is obtained by simply complimenting each bit of the no., & also, 1's comp of a no, is subtracting each bit of the no. from 1. This complemented value rep the -ve of the original no. One of the difficulties of using 1's comp is its rep of zero. Both 00000000 & its 1's comp 11111111 rep zero.
- The 00000000 called +ve zero & 11111111 called -ve zero.

Ex: -99 & -77.25 in 8 bit 1's comp

$$\begin{array}{r} +99 = 01100011 \\ -99 = 10011100 \end{array}$$

$$\begin{array}{r} +77.25 = 01001101.0100 \\ -77.25 = 10110010.1011 \end{array}$$

### 1's compliment arithmetic:

In 1's comp subtraction, add the 1's comp of the subtrahend to the minuend. If there is a carryout, bring the carry around & add it to the LSB called the **end around carry**. Look at the sign bit (MSB). If this is a 0, the result is +ve & is in true binary. If the MSB is a 1 (carry or no carry), the result is -ve & is in its 1's comp form. Take its 1's comp to get the magnitude in binary.

Ex: Subtract 14 from 25 using 8 bit 1's E↓: ADD -25 to +14

$$\begin{array}{r}
 25 = 00011001 \quad +14 = 00001110 \\
 -45 = 11110001 \quad -25 = +11100110 \\
 \hline
 +11 \quad (1)00001010 \quad -11 \quad 11110100 \\
 \\
 +1 \\
 \hline
 00001011 \quad \text{No carry MSB = 1} \\
 \text{result = -ve = -11}_{10}
 \end{array}$$

MSB is a 0 so result is +ve (binary )

=+11<sub>10</sub>

**Binary codes**

Binary codes are codes which are represented in binary system with modification from the original ones.

- Weighted Binary codes
- Non Weighted Codes

Weighted binary codes are those which obey the positional weighting principles, each position of the number represents a specific weight. The binary counting sequence is an example.

Decimal	BCD 8421	Excess-3	84-2-1	2421	5211	Bi-Quinary 5043210		5	0	4	3	2	1	0
0	0000	0011	0000	0000	0000	0100001		0	X					X
1	0001	0100	0111	0001	0001	0100010		1	X				X	
2	0010	0101	0110	0010	0011	0100100		2	X			X		
3	0011	0110	0101	0011	0101	0101000		3	X		X			
4	0100	0111	0100	0100	0111	0110000		4	X	X				
5	0101	1000	1011	1011	1000	1000001		5	X					X
6	0110	1001	1010	1100	1010	1000010		6	X				X	
7	0111	1010	1001	1101	1100	1000100		7	X			X		
8	1000	1011	1000	1110	1110	1001000		8	X		X			
9	1001	1111	1111	1111	1111	1010000		9	X	X				

**Reflective Code**

A code is said to be reflective when code for 9 is complement for the code for 0, and

so is for 8 and 1 codes, 7 and 2, 6 and 3, 5 and 4. Codes 2421, 5211, and excess-3 are reflective, whereas the 8421 code is not.

### Sequential Codes

A code is said to be sequential when two subsequent codes, seen as numbers in binary representation, differ by one. This greatly aids mathematical manipulation of data. The 8421 and Excess-3 codes are sequential, whereas the 2421 and 5211 codes are not.

### Non weighted codes

Non weighted codes are codes that are not positionally weighted. That is, each position within the binary number is not assigned a fixed value. Ex: Excess-3 code

### Excess-3 Code

Excess-3 is a non weighted code used to express decimal numbers. The code derives its name from the fact that each binary code is the corresponding 8421 code plus 0011(3).

### Gray Code

The gray code belongs to a class of codes called minimum change codes, in which only one bit in the code changes when moving from one code to the next. The Gray code is non-weighted code, as the position of bit does not contain any weight. The gray code is a reflective digital code which has the special property that any two subsequent numbers codes differ by only one bit. This is also called a unit-distance code. In digital Gray code has got a special place.

Decimal Number	Binary Code	Gray Code	Decimal Number	Binary Code	Gray Code
0	0000	0000	8	1000	1100
1	0001	0001	9	1001	1101
2	0010	0011	10	1010	1111
3	0011	0010	11	1011	1110
4	0100	0110	12	1100	1010
5	0101	0111	13	1101	1011
6	0110	0101	14	1110	1001
7	0111	0100	15	1111	1000



## Binary to Gray Conversion

- Gray Code MSB is binary code MSB.
- Gray Code MSB-1 is the XOR of binary code MSB and MSB-1.
- MSB-2 bit of gray code is XOR of MSB-1 and MSB-2 bit of binary code.
- MSB-N bit of gray code is XOR of MSB-N-1 and MSB-N bit of binary code.

## 8421 BCD code ( Natural BCD code):

Each decimal digit 0 through 9 is coded by a 4 bit binary no. called natural binary codes. Because of the 8,4,2,1 weights attached to it. It is a weighted code & also sequential . it is useful for mathematical operations. The advantage of this code is its ease of conversion to & from decimal. It is less efficient than the pure binary, it requires more bits.

Ex: 14 → 1110 in binary

But as 0001 0100 in 8421 code.

The disadvantage of the BCD code is that , arithmetic operations are more complex than they are in pure binary . There are 6 illegal combinations 1010,1011,1100,1101,1110,1111 in these codes, they are not part of the 8421 BCD code system . The disadvantage of 8421 code is, the rules of binary addition 8421 no, but only to the individual 4 bit groups.

## BCD Addition:

It is individually adding the corresponding digits of the decimal no,s expressed in 4 bit binary groups starting from the LSD . If there is no carry & the sum term is not an illegal code , no correction is needed .If there is a carry out of one group to the next group or if the sum term is an illegal code then  $6_{10}(0100)$  is added to the sum term of that group & the resulting carry is added to the next group.

Ex: Perform decimal additions in 8421 code

(a) 25+13

In BCD      25 = 0010 0101

In BCD      +13 = +0001 0011

\_\_\_\_\_

38      0011 1000

No carry , no illegal code .This is the corrected sum

(b). 679.6 + 536.8

679.6 = 0110 0111 1001 .0110 in BCD  
 +536.8 = +0101 0011 0010 .1000 in BCD

-----  
 1216.4      1011      1010      0110      .1110      illegal codes  
                  +0110      + 0011      +0110      . + 0110      add 0110 to each

(1)0001      (1)0000      (1)0101      . (1)0100      propagate carry  
 /              /              /              /  
 +1              +1              +1              +1

-----  
 0001      0010      0001      0110      .      0100

1              2              1              6              .      4

**BCD Subtraction:**

Performed by subtracting the digits of each 4 bit group of the subtrahend the digits from the corresponding 4- bit group of the minuend in binary starting from the LSD . if there is no borrow from the next group , then  $6_{10}(0110)$  is subtracted from the difference term of this group.

(a)38-15

In BCD      38= 0011      1000  
 In BCD      -15 = -0001      0101

-----  
 23      0010      0011      TOPPERWorld

No borrow, so correct difference.

(b) 206.7-147.8

206.7 = 0010 0000 0110 . 0111      in BCD  
 -147.8 = -0001 0100 0111 . 0110      in BCD

-----  
 58.9      0000 1011 1110 . 1111      borrows are present  
                  -0110 -0110 .      -0110      subtract 0110

-----  
 0101 1000 . 1001

### BCD Subtraction using 9's & 10's compliment methods:

Form the 9's & 10's compliment of the decimal subtrahend & encode that no. in the 8421 code . the resulting BCD no.s are then added.

EX: 305.5 – 168.8

$$\begin{array}{r}
 305.5 = 305.5 \\
 -168.8 = +83.1 \quad \text{9's comp of -168.8} \\
 \hline
 (1)136.6 \\
 \quad \quad +1 \quad \quad \text{end around carry} \\
 \quad \quad \mathbf{136.7} \quad \quad \text{corrected difference} \\
 305.5_{10} = 0011 \ 0000 \ 0101 \ . \ 0101 \\
 +831.1_{10} = +1000 \ 0011 \ 0001 \ . \ 0001 \quad \text{9's comp of 168.8 in BCD} \\
 \hline
 +1011 \ 0011 \ 0110 \ . \ 0110 \quad \text{1011 is illegal code} \\
 +0110 \quad \quad \quad \quad \quad \text{add 0110} \\
 \hline
 (1)0001 \ 0011 \ 0110 \ . \ 0110 \\
 \quad \quad \quad \quad \quad \quad \quad \quad +1 \quad \text{End around carry} \\
 \hline
 0001 \ 0011 \ 0110 \ . \ 0111 \\
 \quad \quad \quad \quad \quad \quad \quad \quad = 136.7
 \end{array}$$

### Excess three(xs-3)code:

It is a non-weighted BCD code .Each binary codeword is the corresponding 8421 codeword plus 0011(3).It is a sequential code & therefore , can be used for arithmetic operations..It is a self-complementing code.s o the subtraction by the method of compliment addition is more direct in xs-3 code than that in 8421 code. The xs-3 code has six invalid states 0000,0010,1101,1110,1111.. It has interesting properties when used in addition & subtraction.

### Excess-3 Addition:

Add the xs-3 no.s by adding the 4 bit groups in each column starting from the LSD. If there is no carry starting from the addition of any of the 4-bit groups , subtract 0011 from the sum term of those groups ( because when 2 decimal digits are added in xs-3 & there is no carry , result in xs-6). If there is a carry out, add 0011 to the sum term of those groups( because when there is a carry, the invalid states are skipped and the result is normal binary).

EX:	37	0110	1010	
	+28	+0101	1011	
-----				
	65	1011	(1)0101	carry generated
		+1	←	propagate carry
-----				
		1100	0101	add 0011 to correct 0101 &
		-0011	+0011	subtract 0011 to correct 1100
-----				
		1001	1000	=65 <sub>10</sub>

**Excess -3 (XS-3) Subtraction:**

Subtract the xs-3 no.s by subtracting each 4 bit group of the subtrahend from the corresponding 4 bit group of the minuend starting from the LSD .if there is no borrow from the next 4-bit group add 0011 to the difference term of such groups (because when decimal digits are subtracted in xs-3 & there is no borrow , result is normal binary). If there is a borrow , subtract 0011 from the differenceterm(b coz taking a borrow is equivalent to adding six invalid states , result is in xs-6)

Ex: 267-175

267 =	0101	1001	1010	
-175 =	-0100	1010	1000	
-----				
	0000	1111	0010	
	+0011	-0011	+0011	
-----				
	0011	1100	+0011	=92 <sub>10</sub>

**Xs-3 subtraction using 9's & 10's compliment methods:**

Subtraction is performed by the 9's compliment or 10's compliment

Ex:687-348 The subtrahend (348) xs -3 code & its compliment are:

9's comp of 348 = 651

Xs-3 code of 348 = 0110 0111 1011

1's comp of 348 in xs-3 = 1001 1000 0100

Xs=3 code of 348 in xs=3 = 1001 1000 0100

$$\begin{array}{r} 687 \\ -348 \end{array} \rightarrow \begin{array}{r} 687 \\ +651 \text{ 9's compl of 348} \end{array}$$


339		(1)338			
		+1 end around carry			
		339		corrected difference in decimal	
1001	1011	1010	687 in xs-3		
+1001	1000	0100	1's comp 348 in xs-3		
(1)0010	(1)0011	1110	carry generated		
+1	+1	propagate carry			
(1)0011	0010	1110	+1	end around carry	
0011	0011	1111	(correct 1111 by sub0011 and		
+0011	+0011	+0011	correct both groups of 0011 by		
0011	0011	1100	adding 0011)		
0110	0110	1100	corrected diff in xs-3 = 330 <sub>10</sub>		

**The Gray code (reflective –code):**

Gray code is a non-weighted code & is not suitable for arithmetic operations. It is not a BCD code . It is a cyclic code because successive code words in this code differ in one bit position only i.e, it is a unit distance code.Popular of the unit distance code.It is also a reflective code i.e,both reflective & unit distance. The n least significant bits for  $2^n$  through  $2^{n+1}-1$  are the mirror images of those for 0 through  $2^n-1$ .An N bit gray code can be obtained by reflecting an N- 1 bit code about an axis at the end of the code, & putting the MSB of 0 above the axis & the MSB of 1 below the axis.

Reflection of gray codes:

Gray Code				Decimal	4 bit binary
1 bit	2 bit	3 bit	4 bit		
0	00	000	0000	0	0000
1	01	001	0001	1	0001
	11	011	0011	2	0010
	10	010	0010	3	0011
		110	0110	4	0100
		111	0111	5	0101
		101	0101	6	0110
		110	0100	7	0111
			1100	8	1000
			1101	9	1001
			1111	10	1010
			1110	11	1011
			1010	12	1100
			1011	13	1101
			1001	14	1110
			1000	15	1111

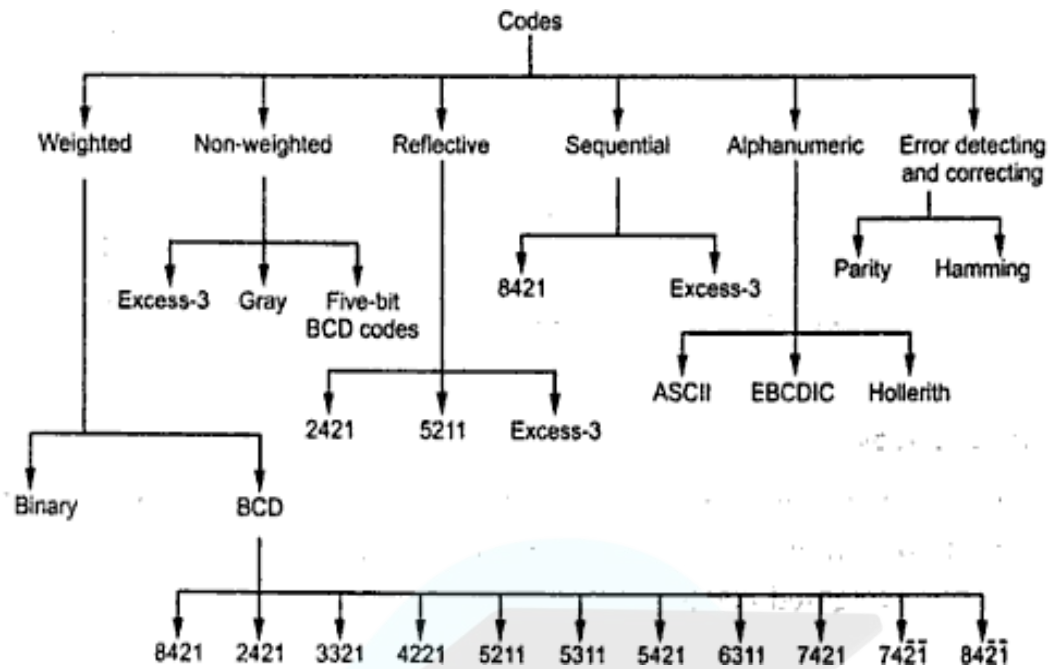

Binary codes block diagram

**Error – Detecting codes:** When binary data is transmitted & processed, it is susceptible to noise that can alter or distort its contents. The 1's may get changed to 0's & 1's, because digital systems must be accurate to the digit, error can pose a problem. Several schemes have been devised to detect the occurrence of a single bit error in a binary word, so that whenever such an error occurs the concerned binary word can be corrected & retransmitted.

**Parity:** The simplest techniques for detecting errors is that of adding an extra bit known as parity bit to each word being transmitted. Two types of parity: Odd parity, even parity. For odd parity, the parity bit is set to a '0' or a '1' at the transmitter such that the total no. of 1 bit in the word including the parity bit is an odd no. For even parity, the parity bit is set to a '0' or a '1' at the transmitter such that the parity bit is an even no.

Decimal	8421 code	Odd parity	Even parity
0	0000	1	0
1	0001	0	1
2	0010	0	1
3	0011	1	0
4	0100	0	1
5	0100	1	0
6	0110	1	0
7	0111	0	1
8	1000	0	1
9	1001	1	0

When the digit data is received, a parity checking circuit generates an error signal if the total no of 1's is even in an odd parity system or odd in an even parity system. This parity check can always detect a single bit error but cannot detect 2 or more errors within the same word. Odd parity is used more often than even parity does not detect the situation. → here all 0's are created by a short ckt or some other fault condition.

Ex: Even parity scheme

(a) 10101010 (b) 11110110 (c) 10111001

Ans:

- (a) No. of 1's in the word is even is 4 so there is no error
- (b) No. of 1's in the word is even is 6 so there is no error
- (c) No. of 1's in the word is odd is 5 so there is error

Ex: odd parity

(a) 10110111 (b) 10011010 (c) 11101010

Ans:

- (a) No. of 1's in the word is even is 6 so word has error
- (b) No. of 1's in the word is even is 4 so word has error
- (c) No. of 1's in the word is odd is 5 so there is no error

### Checksums:

Simple parity can't detect two errors within the same word. To overcome this, use a sort of 2 dimensional parity. As each word is transmitted, it is added to the sum of the previously transmitted words, and the sum retained at the transmitter end. At the end of transmission, the sum called the check sum. Up to that time sent to the receiver. The receiver can check its sum with the transmitted sum. If the two sums are the same, then no errors were detected at the receiver end. If there is an error, the receiving location can ask for retransmission of the entire data, used in teleprocessing systems.

### Block parity:

Block of data shown is create the row & column parity bits for the data using odd parity. The parity bit 0 or 1 is added column wise & row wise such that the total no. of 1's in each column & row including the data bits & parity bit is odd as



Data	Parity bit	data
10110	0	10110
10001	1	10001
10101	0	10101
00010	0	00010
11000	1	11000
00000	1	00000
11010	0	11010

### Error –Correcting Codes:

A code is said to be an error –correcting code, if the code word can always be deduced from an erroneous word. For a code to be a single bit error correcting code, the minimum distance of that code must be three. The minimum distance of that code is the smallest no. of bits by which any two code words must differ. A code with minimum distance of 3 can't only correct single bit errors but also detect ( can't correct) two bit errors, The key to error correction is that it must be possible to detect & locate erroneous that it must be possible to detect & locate erroneous digits. If the location of an error has been determined. Then by complementing the erroneous digit, the message can be corrected , error correcting , code is the Hamming code , In this , to each group of m information or message or data bits, K parity checking bits denoted by P1,P2, -----pk located at positions  $2^{k-1}$  from left are added to form an (m+k) bit code word. To correct the error, k parity checks are performed on selected digits of each code word, & the position of the error bit is located by forming an error word, & the error bit is then complemented. The k bit error word is generated by putting a 0 or a 1 in the  $2^{k-1}$ th position depending upon whether the check for parity involving the parity bit  $P_k$  is satisfied or not. Error positions & their corresponding values :

Error Position	For 15 bit code C <sub>4</sub> C <sub>3</sub> C <sub>2</sub> C <sub>1</sub>	For 12 bit code C <sub>4</sub> C <sub>3</sub> C <sub>2</sub> C <sub>1</sub>	For 7 bit code C <sub>3</sub> C <sub>2</sub> C <sub>1</sub>
0	0000	0000	000
1	0001	0001	001
2	0010	0010	010
3	0011	0011	011
4	0100	0100	100
5	0101	0101	101
6	0 1 10	0 1 10	1 10
7	0 1 1 1	0 1 1 1	1 1 1
8	1 0 0 0	1 0 0 0	
9	1 0 0 1	1 0 0 1	
10	1 0 1 0	1 0 1 0	
11	1 0 1 1	1 0 1 1	
12	1 1 0 0	1 1 0 0	
13	1 1 0 1		
14	1 1 1 0		
15	1 1 1 1		

### 7-bit Hamming code:

To transmit four data bits, 3 parity bits located at positions  $2^0$   $2^1$  &  $2^2$  from left are added to make a 7 bit codeword which is then transmitted.

The word format

P <sub>1</sub>	P <sub>2</sub>	D <sub>3</sub>	P <sub>4</sub>	D <sub>5</sub>	D <sub>6</sub>	D <sub>7</sub>
----------------	----------------	----------------	----------------	----------------	----------------	----------------

D—Data bits P-

Parity bits

Decimal Digit	For BCD P <sub>1</sub> P <sub>2</sub> D <sub>3</sub> P <sub>4</sub> D <sub>5</sub> D <sub>6</sub> D <sub>7</sub>	For Excess-3 P <sub>1</sub> P <sub>2</sub> D <sub>3</sub> P <sub>4</sub> D <sub>5</sub> D <sub>6</sub> D <sub>7</sub>
0	0 0 0 0 0 0 0	1 0 0 0 0 1 1
1	1 1 0 1 0 0 1	1 0 0 1 1 0 0
2	0 1 0 1 0 1 1	0 1 0 0 1 0 1
3	1 0 0 0 0 1 1	1 1 0 0 1 1 0
4	1 0 0 1 1 0 0	0 0 0 1 1 1 1
5	0 1 0 0 1 0 1	1 1 1 0 0 0 0
6	1 1 0 0 1 1 0	0 0 1 1 0 0 1
7	0 0 0 1 1 1 1	1 0 1 1 0 1 0
8	1 1 1 0 0 0 0	0 1 1 0 0 1 1
9	0 0 1 1 0 0 1	0 1 1 1 1 0 0

Ex: Encode the data bits 1101 into the 7 bit even parity Hamming Code

The bit pattern is

$P_1P_2D_3P_4D_5D_6D_7$

1 1 0 1

Bits 1,3,5,7 ( $P_1$  111) must have even parity, so  $P_1=1$

Bits 2, 3, 6, 7( $P_2$  101) must have even parity, so  $P_2=0$

Bits 4,5,6,7 ( $P_4$  101) must have even parity, so  $P_4=0$

The final code is 1010101

EX: Code word is 1001001

Bits 1,3,5,7 ( $C_1$  1001) →no error →put a 0 in the 1's position→ $C_1=0$

Bits 2, 3, 6, 7( $C_2$  0001)) → error →put a 1 in the 2's position→ $C_2=1$

Bits 4,5,6,7 ( $C_4$  1001)) →no error →put a 0 in the 4's position→ $C_3=0$

**15-bit Hamming Code:** It transmit 11 data bits, 4 parity bits located  $2^0 2^1 2^2 2^3$

Word format is

$P_1$	$P_2$	$D_3$	$P_4$	$D_5$	$D_6$	$D_7$	$P_8$	$D_9$	$D_{10}$	$D_{11}$	$D_{12}$	$D_{13}$	$D_{14}$	$D_{15}$
-------	-------	-------	-------	-------	-------	-------	-------	-------	----------	----------	----------	----------	----------	----------

**12-Bit Hamming Code:**It transmit 8 data bits, 4 parity bits located at position  $2^0 2^1 2^2 2^3$

Word format is









$P_1$	$P_2$	$D_3$	$P_4$	$D_5$	$D_6$	$D_7$	$P_8$	$D_9$	$D_{10}$	$D_{11}$	$D_{12}$
-------	-------	-------	-------	-------	-------	-------	-------	-------	----------	----------	----------

### Alphanumeric Codes:

These codes are used to encode the characteristics of alphabet in addition to the decimal digits. It is used for transmitting data between computers & its I/O device such as printers, keyboards & video display terminals. Popular modern alphanumeric codes are ASCII code & EBCDIC code.

## Digital Logic Gates

Boolean functions are expressed in terms of AND, OR, and NOT operations, it is easier to implement a Boolean function with these type of gates.

Name	Graphic symbol	Algebraic function	Truth table															
AND		$F = x \cdot y$	<table border="1"> <thead> <tr> <th>x</th> <th>y</th> <th>F</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>1</td></tr> </tbody> </table>	x	y	F	0	0	0	0	1	0	1	0	0	1	1	1
x	y	F																
0	0	0																
0	1	0																
1	0	0																
1	1	1																
OR		$F = x + y$	<table border="1"> <thead> <tr> <th>x</th> <th>y</th> <th>F</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>1</td></tr> </tbody> </table>	x	y	F	0	0	0	0	1	1	1	0	1	1	1	1
x	y	F																
0	0	0																
0	1	1																
1	0	1																
1	1	1																
Inverter		$F = x'$	<table border="1"> <thead> <tr> <th>x</th> <th>F</th> </tr> </thead> <tbody> <tr><td>0</td><td>1</td></tr> <tr><td>1</td><td>0</td></tr> </tbody> </table>	x	F	0	1	1	0									
x	F																	
0	1																	
1	0																	
Buffer		$F = x$	<table border="1"> <thead> <tr> <th>x</th> <th>F</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td></tr> </tbody> </table>	x	F	0	0	1	1									
x	F																	
0	0																	
1	1																	
NAND		$F = (xy)'$	<table border="1"> <thead> <tr> <th>x</th> <th>y</th> <th>F</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </tbody> </table>	x	y	F	0	0	1	0	1	1	1	0	1	1	1	0
x	y	F																
0	0	1																
0	1	1																
1	0	1																
1	1	0																
NOR		$F = (x + y)'$	<table border="1"> <thead> <tr> <th>x</th> <th>y</th> <th>F</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </tbody> </table>	x	y	F	0	0	1	0	1	0	1	0	0	1	1	0
x	y	F																
0	0	1																
0	1	0																
1	0	0																
1	1	0																
Exclusive-OR (XOR)		$F = xy' + x'y$ $= x \oplus y$	<table border="1"> <thead> <tr> <th>x</th> <th>y</th> <th>F</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </tbody> </table>	x	y	F	0	0	0	0	1	1	1	0	1	1	1	0
x	y	F																
0	0	0																
0	1	1																
1	0	1																
1	1	0																
Exclusive-NOR or equivalence		$F = xy + x'y'$ $= (x \oplus y)'$	<table border="1"> <thead> <tr> <th>x</th> <th>y</th> <th>F</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>1</td></tr> </tbody> </table>	x	y	F	0	0	1	0	1	0	1	0	0	1	1	1
x	y	F																
0	0	1																
0	1	0																
1	0	0																
1	1	1																

## Properties of XOR Gates

- XOR (also  $\oplus$ ) : the “not-equal” function
- $XOR(X,Y) = X \oplus Y = X'Y + XY'$
- Identities:
  - $X \oplus 0 = X$
  - $X \oplus 1 = X'$
  - $X \oplus X = 0$
  - $X \oplus X' = 1$
- Properties:
  - $X \oplus Y = Y \oplus X$
  - $(X \oplus Y) \oplus W = X \oplus (Y \oplus W)$


## Universal Logic Gates

NAND and NOR gates are called Universal gates. All fundamental gates (NOT, AND, OR) can be realized by using either only NAND or only NOR gate. A universal gate provides flexibility and offers enormous advantage to logic designers.
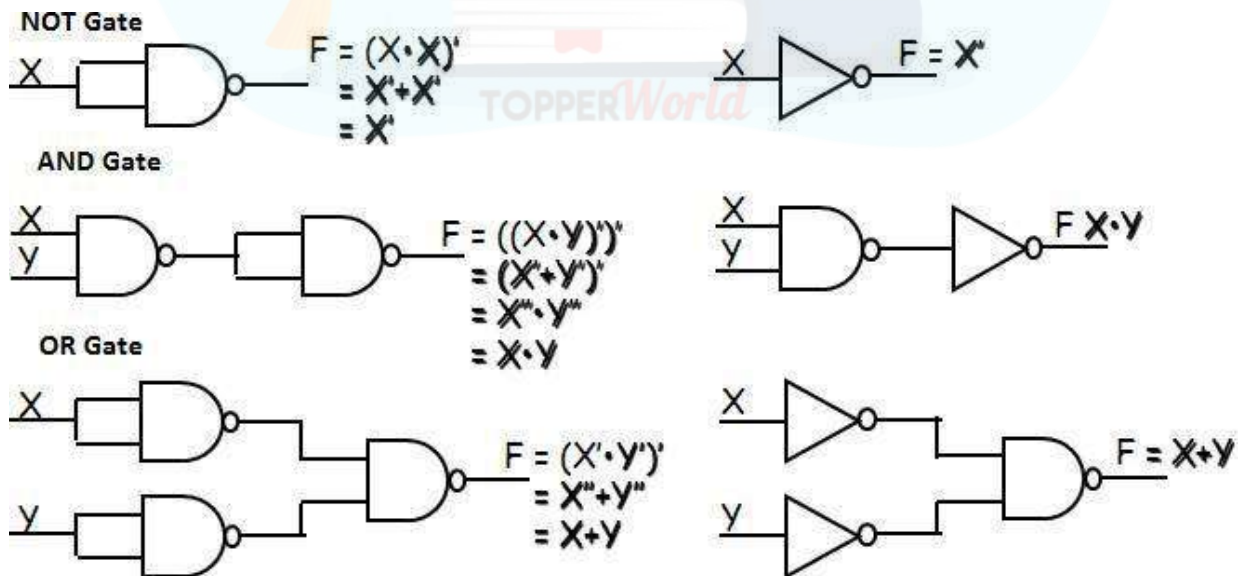
### NAND as a Universal Gate

NAND Known as a “universal” gate because ANY digital circuit can be implemented with NAND gates alone.

To prove the above, it suffices to show that AND, OR, and NOT can be implemented using NAND gates only.



**Boolean Algebra:** In 1854, George Boole developed an algebraic system now called Boolean algebra. In 1938, Claude E. Shannon introduced a two-valued Boolean algebra called switching algebra that represented the properties of bistable electrical switching circuits. For the formal definition of Boolean algebra, we shall employ the postulates formulated by E. V. Huntington in 1904.

Boolean algebra is a system of mathematical logic. It is an algebraic system consisting of the set of elements (0, 1), two binary operators called OR, AND, and one unary operator NOT. It is the basic mathematical tool in the analysis and synthesis of switching circuits. It is a way to express logic functions algebraically.

Boolean algebra, like any other deductive mathematical system, may be defined with a set of elements, a set of operators, and a number of unproved axioms or postulates. A *set* of elements is any collection of objects having a common property. If  $S$  is a set and  $x$  and  $y$  are certain objects, then  $x \in S$  denotes that  $x$  is a member of the set  $S$ , and  $y \notin S$  denotes that  $y$  is not an element of  $S$ . A set with a denumerable number of elements is specified by braces:  $A = \{1,2,3,4\}$ , *i.e.* the elements of set  $A$  are the numbers 1, 2, 3, and 4. A *binary operator* defined on a set  $S$  of elements is a rule that assigns to each pair of elements from  $S$  a unique element from  $S$ . Example: In  $a*b=c$ , we say that  $*$  is a binary operator if it specifies a rule for finding  $c$  from the pair  $(a,b)$  and also if  $a, b, c \in S$ .

### Axioms and laws of Boolean algebra

Axioms or Postulates of Boolean algebra are a set of logical expressions that we accept without proof and upon which we can build a set of useful theorems.

	AND Operation	OR Operation	NOT Operation
Axiom1 :	$0 \cdot 0 = 0$	$0 + 0 = 0$	$0 = 1$
Axiom2:	$0 \cdot 1 = 0$	$0 + 1 = 1$	$1 = 0$
Axiom3:	$1 \cdot 0 = 0$	$1 + 0 = 1$	
Axiom4:	$1 \cdot 1 = 1$	$1 + 1 = 1$	

#### AND Law

- Law1:  $A \cdot 0 = 0$  (Null law)
- Law2:  $A \cdot 1 = A$  (Identity law)
- Law3:  $A \cdot A = A$  (Idempotence law)

#### OR Law

- Law1:  $A + 0 = A$
- Law2:  $A + 1 = 1$
- Law3:  $A + A = A$  (Idempotence law)

**CLOSURE:** The Boolean system is *closed* with respect to a binary operator if for every pair of Boolean values, it produces a Boolean result. For example, logical AND is closed in the Boolean system because it accepts only Boolean operands and produces only Boolean results.

\_ A set  $S$  is closed with respect to a binary operator if, for every pair of elements of  $S$ , the binary operator specifies a rule for obtaining a unique element of  $S$ .

\_ For example, the set of natural numbers  $N = \{1, 2, 3, 4, \dots, 9\}$  is closed with respect to the binary operator plus (+) by the rule of arithmetic addition, since for any  $a, b \in N$  we obtain a unique  $c \in N$  by the operation  $a + b = c$ .

### ASSOCIATIVE LAW:

A binary operator  $*$  on a set  $S$  is said to be associative whenever  $(x * y) * z = x * (y * z)$  for all  $x, y, z \in S$ , for all Boolean values  $x, y$  and  $z$ .

### COMMUTATIVE LAW:

A binary operator  $*$  on a set  $S$  is said to be commutative whenever  $x * y = y * x$  for all  $x, y, z \in S$

### IDENTITY ELEMENT:

A set  $S$  is said to have an identity element with respect to a binary operation  $*$  on  $S$  if there exists an element  $e \in S$  with the property  $e * x = x * e = x$  for every  $x \in S$

### BASIC IDENTITIES OF BOOLEAN ALGEBRA

- *Postulate 1(Definition):* A Boolean algebra is a closed algebraic system containing a set  $K$  of two or more elements and the two operators  $\cdot$  and  $+$  which refer to logical AND and logical OR •  $x + 0 = x$
- $x \cdot 0 = 0$
- $x + 1 = 1$
- $x \cdot 1 = x$
- $x + x = x$
- $x \cdot x = x$
- $x + x' = 1$
- $x \cdot x' = 0$
- $x + y = y + x$
- $xy = yx$
- $x + (y + z) = (x + y) + z$
- $x(yz) = (xy)z$
- $x(y + z) = xy + xz$
- $x + yz = (x + y)(x + z)$
- $(x + y)' = x'y'$
- $(xy)' = x' + y'$

- $(x')' = x$

### DeMorgan's Theorem

**(a)**  $(a + b)' = a'b'$

**(b)**  $(ab)' = a' + b'$

### Generalized DeMorgan's Theorem

(a)  $(a + b + \dots + z)' = a'b' \dots z'$

(b)  $(a.b \dots z)' = a' + b' + \dots + z'$

### Basic Theorems and Properties of Boolean algebra Commutative law

Law1:  $A+B=B+A$

Law2:  $A.B=B.A$

### Associative law

Law1:  $A + (B + C) = (A + B) + C$

Law2:  $A(B.C) = (A.B)C$

### Distributive law

Law1:  $A.(B + C) = AB + AC$

Law2:  $A + BC = (A + B).(A + C)$

### Absorption law

Law1:  $A + AB = A$

Law2:  $A(A + B) = A$

Solution:  $\frac{A(1+B)}{A}$

Solution:  $\frac{A.A+A.B}{A}$   
 $\frac{A+A.B}{A}$   
 $\frac{A(1+B)}{A}$

### Consensus Theorem

Theorem1.  $AB + A'C + BC = AB + A'C$  Theorem2.  $(A+B).(A'+C).(B+C) = (A+B).(A'+C)$

The BC term is called the consensus term and is redundant. The consensus term is formed from a PAIR OF TERMS in which a variable (A) and its complement (A') are present; the consensus term is formed by multiplying the two terms and leaving out the selected variable and its complement

Consensus Theorem1 Proof:

$$AB + A'C + BC = AB + A'C + (A + A')BC$$

$$= AB + A'C + ABC + A'BC$$



$$=AB(1+C)+A'C(1+B)$$

$$= AB+ A'C$$

### Principle of Duality

Each postulate consists of two expressions statement one expression is transformed into the other by interchanging the operations (+) and (·) as well as the identity elements 0 and 1. Such expressions are known as duals of each other.

If some equivalence is proved, then its dual is also immediately true.

If we prove:  $(x.x)+(x'+x')=1$ , then we have by duality:  $(x+x)·(x'·x')=0$

The Huntington postulates were listed in pairs and designated by part (a) and part (b) in below table.

**Table for Postulates and Theorems of Boolean algebra**


Part-A	Part-B
$A+0=A$	$A·0=0$
$A+1=1$	$A·1=A$
$A+A=A$ (Impotence law)	$A·A=A$ (Impotence law)
$A+\bar{A}1$	$A·\bar{A}0$
$\bar{\bar{A}}$ (double inversion law)	--
<b>Commutative law:</b> $A+B=B+A$	$A·B=B·A$
<b>Associative law:</b> $A+(B+C)=(A+B)+C$	$A(B·C)=(A·B)C$
<b>Distributive law:</b> $A·(B+C)=AB+AC$	$A+(B·C)=(A+B)·(A+C)$
<b>Absorption law:</b> $A+AB=A$	$A(A+B)=A$
<b>DeMorgan Theorem:</b> $\overline{(A+B)} = \bar{A}·\bar{B}$	$\overline{(A·B)} = \bar{A}+\bar{B}$
<b>Redundant Literal Rule:</b> $A+\bar{A}B=A+B$	$A·(\bar{A}+B)=AB$
<b>Consensus Theorem:</b> $AB+A'C+BC=AB+A'C$	$(A+B)·(A'+C)·(B+C)=(A+B)·(A'+C)$

### Boolean Function

Boolean algebra is an algebra that deals with binary variables and logic operations.

A Boolean function described by an algebraic expression consists of binary variables, the constants 0 and 1, and the logic operation symbols.

 For a given value of the binary variables, the function can be equal to either 1 or 0.



Consider an example for the Boolean function

$$F1 = x + y'z$$


The function  $F_1$  is equal to 1 if  $x$  is equal to 1 or if both  $y'$  and  $z$  are equal to 1.  $F_1$  is equal to 0 otherwise. The complement operation dictates that when  $y' = 1$ ,  $y = 0$ . Therefore,  $F_1 = 1$  if  $x = 1$  or if  $y = 0$  and  $z = 1$ .

A Boolean function expresses the logical relationship between binary variables and is evaluated by determining the binary value of the expression for all possible values of the variables.

A Boolean function can be represented in a truth table. The number of rows in the truth table is  $2^n$ , where  $n$  is the number of variables in the function. The binary combinations for the truth table are obtained from the binary numbers by counting from 0 through  $2^n - 1$ .

Truth Table for  $F_1$

x	y	z	$F_1$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

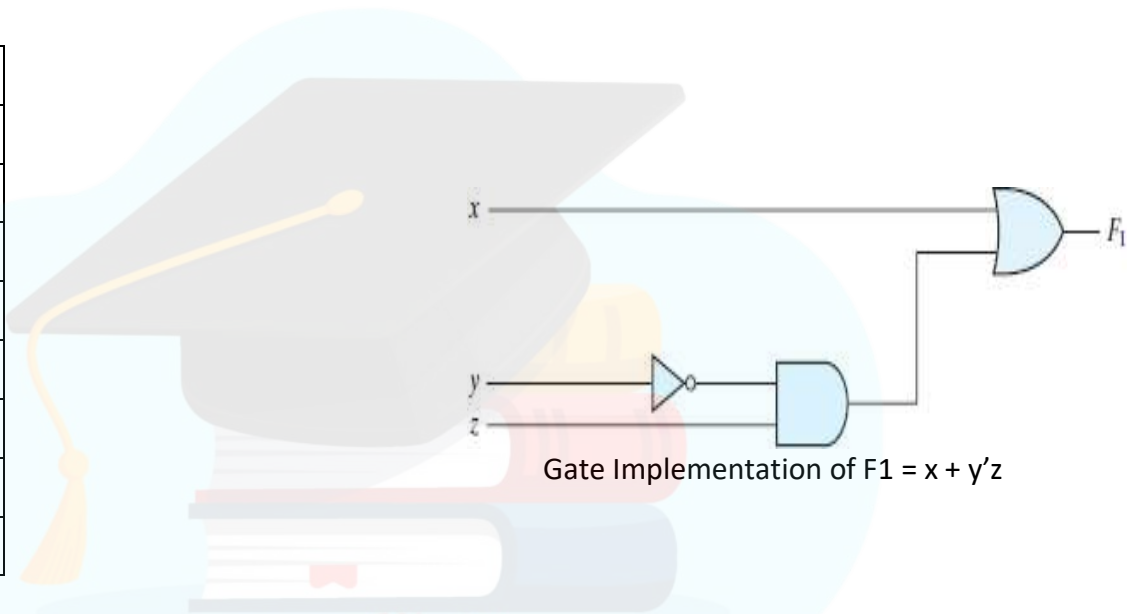

**Note:**

Q: Let a function  $F()$  depend on  $n$  variables. How many rows are there in the truth table of  $F()$  ?

A:  $2^n$  rows, since there are  $2^n$  possible binary patterns/combinations for the  $n$  variables.

Truth Tables

- Enumerates all possible combinations of variable values and the corresponding function value
- Truth tables for some arbitrary functions  
 $F_1(x,y,z)$ ,  $F_2(x,y,z)$ , and  $F_3(x,y,z)$  are shown to the below.

x	y	z	$F_1$	$F_2$	$F_3$
0	0	0	0	1	1
0	0	1	0	0	1

0	1	0	0	0	1
0	1	1	0	1	1
1	0	0	0	1	0
1	0	1	0	1	0
1	1	0	0	0	0
1	1	1	1	0	1

- Truth table: a unique representation of a Boolean function
- If two functions have identical truth tables, the functions are equivalent (and vice-versa).
- Truth tables can be used to prove equality theorems.
- However, the size of a truth table grows exponentially with the number of variables involved, hence unwieldy. This motivates the use of Boolean Algebra.

### Boolean expressions-NOT unique

Unlike truth tables, expressions representing a Boolean function are NOT unique.

- Example:
  - $F(x,y,z) = x' \cdot y' \cdot z' + x' \cdot y \cdot z' + x \cdot y \cdot z'$
  - $G(x,y,z) = x' \cdot y' \cdot z' + y \cdot z'$
- The corresponding truth tables for F() and G() are to the right. They are identical.
- Thus,  $F() = G()$

x	y	z	F	G
0	0	0	1	1
0	0	1	0	0
0	1	0	1	1
0	1	1	0	0
1	0	0	0	0
1	0	1	0	0
1	1	0	1	1
1	1	1	0	0

### Algebraic Manipulation (Minimization of Boolean function)

- Boolean algebra is a useful tool for simplifying digital circuits.
- Why do it? Simpler can mean cheaper, smaller, faster.
- Example: Simplify  $F = x'yz + x'yz' + xz$ .

$$\begin{aligned}
 F &= x'yz + x'yz' + xz \\
 &= x'y(z+z') + xz \\
 &= x'y \cdot 1 + xz
 \end{aligned}$$

$$= x'y + xz$$

- Example: Prove

$$x'y'z' + x'yz' + xyz' = x'z' + yz'$$

- **Proof:**

$$\begin{aligned} x'y'z' + x'yz' + xyz' \\ &= x'y'z' + x'yz' + x'yz' + xyz' \\ &= x'z'(y'+y) + yz'(x'+x) \\ &= x'z' \cdot 1 + yz' \cdot 1 \\ &= x'z' + yz' \end{aligned}$$

### Complement of a Function

- The complement of a function is derived by interchanging ( $\bullet$  and  $+$ ), and (1 and 0), and complementing each variable.
- Otherwise, interchange 1s to 0s in the truth table column showing F.
- The *complement* of a function IS NOT THE SAME as the *dual* of a function.

Example

- Find  $G(x,y,z)$ , the complement of  $F(x,y,z) = xy'z' + x'yz$

$$\begin{aligned} \text{Ans: } G = F' &= (xy'z' + x'yz)' \\ &= (xy'z')' \cdot (x'yz)' && \text{DeMorgan} \\ &= (x'+y+z) \cdot (x+y'+z') && \text{DeMorgan again} \end{aligned}$$

**Note:** The complement of a function can also be derived by finding the function's *dual*, and then complementing all of the literals

### Canonical and Standard Forms

We need to consider formal techniques for the simplification of Boolean functions.

Identical functions will have exactly the same canonical form.

- Minterms and Maxterms
- Sum-of-Minterms and Product-of- Maxterms
- Product and Sum terms
- Sum-of-Products (SOP) and Product-of-Sums (POS)

### Definitions

**Literal:** A variable or its complement

**Product term:** literals connected by  $\bullet$

**Sum term:** literals connected by  $+$

**Minterm:** a product term in which all the variables appear exactly once, either complemented or uncomplemented.

**Maxterm:** a sum term in which all the variables appear exactly once, either complemented or uncomplemented.

**Canonical form:** Boolean functions expressed as a sum of Minterms or product of Maxterms are said to be in canonical form.

### Minterm

- Represents exactly one combination in the truth table.
- Denoted by  $m_j$ , where  $j$  is the decimal equivalent of the minterm's corresponding binary combination ( $b_j$ ).
- A variable in  $m_j$  is complemented if its value in  $b_j$  is 0, otherwise is uncomplemented.

Example: Assume 3 variables (A, B, C), and  $j=3$ . Then,  $b_j = 011$  and its corresponding minterm is denoted by  $m_j = A'BC$

### Maxterm

- Represents exactly one combination in the truth table.
- Denoted by  $M_j$ , where  $j$  is the decimal equivalent of the maxterm's corresponding binary combination ( $b_j$ ).
- A variable in  $M_j$  is complemented if its value in  $b_j$  is 1, otherwise is uncomplemented.

Example: Assume 3 variables (A, B, C), and  $j=3$ . Then,  $b_j = 011$  and its corresponding maxterm is denoted by  $M_j = A+B'+C'$

### Truth Table notation for Minterms and Maxterms

- Minterms and Maxterms are easy to denote using a truth table.

Example: Assume 3 variables  $x,y,z$  (order is fixed)

x	y	z	Minterm	Maxterm
0	0	0	$x'y'z' = m_0$	$x+y+z = M_0$
0	0	1	$x'y'z = m_1$	$x+y+z' = M_1$
0	1	0	$x'yz' = m_2$	$x+y'+z = M_2$
0	1	1	$x'yz = m_3$	$x+y'+z' = M_3$
1	0	0	$xy'z' = m_4$	$x'+y+z = M_4$
1	0	1	$xy'z = m_5$	$x'+y+z' = M_5$
1	1	0	$xyz' = m_6$	$x'+y'+z = M_6$
1	1	1	$xyz = m_7$	$x'+y'+z' = M_7$

### Canonical Forms

- Every function  $F()$  has two canonical forms:
  - Canonical Sum-Of-Products (sum of minterms)
  - Canonical Product-Of-Sums (product of maxterms)

Canonical Sum-Of-Products:

The minterms included are those  $m_j$  such that  $F() = 1$  in row  $j$  of the truth table for  $F()$ .

Canonical Product-Of-Sums:

The maxterms included are those  $M_j$  such that  $F() = 0$  in row  $j$  of the truth table for  $F()$ .

### Example

Consider a Truth table for  $f_1(a,b,c)$  at right

The canonical sum-of-products form for  $f_1$  is

$$f_1(a,b,c) = m_1 + m_2 + m_4 + m_6$$

$$= a'b'c + a'bc' + ab'c' + abc'$$


The canonical product-of-sums form for  $f_1$  is

$$f_1(a,b,c) = M_0 \cdot M_3 \cdot M_5 \cdot M_7$$

$$= (a+b+c) \cdot (a+b'+c') \cdot (a'+b+c') \cdot (a'+b'+c')$$

- Observe that:  $m_j = M_j'$

a	b	c	$f_1$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

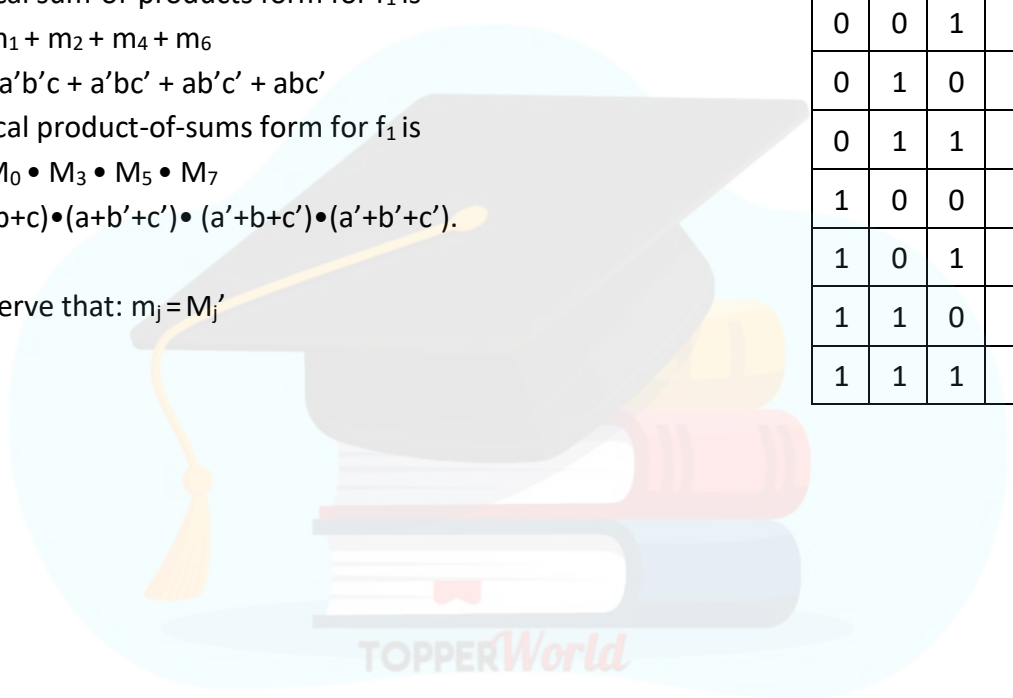

## Shorthand: $\Sigma$ and $\Pi$

- $f_1(a,b,c) = \Sigma m(1,2,4,6)$ , where  $\Sigma$  indicates that this is a sum-of-products form, and  $m(1,2,4,6)$  indicates that the minterms to be included are  $m_1$ ,  $m_2$ ,  $m_4$ , and  $m_6$ .
- $f_1(a,b,c) = \Pi M(0,3,5,7)$ , where  $\Pi$  indicates that this is a product-of-sums form, and  $M(0,3,5,7)$  indicates that the maxterms to be included are  $M_0$ ,  $M_3$ ,  $M_5$ , and  $M_7$ .
- Since  $m_j = M_j'$  for any  $j$ ,  
 $\Sigma m(1,2,4,6) = \Pi M(0,3,5,7) = f_1(a,b,c)$
- 

## Conversion between Canonical Forms

- Replace  $\Sigma$  with  $\Pi$  (or *vice versa*) and replace those  $j$ 's that appeared in the original form with those that do not.
  - Example:

$$\begin{aligned}f_1(a,b,c) &= a'b'c + a'bc' + ab'c' + abc' \\ &= m_1 + m_2 + m_4 + m_6 \\ &= \Sigma(1,2,4,6) \\ &= \Pi(0,3,5,7) \\ &= (a+b+c) \cdot (a+b'+c') \cdot (a'+b+c') \cdot (a'+b'+c')\end{aligned}$$

## Standard Forms

Another way to express Boolean functions is in standard form. In this configuration, the terms that form the function may contain one, two, or any number of literals.

There are two types of standard forms: the sum of products and products of sums.

The sum of products is a Boolean expression containing AND terms, called product terms, with one or more literals each. The sum denotes the ORing of these terms. An example of a function expressed as a sum of products is

$$F1 = y' + xy + x'yz'$$

The expression has three product terms, with one, two, and three literals. Their sum is, in effect, an OR operation.

A product of sums is a Boolean expression containing OR terms, called sum terms. Each term may have any number of literals. The product denotes the ANDing of these terms. An example of a function expressed as a product of sums is

$$F2 = x(y' + z)(x' + y + z')$$

This expression has three sum terms, with one, two, and three literals. The product is an AND operation.

## Conversion of SOP from standard to canonical form

### Example-1.

Express the Boolean function  $F = A + B'C$  as a sum of minterms.

Solution: The function has three variables: A, B, and C. The first term A is missing two variables; therefore,

$$A = A(B + B') = AB + AB'$$

This function is still missing one variable, so

$$\begin{aligned} A &= AB(C + C') + AB'(C + C') \\ &= ABC + ABC' + AB'C + AB'C' \end{aligned}$$

The second term  $B'C$  is missing one variable; hence,

$$B'C = B'C(A + A') = AB'C + A'B'C$$

Combining all terms, we have

$$\begin{aligned} F &= A + B'C \\ &= ABC + ABC' + AB'C + AB'C' + A'B'C \end{aligned}$$

But  $AB'C$  appears twice, and according to theorem  $(x + x = x)$ , it is possible to remove one of those occurrences. Rearranging the minterms in ascending order, we finally obtain

$$\begin{aligned} F &= A'B'C + AB'C + AB'C + ABC' + ABC \\ &= m_1 + m_4 + m_5 + m_6 + m_7 \end{aligned}$$

When a Boolean function is in its sum-of-minterms form, it is sometimes convenient to express the function in the following brief notation:

$$F(A, B, C) = \sum m(1, 4, 5, 6, 7)$$

### Example-2.

Express the Boolean function  $F = xy + x'z$  as a product of maxterms.

Solution: First, convert the function into OR terms by using the distributive law:

$$\begin{aligned} F &= xy + x'z = (xy + x')(xy + z) \\ &= (x + x')(y + x')(x + z)(y + z) \\ &= (x' + y)(x + z)(y + z) \end{aligned}$$

The function has three variables: x, y, and z. Each OR term is missing one variable; therefore,

$$\begin{aligned} x' + y &= x' + y + zz' = (x' + y + z)(x' + y + z') \\ x + z &= x + z + yy' = (x + y + z)(x + y' + z) \\ y + z &= y + z + xx' = (x + y + z)(x' + y + z) \end{aligned}$$

Combining all the terms and removing those which appear more than once, we finally obtain

$$\begin{aligned} F &= (x + y + z)(x + y' + z)(x' + y + z)(x' + y + z) \\ F &= M_0M_2M_4M_5 \end{aligned}$$

A convenient way to express this function is as

$$\text{follows: } F(x, y, z) = \pi M(0, 2, 4, 5)$$

The product symbol,  $\pi$ , denotes the ANDing of maxterms; the numbers are the indices of the maxterms of the function.



## Unit-II

### Minimization Techniques

#### Two-variable k-map:

A two-variable k-map can have  $2^2=4$  possible combinations of the input variables A and B. Each of these combinations,  $\bar{A}\bar{B}$ ,  $\bar{A}B$ ,  $A\bar{B}$ ,  $AB$  (in the SOP form) is called a minterm. The minterm may be represented in terms of their decimal designations –  $m_0$  for  $\bar{A}\bar{B}$ ,  $m_1$  for  $\bar{A}B$ ,  $m_2$  for  $A\bar{B}$  and  $m_3$  for  $AB$ , assuming that A represents the MSB. The letter m stands for minterm and the subscript represents the decimal designation of the minterm. The presence or absence of a minterm in the expression indicates that the output of the logic circuit assumes logic 1 or logic 0 level for that combination of input variables.

The expression  $f = \bar{A}\bar{B} + A\bar{B} + AB$ , it can be expressed using min

$$\text{term as } F = m_0 + m_2 + m_3 = \sum m(0, 2, 3)$$

Using Truth Table:

Minterm	Inputs		Output F
	A	B	
0	0	0	1
1	0	1	0
2	1	0	1
3	1	1	1

A 1 in the output contains that particular minterm in its sum and a 0 in that column indicates that the particular minterm does not appear in the expression for output. This information can also be indicated by a two-variable k-map.

#### Mapping of SOP Expressions:

A two-variable k-map has  $2^2=4$  squares. These squares are called cells. Each square on the k-map represents a unique minterm. The minterm designation of the squares are placed in any square, indicates that the corresponding minterm does output expressions. And a 0 or no entry in any square indicates that the corresponding minterm does not appear in the expression for output.

	<b>B</b>	<b>0</b>	<b>1</b>
<b>A</b>	<b>0</b>	<b>A'B'</b>	<b>A'B</b>
<b>1</b>		<b>AB'</b>	<b>AB</b>

The minterms of a two-variable k-map

The mapping of the expressions  $=\sum m(0,2,3)$  is

	<b>B</b>	<b>0</b>	<b>1</b>
<b>A</b>	<b>0</b>	<b>1</b> <sup>0</sup>	<b>0</b> <sup>1</sup>
<b>1</b>	<b>1</b> <sup>2</sup>	<b>1</b> <sup>3</sup>	

k-map of  $\sum m(0,2,3)$

**EX:** Map the expressions  $f = B + A$

$F = m_1 + m_2 = \sum m(1,2)$  The k-map is

	<b>B</b>	<b>0</b>	<b>1</b>
<b>A</b>	<b>0</b>	<b>0</b> <sup>0</sup>	<b>1</b> <sup>1</sup>
<b>1</b>	<b>1</b> <sup>2</sup>	<b>0</b> <sup>3</sup>	

### Minimizations of SOP expressions:

To minimize Boolean expressions given in the SOP form by using the k-map, look for adjacent adjacent squares having 1's minterms adjacent to each other, and combine them to form larger squares to eliminate some variables. Two squares are said to be adjacent to each other, if their minterms differ in only one variable. (i.e., B & A differ only in one variable. so they may be combined to form a 2-square to eliminate the variable B. similarly all other.

The necessary condition for adjacency of minterms is that their decimal designations must differ by a power of 2. A minterm can be combined with any number of minterms adjacent to it to form larger squares. Two minterms which are adjacent to each other can be combined to form a bigger square called a 2-square or a pair. This eliminates one variable – the variable that is not common to both the minterms. For EX:

$m_0$  and  $m_1$  can be combined to yield,

$$f_1 = m_0 + m_1 = \bar{A}B + A\bar{B} = (B + \bar{A})\bar{A} + (A + \bar{B})\bar{A} = \bar{A}(B + A) = \bar{A}$$

$m_0$  and  $m_2$  can be combined to yield,

$$f_2 = m_0 + m_2 = \bar{A}\bar{B} + A\bar{B} = (\bar{A} + A)\bar{B} = \bar{B}$$

$m_1$  and  $m_3$  can be combined to yield,


$$f_3 = m_1 + m_3 = B + AB = B(1 + A) = B$$

$m_2$  and  $m_3$  can be combined to yield,

$$f_4 = m_2 + m_3 = A + AB = A(B + 1) = A$$

$m_0, m_1, m_2$  and  $m_3$  can be combined to yield,

 
$$\begin{aligned} &= m_0 + m_1 + m_2 + m_3 \\ &= (B + 1) + A(B + 1) \\ &= 1 + A \\ &= 1 \end{aligned}$$



The possible minterm groupings in a two-variable k-map.

Two 2-squares adjacent to each other can be combined to form a 4-square. A 4-square eliminates 2 variables. A 4-square is called a quad. To read the squares on the map after minimization, consider only those variables which remain constant through the square, and ignore the variables which are varying. Write the non complemented variable if the variable is remaining constant as a 1, and the complemented variable if the variable is remaining constant as a 0, and write the variables as a product term. In the above figure  $f_1$  read as  $A'$ , because, along the square, A remains constant as a 0, that is, as  $A'$ , where as B is changing from 0 to 1.

**EX:** Reduce the minterm  $f = A' + AB$  using mapping. Expressed in terms of minterms, the given expression is  $F = m_0 + m_1 + m_2 + m_3 = m \sum(0,1,3)$  & the figure shows the k-map for  $f$  and its reduction. In one 2-square, A is constant as a 0 but B varies from a 0 to a 1, and in the other 2-square, B is constant as a 1 but A varies from a 0 to a 1. So, the reduced expressions is  $A' + B$ .

 

It requires two gate inputs for realization as

$$f = A' + B \quad (\text{k-map in SOP form, and logic diagram.})$$

The main criterion in the design of a digital circuit is that its cost should be as low as possible. For that the expression used to realize that circuit must be minimal. Since the cost is proportional to number of gate inputs in the circuit, an expression is considered minimal only if it corresponds to the least possible number of gate inputs. & there is no guarantee for that k-map in SOP is the real minimal. To obtain real minimal expression, obtain the minimal expression both in SOP & POS form by using k-maps and take the minimal of these two minimal.

The 1's on the k-map indicate the presence of minterms in the output expressions, where as the 0s indicate the absence of minterms. Since the absence of a minterm in the SOP expression means the presence of the corresponding maxterm in the POS expression of the same. when a SOP expression is plotted on the k-map, 0s or no entries on the k-map represent the maxterms. To obtain the minimal expression in the POS form, consider the 0s on the k-map and follow the procedure used for combining 1s. Also, since the absence of a maxterm in the POS expression means the presence of the corresponding minterm in the SOP expression of the same, when a POS expression is plotted on the k-map, 1s or no entries on the k-map represent the minterms.


### Mapping of POS expressions:

Each sum term in the standard POS expression is called a maxterm. A function in two variables (A, B) has four possible maxterms,  $A+B$ ,  $A+\bar{B}$ ,  $A+\bar{B}$ ,  $A+B$

. They are represented as  $M_0$ ,  $M_1$ ,  $M_2$ , and  $M_3$  respectively. The uppercase letter M stands for maxterm and its subscript denotes the decimal designation of that maxterm obtained by treating the non-complemented variable as a 0 and the complemented variable as a 1 and putting them side by side for reading the decimal equivalent of the binary number so formed.

For mapping a POS expression on to the k-map, 0s are placed in the squares corresponding to the maxterms which are presented in the expression and 1s are placed in the squares corresponding to the maxterm which are not present in the expression. The decimal designation of the squares of the squares for maxterms is the same as that for the minterms. A two-variable k-map & the associated maxterms are as the maxterms of a two-variable k-map

 The possible maxterm groupings in a two-variable k-map



### Minimization of POS Expressions:


To obtain the minimal expression in POS form, map the given POS expression on to the K-map and combine the adjacent 0s into as large squares as possible. Read the squares putting the complemented variable if its value remains constant as a 1 and the non-complemented variable if its value remains constant as a 0 along the entire square ( ignoring the variables which do not remain constant throughout the square) and then write them as a sum term.

Various maxterm combinations and the corresponding reduced expressions are shown in figure. In this  $f_1$  read as  $A$  because  $A$  remains constant as a 0 throughout the square and  $B$  changes from a 0 to a 1.  $f_2$  is read as  $B'$  because  $B$  remains constant along the square as a 1 and  $A$  changes from a 0 to a 1.  $f_3$  is read as  $A'B$  because both the variables are changing along the square.

Is read as a 0 because both the variables are changing along the square.

**Ex:** Reduce the expression  $f=(A+B)(A+B')(A'+B')$  using mapping.

 The given expression in terms of maxterms is  $f=\pi M(0,1,3)$ . It requires two gates inputs for realization of the reduced expression as



In this given expression, the maxterm  $M_2$  is absent. This is indicated by a 1 on the k-map. The corresponding SOP expression is  $\sum m_2$  or  $AB'$ . This realization is the same as that for the POS form.

### Three-variable K-map:

A function in three variables ( $A, B, C$ ) expressed in the standard SOP form can have eight possible combinations:  $A B C, A B C', A B C, A B C', A B C, A B C, A B C, A B C$ . Each one of these combinations designate d by  $m_0, m_1, m_2, m_3, m_4, m_5, m_6$ , and  $m_7$ , respectively, is called a minterm.  $A$  is the MSB of the minterm designator and  $C$  is the LSB.

In the standard POS form, the eight possible combinations are:  $A+B+C, A+B+C, A+B+C, A+B+C, A+B+C, A+B+C, A+B+C, A+B+C$ . Each one of these combinations designated by  $M_0, M_1, M_2, M_3, M_4, M_5, M_6$ , and  $M_7$  respectively is called a maxterm.  $A$  is the MSB of the maxterm designator and  $C$  is the LSB.

A three-variable k-map has, therefore,  $8(=2^3)$  squares or cells, and each square on the map represents a minterm or maxterm as shown in figure. The small number on the top right corner of each cell indicates the minterm or maxterm designation.

	BC	00	01	11	10
A	0	$\bar{A}\bar{B}\bar{C}$ <sup>0</sup>	$\bar{A}\bar{B}C$ <sup>1</sup>	$\bar{A}B\bar{C}$ <sup>3</sup>	$\bar{A}BC$ <sup>2</sup>
	1	$A\bar{B}\bar{C}$ <sup>4</sup>	$A\bar{B}C$ <sup>5</sup>	$AB\bar{C}$ <sup>7</sup>	$ABC$ <sup>6</sup>

(a) Minterms

	BC	00	01	11	10
A	0	$A+B+C$ <sup>0</sup>	$A+B+\bar{C}$ <sup>1</sup>	$A+\bar{B}+\bar{C}$ <sup>3</sup>	$A+\bar{B}+C$ <sup>2</sup>
	1	$\bar{A}+B+C$ <sup>4</sup>	$\bar{A}+B+\bar{C}$ <sup>5</sup>	$\bar{A}+\bar{B}+\bar{C}$ <sup>7</sup>	$\bar{A}+\bar{B}+C$ <sup>6</sup>

(b) Maxterms

The three-variable k-map.

The binary numbers along the top of the map indicate the condition of B and C for each column. The binary number along the left side of the map against each row indicates the condition of A for that row. For example, the binary number 01 on top of the second column in fig indicates that the variable B appears in complemented form and the variable C in non-complemented form in all the minterms in that column. The binary number 0 on the left of the first row indicates that the variable A appears in complemented form in all the minterms in that row, the binary numbers along the top of the k-map are not in normal binary order. They are, in fact, in the Gray code. This is to ensure that two physically adjacent squares are really adjacent, i.e., their minterms or maxterms differ by only one variable.

Ex: Map the expression  $f = C + \dots + \dots + ABC$

In the given expression, the minterms are :  $C=001=m_1$  ;  $=101=m_5$ ;  
 $=010=m_2$ ;  
 $=110=m_6$ ;  $ABC=111=m_7$ .

So the expression is  $f = \sum m(1,5,2,6,7) = \sum m(1,2,5,6,7)$ . The corresponding k-map is

	BC	00	01	11	10
A	0	0 <sup>0</sup>	1 <sup>1</sup>	0 <sup>3</sup>	1 <sup>2</sup>
	1	0 <sup>4</sup>	1 <sup>5</sup>	1 <sup>7</sup>	1 <sup>6</sup>

K-map in SOP form

Ex: Map the expression  $f = (A+B+C)(\dots)(\dots)(A+\dots)(\dots)$

In the given expression the maxterms are  
 $:A+B+C=000=M_0$ ;  $\dots = 101=M_5$ ;  $\dots = 111=M_7$ ;  $A+\dots = 011=M_3$ ;  $\dots$   
 $=110=M_6$ .

So the expression is  $f = \pi M(0,5,7,3,6) = \pi M(0,3,5,6,7)$ . The mapping of the expression is

	BC			
A	00	01	11	10
0	0 <sup>0</sup>	1 <sup>1</sup>	0 <sup>3</sup>	1 <sup>2</sup>
1	1 <sup>4</sup>	0 <sup>5</sup>	0 <sup>7</sup>	0 <sup>6</sup>

K-map in POS form.

### Minimization of SOP and POS expressions:

For reducing the Boolean expressions in SOP (POS) form plotted on the k-map, look at the 1s (0s) present on the map. These represent the minterms (maxterms). Look for the minterms (maxterms) adjacent to each other, in order to combine them into larger squares. Combining of adjacent squares in a k-map containing 1s (or 0s) for the purpose of simplification of a SOP (or POS) expression is called *looping*. Some of the minterms (maxterms) may have many adjacencies. Always start with the minterms (maxterm) with the least number of adjacencies and try to form as large as large a square as possible. The larger must form a geometric square or rectangle. They can be formed even by wrapping around, but cannot be formed by using diagonal configurations. Next consider the minterm (maxterm) with next to the least number of adjacencies and form as large a square as possible. Continue this till all the minterms (maxterms) are taken care of . A minterm (maxterm) can be part of any number of squares if it is helpful in reduction. Read the minimal expression from the k-map, corresponding to the squares formed. There can be more than one minimal expression.

Two squares are said to be adjacent to each other (since the binary designations along the top of the map and those along the left side of the map are in Gray code), if they are physically adjacent to each other, or can be made adjacent to each other by wrapping around. For squares to be combinable into bigger squares it is essential but not sufficient that their minterm designations must differ by a power of two.

General procedure to simplify the Boolean expressions:


1. Plot the k-map and place 1s(0s) corresponding to the minterms (maxterms) of the SOP (POS) expression.
2. Check the k-map for 1s(0s) which are not adjacent to any other 1(0). They are isolated minterms(maxterms) . They are to be read as they are because they cannot be combined even into a 2-square.
3. Check for those 1s(0s) which are adjacent to only one other 1(0) and make them pairs (2 squares).
4. Check for quads (4 squares) and octets (8 squares) of adjacent 1s (0s) even if they contain some 1s(0s) which have already been combined. They must geometrically form a square or a rectangle.
5. Check for any 1s(0s) that have not been combined yet and combine them into bigger squares if possible.
6. Form the minimal expression by summing (multiplying) the product the product (sum) terms of all the groups.

### Reading the K-maps:

While reading the reduced k-map in SOP (POS) form, the variable which remains constant as 0 along the square is written as the complemented (non-complemented) variable and the one which remains constant as 1 along the square is written as non-complemented (complemented) variable and the term as a product (sum) term. All the product (sum) terms are added (multiplied).

Some possible combinations of minterms and the corresponding minimal expressions read from the k-maps are shown in fig: Here  $f_6$  is read as 1, because along the 8-square no variable remains constant.  $f_5$  is read as  $\bar{A}$ , because, along the 4-square formed by  $m_0, m_1, m_2$  and  $m_3$ , the variables B and C are changing, and A remains constant as a 0. Algebraically,
 
$$\begin{aligned} f_5 &= m_0 + m_1 + m_2 + m_3 \\ &= \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + \bar{A}BC + \bar{A}B\bar{C} \\ &= \bar{A}(\bar{B}\bar{C} + B\bar{C} + BC + B\bar{C}) \\ &= \bar{A}(\bar{B} + B)(\bar{C} + C) \\ &= \bar{A}(1)(1) \\ &= \bar{A} \end{aligned}$$




$f_3$  is read as  $\bar{C} + \bar{B}$ , because in the 4-square formed by  $m_0, m_2, m_6$ , and  $m_4$ , the variable A and B are changing, whereas the variable C remains constant as a 0. So it is read as  $\bar{C}$ . In the 4-square formed by  $m_0, m_1, m_4, m_5$ , A and C are changing but B remains constant as a 0. So it is read as  $\bar{B}$ . So, the resultant expression for  $f_3$  is the sum of these two, i.e.,  $\bar{C} + \bar{B}$ .

$f_1$  is read as  $\bar{B}\bar{C} + \bar{A}\bar{B}\bar{C}$ , because in the 2-square formed by  $m_0$  and  $m_4$ , A is changing from a 0 to a 1. Whereas B and C remain constant as a 0. So it is read as  $\bar{B}\bar{C}$ . In the 2-square formed by  $m_0$  and  $m_1$ , C is changing from a 0 to a 1, whereas A and B remain constant as a 0. So it is read as  $\bar{A}\bar{B}\bar{C}$ . In the 2-square formed by  $m_0$  and  $m_2$ , B is changing from a 0 to a 1 whereas A and C remain constant as a 0. So, it is read as  $\bar{A}\bar{C}$ . Therefore, the resultant SOP expression is

$$\bar{B}\bar{C} + \bar{A}\bar{B}\bar{C} + \bar{A}\bar{C}$$

 Some possible maxterm groupings and the corresponding minimal POS expressions read from the k-map are






In this figure, along the 4-square formed by  $M_1, M_3, M_7, M_5$ , A and B are changing from a 0 to a 1, where as C remains constant as a 1. SO it is read as  $\bar{C}$ . Along the 4-squad formed by  $M_3, M_2, M_7$ , and  $M_6$ , variables A and C are changing from a 0 to a 1. But B remains constant as a 1. So it is read as  $\bar{B}$ . The minimal expression is the product of these two terms, i.e.,  $f_1 = (\bar{C})(\bar{B})$ . also in this figure, along the 2-square formed by  $M_4$  and  $M_6$ , variable B is changing from a 0 to a 1, while variable A remains constant as a 1 and variable C remains constant as a 0. SO, read it as  $A\bar{C}$ . Similarly, the 2-square formed by  $M_7$  and  $M_6$  is read as  $A\bar{B}$ , while the 2-square formed by  $M_2$  and  $M_6$  is read as  $\bar{A}C$ . The minimal expression is the product of these sum terms, i.e,  $f_2 = (A\bar{C} + A\bar{B} + \bar{A}C)$

**Ex:** Reduce the expression  $f = \sum m(0,2,3,4,5,6)$  using mapping and implement it in AOI logic as well as in NAND logic. The Sop k-map and its reduction, and the implementation of the minimal expression using AOI logic and the corresponding NAND logic are shown in figures below

In SOP k-map, the reduction is done as:

- $m_5$  has only one adjacency  $m_4$ , so combine  $m_5$  and  $m_4$  into a square. Along this 2-square A remains constant as 1 and B remains constant as 0 but C varies from 0 to 1. So read it as  $A\bar{B}$ .
- $m_3$  has only one adjacency  $m_2$ , so combine  $m_3$  and  $m_2$  into a square. Along this 2-square A remains constant as 0 and B remains constant as 1 but C varies from 1 to 0. So read it as  $\bar{A}B$ .
- $m_6$  can form a 2-square with  $m_2$  and  $m_4$  can form a 2-square with  $m_0$ , but observe that by wrapping the map from left to right  $m_0, m_4, m_2, m_6$  can form a 4-square. Out of these  $m_2$  and  $m_4$  have already been combined but they can be utilized again. So make it. Along this 4-square, A is changing from 0 to 1 and B is also changing from 0 to 1 but C is remaining constant as 0. so read it as  $\bar{C}$ .
- Write all the product terms in SOP form. So the minimal SOP expression is

 

### Four variable k-maps:

Four variable k-map expressions can have  $2^4=16$  possible combinations of input variables such as  $\bar{A}\bar{B}\bar{C}\bar{D}$ ,  $\bar{A}\bar{B}\bar{C}D$ ,  $\bar{A}\bar{B}C\bar{D}$ ,  $\bar{A}\bar{B}CD$  with minterm designations  $m_0, m_1, \dots, m_{15}$  respectively in SOP form &  $A+B+C+D, A+B+C+\bar{D}, \dots, \bar{A}+\bar{B}+\bar{C}+\bar{D}$  with maxterms  $M_0, M_1, \dots, M_{15}$  respectively in POS form. It has  $2^4=16$  squares or cells. The binary number designations of rows & columns are in the gray code. Here follows 01 & 10 follows 11 called Adjacency ordering.

CD	00	01	11	10
AB	00	01	11	10
00	0 $\bar{A}\bar{B}\bar{C}\bar{D}$	1 $\bar{A}\bar{B}\bar{C}D$	3 $\bar{A}\bar{B}C\bar{D}$	2 $\bar{A}\bar{B}CD$
01	4 $\bar{A}B\bar{C}\bar{D}$	5 $\bar{A}B\bar{C}D$	7 $\bar{A}BC\bar{D}$	6 $\bar{A}BCD$
11	12 $A\bar{B}\bar{C}\bar{D}$	13 $A\bar{B}\bar{C}D$	15 $A\bar{B}C\bar{D}$	14 $A\bar{B}CD$
10	8 $AB\bar{C}\bar{D}$	9 $AB\bar{C}D$	11 $ABC\bar{D}$	10 $ABCD$


SOP form

CD	00	01	11	10
AB	00	01	11	10
00	0 $A+B+C+D$	1 $A+B+C+\bar{D}$	3 $A+B+\bar{C}+\bar{D}$	2 $A+B+\bar{C}+D$
01	4 $A+\bar{B}+C+D$	5 $A+\bar{B}+C+\bar{D}$	7 $A+\bar{B}+\bar{C}+\bar{D}$	6 $A+\bar{B}+\bar{C}+D$
11	12 $\bar{A}+\bar{B}+C+D$	13 $\bar{A}+\bar{B}+C+\bar{D}$	15 $\bar{A}+\bar{B}+\bar{C}+\bar{D}$	14 $\bar{A}+\bar{B}+\bar{C}+D$
10	8 $\bar{A}+B+C+D$	9 $\bar{A}+B+C+\bar{D}$	11 $\bar{A}+B+\bar{C}+\bar{D}$	10 $\bar{A}+B+\bar{C}+D$

POS form

EX: Reduce using mapping the expression  $\Sigma m(2, 3, 6, 7, 8, 10, 11, 13, 14)$ .

Start with the minterm with the least number of adjacencies. The minterm  $m_{13}$  has no adjacency. Keep it as it is. The  $m_8$  has only one adjacency,  $m_{10}$ . Expand  $m_8$  into a 2-square with  $m_{10}$ . The  $m_7$  has two adjacencies,  $m_6$  and  $m_3$ . Hence  $m_7$  can be expanded into a 4-square with  $m_6, m_3$  and  $m_2$ . Observe that,  $m_7, m_6, m_2$ , and  $m_3$  form a geometric square. The  $m_{11}$  has 2 adjacencies,  $m_{10}$  and  $m_3$ . Observe that,  $m_{11}, m_{10}, m_3$ , and  $m_2$  form a geometric square on wrapping the K-map. So expand  $m_{11}$  into a 4-square with  $m_{10}, m_3$  and  $m_2$ . Note that,  $m_2$  and  $m_3$ , have already become a part of the 4-square  $m_7, m_6, m_2$ , and  $m_3$ . But if  $m_{11}$  is expanded only into a 2-square with  $m_{10}$ , only one variable is eliminated. So  $m_2$  and  $m_3$  are used again to make another 4-square with  $m_{11}$  and  $m_{10}$  to eliminate two variables. Now only  $m_6$  and  $m_{14}$  are left uncovered. They can form a 2-square that eliminates only one variable. Don't do that. See whether they can be expanded into a larger square. Observe that,  $m_2, m_6, m_{14}$ , and  $m_{10}$  form a rectangle. So  $m_6$  and  $m_{14}$  can be expanded into a 4-square with  $m_2$  and  $m_{10}$ . This eliminates two variables.

 

**Five variable k-map:**

Five variable k-map can have  $2^5 = 32$  possible combinations of input variable as  $0, 1, \dots, E, \dots, ABCDE$  with minterms  $m_0, m_1, \dots, m_{31}$  respectively in SOP &  $A+B+C+D+E, A+B+C+\dots + + + +$  with maxterms  $M_0, M_1, \dots, M_{31}$  respectively in POS form. It has  $2^5 = 32$  squares or cells of the k-map are divided into 2 blocks of 16 squares each. The left block represents minterms from  $m_0$  to  $m_{15}$  in which A is a 0, and the right block represents minterms from  $m_{16}$  to  $m_{31}$  in which A is 1. The 5-variable k-map may contain 2-squares, 4-squares, 8-squares, 16-squares or 32-squares involving these two blocks. Squares are also considered adjacent in these two blocks, if when superimposing one block on top of another, the squares coincide with one another.

Some possible 2-squares in a five-variable map are  $m_0, m_{16}; m_2, m_{18}; m_5, m_{21}; m_{15}, m_{31}; m_{11}, m_{27}$ .

Some possible 4-squares are  $m_0, m_2, m_{16}, m_{18}; m_0, m_1, m_{16}, m_{17}; m_0, m_4, m_{16}, m_{20}; m_{13}, m_{15}, m_{29}, m_{31}; m_5, m_{13}, m_{21}, m_{29}$ .


Some possible 8-squares are  $m_0, m_1, m_3, m_2, m_{16}, m_{17}, m_{19}, m_{18}; m_0, m_4, m_{12}, m_8, m_{16}, m_{20}, m_{28}, m_{24}; m_5, m_7, m_{13}, m_{15}, m_{21}, m_{23}, m_{29}, m_{31}$ .

The squares are read by dropping out the variables which change. Some possible

Grouping is

 - (a)  $m_0, m_{16} = \overline{B}\overline{C}\overline{D}\overline{E}$
- (b)  $m_2, m_{18} = \overline{B}\overline{C}\overline{D}E$
- (c)  $m_4, m_6, m_{20}, m_{22} = \overline{B}\overline{C}E$
- (d)  $m_5, m_7, m_{13}, m_{15}, m_{21}, m_{23}, m_{29}, m_{31} = CE$
- (e)  $m_8, m_9, m_{10}, m_{11}, m_{24}, m_{25}, m_{26}, m_{27} = \overline{B}\overline{C}$

- $M_0, M_{16} = B + C + D + E$
- $M_2, M_{18} = B + C + \overline{D} + E$
- $M_4, M_6, M_{20}, M_{22} = B + \overline{C} + E$
- $M_5, M_7, M_{13}, M_{15}, M_{21}, M_{23}, M_{29}, M_{31} = \overline{C} + \overline{E}$
- $M_8, M_9, M_{10}, M_{11}, M_{24}, M_{25}, M_{26}, M_{27} = \overline{B} + C$



Ex:  $F = \sum m(0,1,4,5,6,13,14,15,22,24,25,28,29,30,31)$  is SOP

POS is  $F = \pi M(2,3,7,8,9,10,11,12,16,17,18,19,20,21,23,26,27)$


The real minimal expression is the minimal of the SOP and POS forms.

The reduction is done as

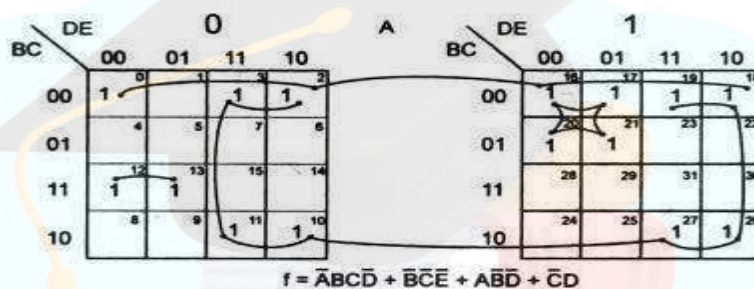1. There is no isolated 1s
2.  $M_{12}$  can go only with  $m_{13}$ . Form a 2-square which is read as  $A'BCD'$
3.  $M_0$  can go with  $m_2, m_{16}$  and  $m_{18}$ . so form a 4-square which is read as  $B'C'E'$
4.  $M_{20}, m_{21}, m_{17}$  and  $m_{16}$  form a 4-square which is read as  $AB'D'$
5.  $M_2, m_3, m_{18}, m_{19}, m_{10}, m_{11}, m_{26}$  and  $m_{27}$  form an 8-square which is read as  $C'd$
6. Write all the product terms in SOP form.

So the minimal expression is


$$F_{\min} = A'BCD' + B'C'E' + AB'D' + C'd \text{ (16 inputs)}$$



In the POS k-map ,the reduction is done as:

 
1. There are no isolated 0s
2.  $M_1$  can go only with  $M_5$ . So, make a 2-square, which is read as  $(A + B + D + \bar{E})$ .
3.  $M_4$  can go with  $M_5, M_7,$  and  $M_6$  to form a 4-square, which is read as  $(A + B + \bar{C})$ .
4.  $M_8$
5.  $M_{28}$
6.  $M_{30}$
7. Sum terms in POS form. So the minimal expression in POS is

$$F_{\min} = A'BcD' + B'C'E' + AB'D' + C'D$$



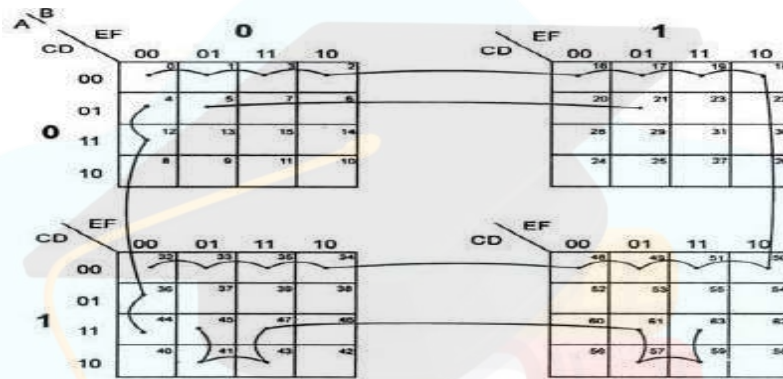**Six variable k-map:**

Six variable k-map can have  $2^6 = 64$  combinations as  $---ABCDEF$  with minterms  $m_0, m_1, \dots, m_{63}$  respectively in SOP &  $(A+B+C+D+E+F), \dots, ( + + + + + )$  with maxterms  $M_0, M_1, \dots, M_{63}$  respectively in POS form. It has  $2^6 = 64$  squares or cells of the k-map are divided into 4 blocks of 16 squares each.



Some possible groupings in a six variable k-map

**Don't care combinations:** For certain input combinations, the value of the output is unspecified either because the input combinations are invalid or because the precise value of the output is of no consequence. The combinations for which the value of experiments are not specified are called don't care combinations are invalid or because the precise value of the output is of no consequence. The combinations for which the value of expressions is not specified are called don't care combinations or Optional Combinations, such expressions stand incompletely specified. The output is a don't care for these invalid combinations.

Ex: In XS-3 code system, the binary states 0000, 0001, 0010, 1101, 1110, 1111 are unspecified. & never occur called don't cares.

A standard SOP expression with don't cares can be converted into a standard POS form by keeping the don't cares as they are & writing the missing minterms of the SOP form as the maxterms of the POS form viceversa.

Don't cares denoted by  $\_ \downarrow \_$  or  $\_ \phi \_$


Ex:  $f = \sum m(1,5,6,12,13,14) + d(2,4)$

Or  $f = \pi M(0,3,7,9,10,11,15) + d(2,4)$

SOP minimal form  $f_{min} = \dots + B + \dots$

POS minimal form  $f_{min} = (B+D)(\dots + B)(\dots + D)$

 $= \dots + \dots + \dots + \dots + (\dots + \dots)$




**Prime implicants, Essential Prime implicants, Redundant prime implicants:**

Each square or rectangle made up of the bunch of adjacent minterms is called a subcube. Each of these subcubes is called a Prime implicant (PI). The PI which contains at least one minterm which cannot be covered by any other prime implicants is called as Essential Prime implicant (EPI). The PI whose each 1 is covered at least by one EPI is called a Redundant Prime implicant (RPI). A PI which is neither an EPI nor a RPI is called a Selective Prime implicant (SPI).

The function has unique MSP comprising EPI is


$F(A,B,C,D) = CD + ABC + A\bar{D} + \bar{B}$

 The RPI  $\bar{B}D$  may be included without changing the function but the resulting expression would not be in minimal SOP(MSP) form.



Essential and Redundant Prime Implicants

 $F(A,B,C,D)=\sum m(0,4,5,10,11,13,15)$  SPI are marked by dotted squares, shows MSP form of a function need not be unique.



Essential and Selective Prime Implicants

Here, the MSP form is obtained by including two EPI's & selecting a set of SPI's to cover remaining uncovered minterms 5,13,15. & these can be covered as

- (A) (4,5) & (13,15) -----  $B + ABD$
- (B) (5,13) & (13,15) -----  $B D + ABD$
- (C) (5,13) & (15,11) -----  $B D + ACD$

$$F(A,B,C,D) = +A C \text{ ----- EPI's } + B + ABD$$

$$(OR) \quad F(A,B,C,D) = +A C \text{ ----- EPI's } + B D + ABD$$

$$(OR) \quad F(A,B,C,D) = +A C \text{ ----- EPI's } + B D + ACD$$


**False PI's Essential False PI's, Redundant False PI's & Selective False PI's:**

The maxterms are called false minterms. The PI's is obtained by using the maxterms are called False PI's (FPI). The FPI which contains at least one  $\_0'$  which can't be covered by only other FPI is called an Essential False Prime implicant (ESPI)

$$F(A,B,C,D) = \sum m(0,1,2,3,4,8,12) \\ = \pi M(5,6,7,9,10,11,13,14,15)$$


$$F_{min} = (+)(+)(+)(+)$$

 All the FPI, EFPI's as each of them contain atleast one  $\_0'$  which can't be covered by any other FPI



Essential False Prime implicants

 Consider Function  $F(A,B,C,D) = \pi M(0,1,2,6,8,10,11,12)$



Essential and Redundant False Prime Implicants

### Mapping when the function is not expressed in minterms (maxterms):

An expression in k-map must be available as a sum (product) of minterms (maxterms). However if not so expressed, it is not necessary to expand the expression algebraically into its minterms (maxterms). Instead, expansion into minterms (maxterms) can be accomplished in the process of entering the terms of the expression on the k-map.

### Limitations of Karnaugh maps:

- Convenient as long as the number of variables does not exceed six.
- Manual technique, simplification process is heavily dependent on the human abilities.

### Quine-Mccluskey Method:

It also known as *Tabular method*. It is more systematic method of minimizing expressions of even larger number of variables. It is suitable for hand computation as well as computation by machines i.e., programmable. . The procedure is based on repeated application of the combining theorem.

$PA+P = P$  (P is set of literals) on all adjacent pairs of terms, yields the set of all PI's from which a minimal sum may be selected.

Consider expression

$$\sum m(0,1,4,5) = + C + A + A C$$



First, second terms & third, fourth terms can be combined

$$(+) + (C+) = +A$$

Reduced to

$$( + ) =$$

The same result can be obtained by combining  $m_0$  &  $m_4$  &  $m_1$  &  $m_5$  in first step & resulting terms in the second step .

Procedure:

- Decimal Representation
- Don't cares
- PI chart
- EPI
- Dominating Rows & Columns
- Determination of Minimal expressions in complex cases.

Branching Method:

**EXAMPLE 3.29** Obtain the set of prime implicants for the Boolean expression  $f = \Sigma m(0, 1, 6, 7, 8, 9, 13, 14, 15)$  using the tabular method.

**Solution**

Group the minterms in terms of the number of 1s present in them and write their binary designations. The procedure to obtain the prime implicants is shown in Table 3.3.

Table 3.3 Example 3.29

	Column 1		Column 2		Column 3
	Minterm	Binary designation	A	B C D	A B C D
Index 0	0	0000 ✓	0, 1 (1)	0 0 0 - ✓	0, 1, 8, 9 (1, 8) - 0 0 - Q
Index 1	1	0001 ✓	0, 8 (8)	- 0 0 0 ✓	...
	8	1000 ✓	1, 9 (8)	- 0 0 1 ✓	...
Index 2	6	0110 ✓	8, 9 (1)	1 0 0 - ✓	6, 7, 14, 15 (1, 8) - 1 1 - P
	9	1001 ✓	6, 7 (1)	0 1 1 - ✓	
Index 3	7	0111 ✓	6, 14 (8)	- 1 1 0 ✓	
	13	1101 ✓	9, 13 (4)	1 - 0 1 S	
	14	1110 ✓	7, 15 (8)	- 1 1 1 ✓	
Index 4	15	1111 ✓	13, 15 (2)	1 1 - 1 R	
			14, 15 (1)	1 1 1 - ✓	

Comparing the terms of index 0 with the terms of index 1 of column 1,  $m_0(0000)$  is combined with  $m_1(0001)$  to yield 0, 1 (1), i.e. 000-. This is recorded in column 2 and 0000 and 0001 are checked off in column 1.  $m_0(0000)$  is combined with  $m_8(1000)$  to yield 0, 8 (8), i.e. -000. This is recorded in column 2 and 1000 is checked off in column 1. Note that 0000 of column 1 has already been checked off. No more combinations of terms of index 0 and index 1 are possible. So, draw a line below the last combination of these groups, i.e. below 0, 8 (8), -000 in column 2. Now 0, 1 (1), i.e. 000- and 0, 8 (8), i.e. -000 are the terms in the first group of column 2.

Comparing the terms of index 1 with the terms of index 2 in column 1,  $m_1(0001)$  is combined with  $m_9(1001)$  to yield 1, 9 (8), i.e. -001. This is recorded in column 2 and 1001 is checked off in column 1 because 0001 has already been checked off.  $m_8(1000)$  is combined with  $m_9(1001)$  to yield 8, 9 (1), i.e. 100-. This is recorded in column 2. 1000 and 1001 of column 1 have already been checked off. So, no need to check them off again. No more combinations of terms of index 1 and index 2 are possible. So, draw a line below the last combination of these groups, i.e. 8, 9 (1),

-001 in column 2. Now 1, 9 (8), i.e. -001 and 8, 9 (1), i.e. 100- are the terms in the second group of column 2.

Similarly, comparing the terms of index 2 with the terms of index 3 in column 1,

$m_6(0110)$  and  $m_7(0111)$  yield 6, 7 (1), i.e. 011-. Record it in column 2 and check off 6(0110) and 7(0111).

$m_6(0110)$  and  $m_{14}(1110)$  yield 6, 14 (8), i.e. -110. Record it in column 2 and check off 6(0110) and 14(1110).

$m_9(1001)$  and  $m_{13}(1101)$  yield 9, 13 (4), i.e. 1-01. Record it in column 2 and check off 9(1001) and 13(1101).

So, 6, 7 (1), i.e. 011-, and 6, 14 (8), i.e. -110 and 9, 13 (4), i.e. 1-01 are the terms in group 3 of column 2. Draw a line at the end of 9, 13 (4), i.e. 1-01.

Also, comparing the terms of index 3 with the terms of index 4 in column 1,

$m_7(0111)$  and  $m_{15}(1111)$  yield 7, 15 (8), i.e. -111. Record it in column 2 and check off 7(0111) and 15(1111).

$m_{13}(1101)$  and  $m_{15}(1111)$  yield 13, 15 (2), i.e. 11-1. Record it in column 2 and check off 13 and 15.

$m_{14}(1110)$  and  $m_{15}(1111)$  yield 14, 15 (1), i.e. 111-. Record it in column 2 and check off 14 and 15.

So, 7, 15 (8), i.e. -111, and 13, 15 (2), i.e. 11-1 and 14, 15 (1), i.e. 111- are the terms in group 4 of column 2. Column 2 is completed now.

Comparing the terms of group 1 with the terms of group 2 in column 2, the terms 0, 1 (1), i.e. 000– and 8, 9 (1), i.e. 100– are combined to form 0, 1, 8, 9 (1, 8), i.e. –00–. Record it in group 1 of column 3 and check off 0, 1 (1), i.e. 000–, and 8, 9 (1), i.e. 100– of column 2. The terms 0, 8 (8), i.e. –000 and 1, 9 (8), i.e. –001 are combined to form 0, 1, 8, 9 (1, 8), i.e. –00–. This has already been recorded in column 3. So, no need to record again. Check off 0, 8 (8), i.e. –000 and 1, 9 (8), i.e. –001 of column 2. Draw a line below 0, 1, 8, 9 (1, 8), i.e. –00–. This is the only term in group 1 of column 3. No term of group 2 of column 2 can be combined with any term of group 3 of column 2. So, no entries are made in group 2 of column 2.

Comparing the terms of group 3 of column 2 with the terms of group 4 of column 2, the terms 6, 7 (1), i.e. 011–, and 14, 15 (1), i.e. 111– are combined to form 6, 7, 14, 15 (1, 8), i.e. –11–. Record it in group 3 of column 3 and check off 6, 7 (1), i.e. 011– and 14, 15 (1), i.e. 111– of column 2. The terms 6, 14 (8), i.e. –110 and 7, 15 (8), i.e. –111 are combined to form 6, 7, 14, 15 (1, 8), i.e. –11–. This has already been recorded in column 3; so, check off 6, 14 (8), i.e. –110 and 7, 15 (8), i.e. –111 of column 2.

Observe that the terms 9, 13 (4), i.e. 1–01 and 13, 15 (2), i.e. 11–1 cannot be combined with any other terms. Similarly in column 3, the terms 0, 1, 8, 9 (1, 8), i.e. –00– and 6, 7, 14, 15 (1, 8), i.e. –11– cannot also be combined with any other terms. So, these 4 terms are the prime implicants.

The terms, which cannot be combined further, are labelled as P, Q, R, and S. These form the set of prime implicants.

EX:

Obtain the minimal expression for  $f = \sum m(1, 2, 3, 5, 6, 7, 8, 9, 12, 13, 15)$  using the tabular method.

**Solution**

The procedure to obtain the set of prime implicants is illustrated in Table 3.4.

**Table 3.4** Example 3.30

	Step 1	Step 2	Step 3	
Index 1	1 ✓	1, 3 (2) ✓	1, 3, 5, 7 (2, 4)	T
	2 ✓	1, 5 (4) ✓	1, 5, 9, 13 (4, 8)	S
	8 ✓	1, 9 (8) ✓	2, 3, 6, 7 (1, 4)	R
Index 2	3 ✓	2, 3 (1) ✓	8, 9, 12, 13 (1, 4)	Q
	5 ✓	2, 6 (4) ✓	5, 7, 13, 15 (2, 8)	P
	6 ✓	8, 9 (1) ✓		
	9 ✓	8, 12 (4) ✓		
Index 3	12 ✓	3, 7 (4) ✓		
	7 ✓	5, 7 (2) ✓		
Index 3	13 ✓	5, 13 (8) ✓		
	Index 4	15 ✓	6, 7 (1) ✓	
		9, 13 (4) ✓		
		12, 13 (1) ✓		
		7, 15 (8) ✓		
		13, 15 (2) ✓		

The non-combinable terms P, Q, R, S and T are recorded as prime implicants.

$$P \rightarrow 5, 7, 13, 15 (2, 8) = X 1 X 1 = BD$$

(Literals with weights 2 and 8, i.e. C and A are deleted. The lowest minterm is  $m_5(5 = 4 + 1)$ . So, literals with weights 4 and 1, i.e. B and D are present in non-complemented form. So, read it as BD.)

$$Q \rightarrow 8, 9, 12, 13 (1, 4) = 1 X 0 X = A\bar{C}$$

(Literals with weights 1 and 4, i.e. D and B are deleted. The lowest minterm is  $m_8$ . So, literal with weight 8 is present in non-complemented form and literal with weight 2 is present in complemented form. So, read it as  $A\bar{C}$ .)

$$R \rightarrow 2, 3, 6, 7 (1, 4) = 0 X 1 X = \bar{A}C$$

(Literals with weights 1 and 4, i.e. D and B are deleted. The lowest minterm is  $m_2$ . So, literal with weight 2 is present in non-complemented form and literal with weight 8 is present in complemented form. So, read it as  $\bar{A}C$ .)

$$S \rightarrow 1, 5, 9, 13 (4, 8) = X X 0 1 = \bar{C}D$$

(Literals with weights 4 and 8, i.e. B and A are deleted. The lowest minterm is  $m_1$ . So, literal with weight 1 is present in non-complemented form and literal with weight 2 is present in complemented form. So, read it as  $\bar{C}D$ .)

$$T \rightarrow 1, 3, 5, 7 (2, 4) = 0 X X 1 = \bar{A}D$$

(Literals with weights 2 and 4, i.e. C and B are deleted. The lowest minterm is 1. So, literal with weight 1 is present in non-complemented form and literal with weight 8 is present in complemented form. So, read it as  $\bar{A}D$ .)

The prime implicant chart of the expression

$$f = \sum m(1, 2, 3, 5, 6, 7, 8, 9, 12, 13, 15)$$

is as shown in Table 3.5. It consists of 11 columns corresponding to the number of minterms and 5 rows corresponding to the prime implicants P, Q, R, S, and T generated. Row R contains four x's at the intersections with columns 2, 3, 6, and 7, because these minterms are covered by the prime implicant R. A row is said to cover the columns in which it has x's. The problem now is to select a minimal subset of prime implicants, such that each column contains at least one x in the rows corresponding to the selected subset and the total number of literals in the prime implicants selected is as small as possible. These requirements guarantee that the number of unions of the selected prime implicants is equal to the original number of minterms and that, no other expression containing fewer literals can be found.

**Table 3.5** Example 3.30: Prime implicant chart

	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	
	1	2	3	5	6	7	8	9	12	13	15
*P → 5, 7, 13, 15 (2, 8)				x		x				x	x
*Q → 8, 9, 12, 13 (1, 4)							x	x	x	x	
*R → 2, 3, 6, 7 (1, 4)		x	x		x	x					
S → 1, 5, 9, 13 (4, 8)	x			x				x		x	
T → 1, 3, 5, 7 (2, 4)	x		x	x		x					

In the prime implicant chart of Table 3.5,  $m_2$  and  $m_6$  are covered by R only. So, R is an essential prime implicant. So, check off all the minterms covered by it, i.e.  $m_2, m_3, m_6,$  and  $m_7$ . Q is also an essential prime implicant because only Q covers  $m_8$  and  $m_{12}$ . Check off all the minterms covered by it, i.e.  $m_8, m_9, m_{12},$  and  $m_{13}$ . P is also an essential prime implicant, because  $m_{15}$  is covered only by P. So check off  $m_{15}, m_5, m_7,$  and  $m_{13}$  covered by it. Thus, only minterm 1 is not covered. Either row S or row T can cover it and both have the same number of literals. Thus, two minimal expressions are possible.

$$P + Q + R + S = BD + A\bar{C} + \bar{A}C + \bar{C}D$$

or

$$P + Q + R + T = BD + A\bar{C} + \bar{A}C + \bar{A}D$$




## UNIT-III

### COMBINATIONAL CIRCUITS
 
#### Combinational Logic

- Logic circuits for digital systems may be combinational or sequential.
- A combinational circuit consists of input variables, logic gates, and output variables.



For  $n$  input variables, there are  $2^n$  possible combinations of binary input variables. For each possible input combination, there is one and only one possible output combination. A combinational circuit can be described by  $m$  Boolean functions one for each output variable. Usually the inputs come from flip-flops and outputs go to flip-flops.

#### Design Procedure:

1. The problem is stated
2. The number of available input variables and required output variables is determined.
3. The input and output variables are assigned letters/symbols.
4. The truth table that defines the required relationship between inputs and outputs is derived.
5. The simplified Boolean function for each output is obtained.

## Adders:

Digital computers perform variety of information processing tasks, the one is arithmetic operations. And the most basic arithmetic operation is the addition of two binary digits. i.e., 4 basic possible operations are:


$$0+0=0, 0+1=1, 1+0=1, 1+1=10$$

The first three operations produce a sum whose length is one digit, but when augends and addend bits are equal to 1, the binary sum consists of two digits. The higher significant bit of this result is called a carry. A combinational circuit that performs the addition of two bits is called a half-adder. One that performs the addition of 3 bits (two significant bits & previous carry) is called a full adder. & 2 half adder can employ as a full-adder.

**The Half Adder:** A Half Adder is a combinational circuit with two binary inputs (augends and addend bits) and two binary outputs (sum and carry bits.) It adds the two inputs (A and B) and produces the sum (S) and the carry (C) bits. It is an arithmetic operation of addition of two single bit words.

Inputs		Outputs	
A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

(a) Truth table

 

(b) Block diagram


The Sum (S) bit and the carry (C) bit, according to the rules of binary addition, the sum (S) is the X-OR of A and B (It represents the LSB of the sum). Therefore,

$$S = A \oplus B$$

The carry (C) is the AND of A and B (it is 0 unless both the inputs are 1). Therefore,

$$C = AB$$

 
A half-adder can be realized by using one X-OR gate and one AND gate a



Logic diagrams of half-adder
 
## NAND LOGIC:


$$\begin{aligned}
 S &= A\bar{B} + \bar{A}B = A\bar{B} + A\bar{A} + \bar{A}B + B\bar{B} \\
 &= A(\bar{A} + \bar{B}) + B(\bar{A} + \bar{B}) \\
 &= A \cdot \bar{A}\bar{B} + B \cdot \bar{A}\bar{B} \\
 &= \overline{A \cdot \bar{A}\bar{B} \cdot B \cdot \bar{A}\bar{B}} \\
 C &= AB = \overline{\overline{AB}}
 \end{aligned}$$



Logic diagram of a half-adder using only 2-input NAND gates.
 
## NOR Logic:

$$\begin{aligned}
 S &= A\bar{B} + \bar{A}B = A\bar{B} + A\bar{A} + \bar{A}B + B\bar{B} \\
 &= A(\bar{A} + \bar{B}) + B(\bar{A} + \bar{B}) \\
 &= (A + B)(\bar{A} + \bar{B}) \\
 &= \overline{\overline{A + B + \bar{A} + \bar{B}}} \\
 C &= AB = \overline{\overline{AB}} = \overline{A + B}
 \end{aligned}$$



Logic diagram of a half-adder using only 2-input NOR gates.

## The Full Adder:

A Full-adder is a combinational circuit that adds two bits and a carry and outputs a sum bit and a carry bit. To add two binary numbers, each having two or more bits, the LSBs can be added by using a half-adder. The carry resulted from the addition of the LSBs is carried over to the next significant column and added to the two bits in that column. So, in the second and higher columns, the two data bits of that column and the carry bit generated from the addition in the previous column need to be added.


The full-adder adds the bits A and B and the carry from the previous column called the carry-in  $C_{in}$  and outputs the sum bit S and the carry bit called the carry-out  $C_{out}$ . The variable S gives the value of the least significant bit of the sum. The variable  $C_{out}$  gives the output carry. The



eight rows under the input variables designate all possible combinations of 1s and 0s that these variables may have. The 1s and 0s for the output variables are determined from the arithmetic sum of the input bits. When all the bits are 0s, the output is 0. The S output is equal to 1 when only 1 input is equal to 1 or when all the inputs are equal to 1. The C<sub>out</sub> has a carry of 1 if two or three inputs are equal to 1.

Inputs			Sum	Carry
A	B	C <sub>in</sub>	S	C <sub>out</sub>
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

(a) Truth table

 

(b) Block diagram

Full-adder.

From the truth table, a circuit that will produce the correct sum and carry bits in response to every possible combination of A,B and C<sub>in</sub> is described by

$$S = \overline{A}\overline{B}C_{in} + \overline{A}B\overline{C_{in}} + A\overline{B}\overline{C_{in}} + ABC_{in}$$


$$C_{out} = ABC_{in} + AB\overline{C_{in}} + A\overline{B}C_{in} + \overline{A}BC_{in}$$

and

$$S = A \oplus B \oplus C_{in}$$


$$C_{out} = AC_{in} + BC_{in} + AB$$

 The sum term of the full-adder is the X-OR of A,B, and C<sub>in</sub>, i.e, the sum bit the modulo sum of the data bits in that column and the carry from the previous column. The logic diagram of the full-adder using two X-OR gates and two AND gates (i.e, Two half adders) and one OR gate is



Logic diagram of a full-adder using two half-adders.

 The block diagram of a full-adder using two half-adders is :



Block diagram of a full-adder using two half-adders.

Even though a full-adder can be constructed using two half-adders, the disadvantage is that the bits must propagate through several gates in accession, which makes the total propagation delay greater than that of the full-adder circuit using AOI logic.

The Full-adder neither can also be realized using universal logic, i.e., either only NAND gates or only NOR gates as


$$A \oplus B = \overline{\overline{A \cdot AB} \cdot \overline{B \cdot AB}}$$

Then


$$S = A \oplus B \oplus C_{in} = \overline{\overline{(A \oplus B) \cdot (A \oplus B)C_{in}} \cdot \overline{C_{in} \cdot (A \oplus B)C_{in}}}$$

NAND Logic:
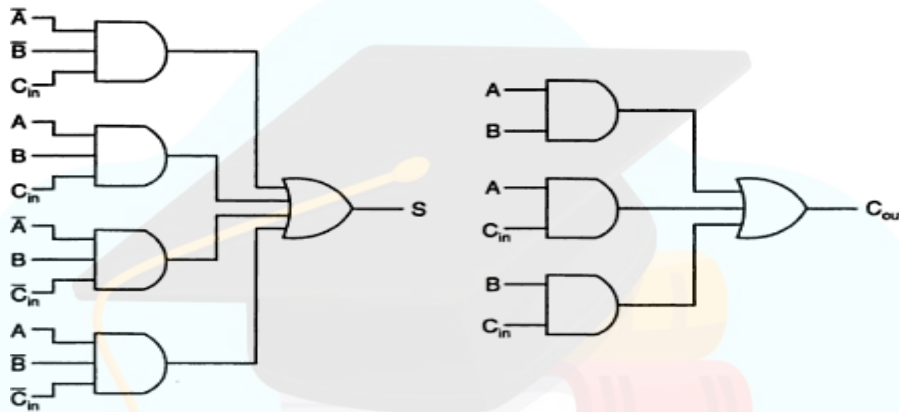
$$C_{out} = C_{in}(A \oplus B) + AB = \overline{\overline{C_{in}(A \oplus B)} \cdot \overline{AB}}$$



 Sum and carry bits of a full-adder using AOI logic.



Logic diagram of a full-adder using only 2-input NAND gates.


NOR Logic:

$$A \oplus B = \overline{\overline{(A + B)} + \overline{A + B}}$$

Then

$$S = A \oplus B \oplus C_{in} = \overline{\overline{(A \oplus B) + C_{in}} + \overline{(A \oplus B) + C_{in}}}$$
 
$$C_{out} = AB + C_{in}(A \oplus B) = \overline{\overline{A + B} + \overline{C_{in} + A \oplus B}}$$



Logic diagram of a full-adder using only 2-input NOR gates.

### Subtractors:

The subtraction of two binary numbers may be accomplished by taking the complement of the subtrahend and adding it to the minuend. By this, the subtraction operation becomes an addition operation and instead of having a separate circuit for subtraction, the adder itself can be used to perform subtraction. This results in reduction of hardware. In subtraction, each subtrahend bit of the number is subtracted from its corresponding significant minuend bit to form a difference bit. If the minuend bit is smaller than the subtrahend bit, a 1 is borrowed from the next significant position., that has been borrowed must be conveyed to the next higher pair of bits by means of a signal coming out (output) of a given stage and going into (input) the next higher stage.


### The Half-Subtractor:

A Half-subtractor is a combinational circuit that subtracts one bit from the other and produces the difference. It also has an output to specify if a 1 has been borrowed. . It is used to subtract the LSB of the subtrahend from the LSB of the minuend when one binary number is subtracted from the other.

A Half-subtractor is a combinational circuit with two inputs A and B and two outputs d and b. d indicates the difference and b is the output signal generated that informs the next stage that a 1 has been borrowed. When a bit B is subtracted from another bit A, a difference bit (d) and a borrow bit (b) result according to the rules given as

Inputs		Outputs	
A	B	d	b
0	0	0	0
1	0	1	0
1	1	0	0
0	1	1	1

(a) Truth table

 

(b) Block diagram


Half-subtractor.

The output borrow  $b$  is a 0 as long as  $A \geq B$ . It is a 1 for  $A=0$  and  $B=1$ . The  $d$  output is the result of the arithmetic operation  $2b+A-B$ .

A circuit that produces the correct difference and borrow bits in response to every possible combination of the two 1-bit numbers is, therefore,

$$d = A \oplus B + A \bar{B} \quad \text{and} \quad b = A \bar{B}$$

 That is, the difference bit is obtained by X-OR ing the two inputs, and the borrow bit is obtained by ANDing the complement of the minuend with the subtrahend. Note that logic for this exactly the same as the logic for output  $S$  in the half-adder.




Logic diagrams of a half-subtractor.

A half-subtractor can also be realized using universal logic either using only NAND gates or using NOR gates as:

NAND Logic:

$$d = A \oplus B = \overline{A \cdot AB} \cdot \overline{B \cdot AB}$$
 
$$b = \bar{A}B = B(\bar{A} + \bar{B}) = B(\overline{AB}) = \overline{B \cdot AB}$$




Logic diagram of a half-subtractor using only 2-input NAND gates.

NOR Logic:

$$d = A \oplus B = A\bar{B} + \bar{A}B = A\bar{B} + B\bar{B} + \bar{A}B + A\bar{A}$$

$$= \bar{B}(A + B) + \bar{A}(A + B) = \overline{B + \bar{A} + B + A + \bar{A} + B}$$
 
$$d = \bar{A}B = \bar{A}(A + B) = \overline{\bar{A}(A + B)} = A + (\bar{A} + B)$$




Logic diagram of a half-subtractor using only 2-input NOR gates.

### The Full-Subtractor:

The half-subtractor can be only for LSB subtraction. IF there is a borrow during the subtraction of the LSBs, it affects the subtraction in the next higher column; the subtrahend bit is subtracted from the minuend bit, considering the borrow from that column used for the subtraction in the preceding column. Such a subtraction is performed by a full-subtractor. It subtracts one bit (B) from another bit (A), when already there is a borrow  $b_i$  from this column for the subtraction in the preceding column, and outputs the difference bit (d) and the borrow bit(b) required from the next d and b. The two outputs present the difference and output borrow. The 1s and 0s for the output variables are determined from the subtraction of  $A-B-b_i$ .

Inputs			Difference	Borrow
A	B	$b_i$	d	b
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

(a) Truth table

 

(b) Block diagram

Full-subtractor.


From the truth table, a circuit that will produce the correct difference and borrow bits in response to every possible combinations of A,B and  $b_i$  is

$$\begin{aligned}
 d &= \bar{A}\bar{B}b_i + \bar{A}B\bar{b}_i + A\bar{B}\bar{b}_i + ABb_i \\
 &= b_i(AB + \bar{A}\bar{B}) + \bar{b}_i(A\bar{B} + \bar{A}B) \\
 &= b_i(\overline{A \oplus B}) + \bar{b}_i(A \oplus B) = A \oplus B \oplus b_i
 \end{aligned}$$

and

$$\begin{aligned}
 b &= \bar{A}\bar{B}b_i + \bar{A}B\bar{b}_i + \bar{A}Bb_i + ABb_i = \bar{A}B(b_i + \bar{b}_i) + (AB + \bar{A}\bar{B})b_i \\
 &= \bar{A}B + (A \oplus B)b_i
 \end{aligned}$$

 A full-subtractor can be realized using X-OR gates and AOI gates as




Logic diagram of a full-subtractor.

The full subtractor can also be realized using universal logic either using only NAND gates or using NOR gates as:

NAND Logic:


$$\begin{aligned}
 d &= A \oplus B \oplus b_i = \overline{\overline{(A \oplus B)} \oplus b_i} = \overline{\overline{(A \oplus B)}(A \oplus B)b_i \cdot b_i(A \oplus B)b_i} \\
 b &= \overline{AB} + b_i(\overline{A \oplus B}) = \overline{AB} + b_i(\overline{A \oplus B}) \\
 &= \overline{AB} \cdot b_i(\overline{A \oplus B}) = \overline{B(\overline{A + B})} \cdot b_i(b_i + (A \oplus B)) \\
 &= \overline{B \cdot AB} \cdot b_i[b_i \cdot (A \oplus B)]
 \end{aligned}$$

 

Logic diagram of a full-subtractor using only 2-input NAND gates.

NOR Logic:

$$\begin{aligned}
 d &= A \oplus B \oplus b_i = \overline{\overline{(A \oplus B)} \oplus b_i} \\
 &= \overline{(A \oplus B)b_i + (A \oplus B)\overline{b_i}} \\
 &= \overline{[(A \oplus B) + (A \oplus B)\overline{b_i}][b_i + (A \oplus B)\overline{b_i}]} \\
 &= \overline{(A \oplus B) + (A \oplus B) + b_i + b_i + (A \oplus B) + b_i} \\
 &= \overline{(A \oplus B) + (A \oplus B) + b_i + b_i + (A \oplus B) + b_i} \\
 b &= \overline{AB} + b_i(\overline{A \oplus B}) \\
 &= \overline{A(A + B)} + \overline{(A \oplus B)[(A \oplus B) + b_i]} \\
 &= \overline{A + (A + B) + (A \oplus B) + (A \oplus B) + b_i}
 \end{aligned}$$

 


Logic diagram of a full subtractor using only 2-input NOR gates.
 
### Binary Parallel Adder:

A binary parallel adder is a digital circuit that adds two binary numbers in parallel form and produces the arithmetic sum of those numbers in parallel form. It consists of full adders connected in a chain, with the output carry from each full-adder connected to the input carry of the next full-adder in the chain.

The interconnection of four full-adder (FA) circuits to provide a 4-bit parallel adder. The augends bits of A and addend bits of B are designated by subscript numbers from right to left, with subscript 1 denoting the lower-order bit. The carries are connected in a chain through the full-adders. The input carry to the adder is  $C_{in}$  and the output carry is  $C_4$ . The S output generates the required sum bits. When the 4-bit full-adder circuit is enclosed within an IC package, it has four terminals for the augends bits, four terminals for the addend bits, four terminals for the sum bits, and two terminals for the input and output carries. An n-bit parallel adder requires n full adders. It can be constructed from 4-bit, 2-bit and 1-bit full adder ICs by cascading several packages. The output carry from one package must be connected to the input carry of the one with the next higher-order bits. The 4-bit full adder is a typical example of an MSI function.



Logic diagram of a 4-bit binary parallel adder.

### Ripple carry adder:

In the parallel adder, the carry-out of each stage is connected to the carry-in of the next stage. The sum and carry-out bits of any stage cannot be produced, until sometime after the carry-in of that stage occurs. This is due to the propagation delays in the logic circuitry,


which lead to a time delay in the addition process. The carry propagation delay for each full-adder is the time between the application of the carry-in and the occurrence of the carry-out.

The 4-bit parallel adder, the sum ( $S_1$ ) and carry-out ( $C_1$ ) bits given by  $FA_1$  are not valid, until after the propagation delay of  $FA_1$ . Similarly, the sum  $S_2$  and carry-out ( $C_2$ ) bits given by  $FA_2$  are not valid until after the cumulative propagation delay of two full adders ( $FA_1$  and  $FA_2$ ), and so on. At each stage, the sum bit is not valid until after the carry bits in all the preceding stages are valid. Carry bits must propagate or ripple through all stages before the most significant sum bit is valid. Thus, the total sum (the parallel output) is not valid until after the cumulative delay of all the adders.

The parallel adder in which the carry-out of each full-adder is the carry-in to the next most significant adder is called a ripple carry adder. The greater the number of bits that a ripple carry adder must add, the greater the time required for it to perform a valid addition. If two numbers are added such that no carries occur between stages, then the add time is simply the propagation time through a single full-adder.
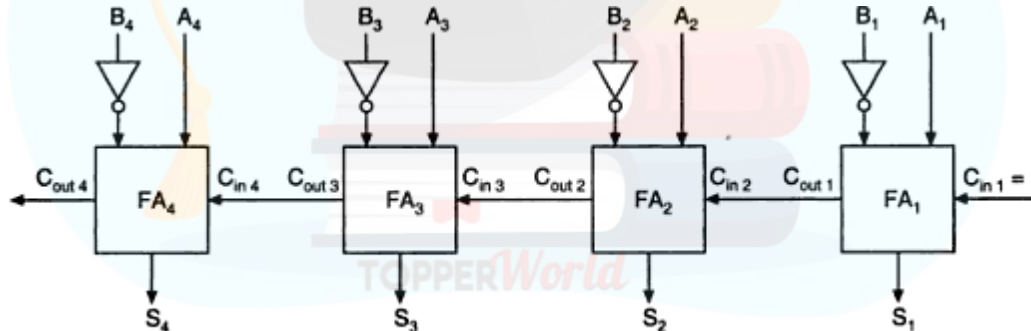
#### 4- Bit Parallel Subtractor:

The subtraction of binary numbers can be carried out most conveniently by means of complements, the subtraction  $A-B$  can be done by taking the 2's complement of  $B$  and adding it to  $A$ . The 2's complement can be obtained by taking the 1's complement and adding 1 to the least significant pair of bits. The 1's complement can be implemented with inverters as



Logic diagram of a 4-bit parallel subtractor.

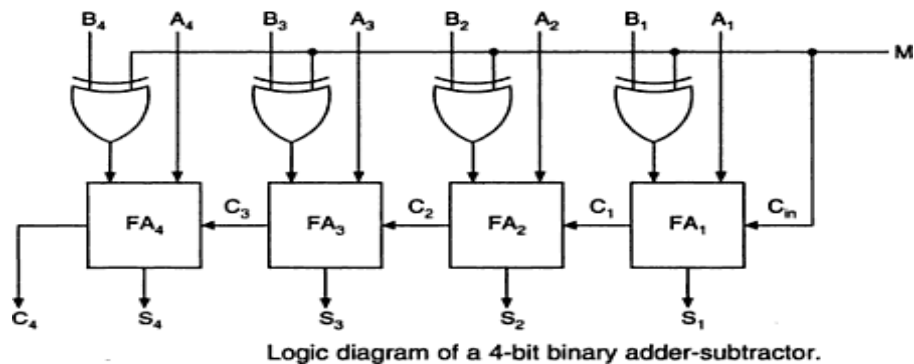
#### Binary-Adder Subtractor:

A 4-bit adder-subtractor, the addition and subtraction operations are combined into one circuit with one common binary adder. This is done by including an X-OR gate with each full-adder. The mode input  $M$  controls the operation. When  $M=0$ , the circuit is an adder, and when  $M=1$ , the circuit becomes a subtractor. Each X-OR gate receives input  $M$  and one of the inputs of  $B$ . When  $M=0$ ,  $B \oplus M = B$ . The full-adder receives the value of  $B$ , the input carry is 0





and the circuit performs  $A+B$ . when  $B \oplus 1 = B'$  and  $C_1=1$ . The B inputs are complemented and a 1 is through the input carry. The circuit performs the operation A plus the 2's complement of B.




### The Look-Ahead –Carry Adder:

In parallel-adder, the speed with which an addition can be performed is governed by the time required for the carries to propagate or ripple through all of the stages of the adder. The look-ahead carry adder speeds up the process by eliminating this ripple carry delay. It examines all the input bits simultaneously and also generates the carry-in bits for all the stages simultaneously.

The method of speeding up the addition process is based on the two additional functions of the full-adder, called the carry generate and carry propagate functions.

Consider one full adder stage; say the  $n$ th stage of a parallel adder as shown in fig. we know that is made by two half adders and that the half adder contains an X-OR gate to produce the sum and an AND gate to produce the carry. If both the bits  $A_n$  and  $B_n$  are 1s, a carry has to be generated in this stage regardless of whether the input carry  $C_{in}$  is a 0 or a 1. This is called generated carry, expressed as  $G_n = A_n \cdot B_n$  which has to appear at the output through the OR gate as shown in fig.

 

There is another possibility of producing a carry out. X-OR gate inside the half-adder at the input produces an intermediary sum bit- call it  $P_n$  –which is expressed as  $P_n = A_n \oplus B_n$ . Next  $P_n$  and  $C_n$  are added using the X-OR gate inside the second half adder to produce the final

sum bit and  $S_n = P_n \oplus C_n$  where  $P_n = A_n \oplus B_n$  and output carry  $C_0 = P_n \cdot C_n = (A_n \oplus B_n) \cdot C_n$  which becomes carry for the (n+1) th stage.

Consider the case of both  $P_n$  and  $C_n$  being 1. The input carry  $C_n$  has to be propagated to the output only if  $P_n$  is 1. If  $P_n$  is 0, even if  $C_n$  is 1, the and gate in the second half-adder will inhibit  $C_n$ . the carry out of the nth stage is 1 when either  $G_n=1$  or  $P_n \cdot C_n=1$  or both  $G_n$  and  $P_n \cdot C_n$  are equal to 1.

For the final sum and carry outputs of the nth stage, we get the following Boolean expressions.

$$S_n = P_n \oplus C_n \text{ where } P_n = A_n \oplus B_n$$

$$C_{n+1} = C_{n+1} = G_n + P_n \cdot C_n \text{ where } G_n = A_n \cdot B_n$$

Observe the recursive nature of the expression for the output carry at the nth stage which becomes the input carry for the (n+1)st stage .it is possible to express the output carry of a higher significant stage is the carry-out of the previous stage.

Based on these , the expression for the carry-outs of various full adders are as follows,

$$C_1 = G_0 + P_0 \cdot C_0$$

$$C_2 = G_1 + P_1 \cdot C_1 = G_1 + P_1 \cdot G_0 + P_1 \cdot P_0 \cdot C_0$$

$$C_3 = G_2 + P_2 \cdot C_2 = G_2 + P_2 \cdot G_1 + P_2 \cdot P_1 \cdot G_0 + P_2 \cdot P_1 \cdot P_0 \cdot C_0$$


$$C_4 = G_3 + P_3 \cdot C_3 = G_3 + P_3 \cdot G_2 + P_3 \cdot P_2 \cdot G_1 + P_3 \cdot P_2 \cdot P_1 \cdot G_0 + P_3 \cdot P_2 \cdot P_1 \cdot P_0 \cdot C_0$$

The general expression for n stages designated as 0 through (n - 1) would be

$$C_n = G_{n-1} + P_{n-1} \cdot C_{n-1} = G_{n-1} + P_{n-1} \cdot G_{n-2} + P_{n-1} \cdot P_{n-2} \cdot G_{n-3} + \dots + P_{n-1} \cdot \dots \cdot P_0 \cdot C_0$$

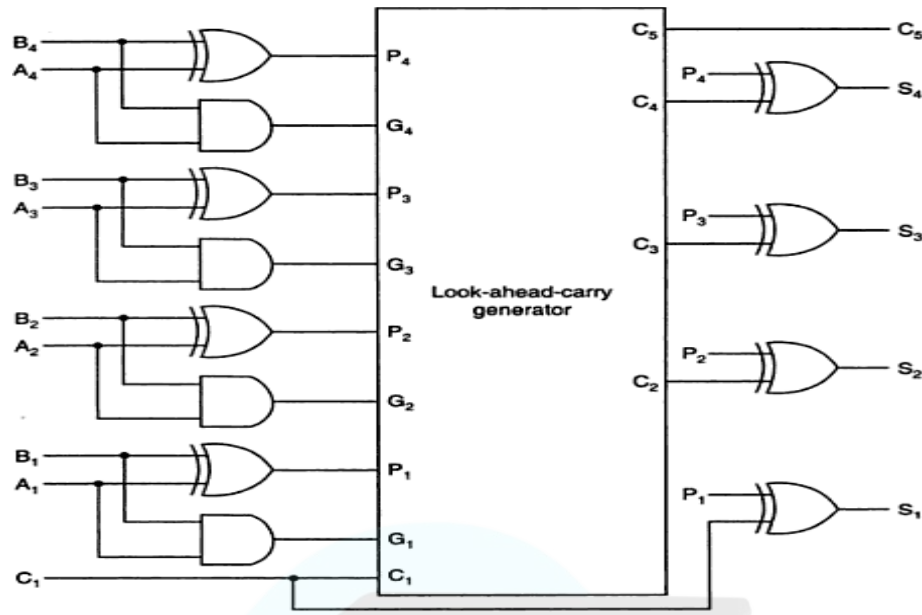Observe that the final output carry is expressed as a function of the input variables in SOP form. Which is two level AND-OR or equivalent NAND-NAND form. Observe that the full look-ahead scheme requires the use of OR gate with (n+1) inputs and AND gates with number of inputs varying from 2 to (n+1).





Logic diagram of a 4-bit look-ahead-carry adder.

## 2's complement Addition and Subtraction using Parallel Adders:

Most modern computers use the 2's complement system to represent negative numbers and to perform subtraction operations of signed numbers can be performed using only the addition operation, if we use the 2's complement form to represent negative numbers.

The circuit shown can perform both addition and subtraction in the 2's complement. This adder/subtractor circuit is controlled by the control signal ADD/SUB'. →hen the ADD/SUB' level is HIGH, the circuit performs the addition of the numbers stored in registers A and B. →hen the ADD/Sub' level is LOW, the circuit subtract the number in register B from the number in register A. The operation is:

→hen ADD/SUB' is a 1:

1. AND gates 1,3,5 and 7 are enabled, allowing  $B_0, B_1, B_2$  and  $B_3$  to pass to the OR gates 9,10,11,12. AND gates 2,4,6 and 8 are disabled, blocking  $B_0', B_1', B_2',$  and  $B_3'$  from reaching the OR gates 9,10,11 and 12.
2. The two levels  $B_0$  to  $B_3$  pass through the OR gates to the 4-bit parallel adder, to be added to the bits  $A_0$  to  $A_3$ . The sum appears at the output  $S_0$  to  $S_3$
3. Add/SUB' = 1 causes no carry into the adder.


When ADD/SUB' is a 0:

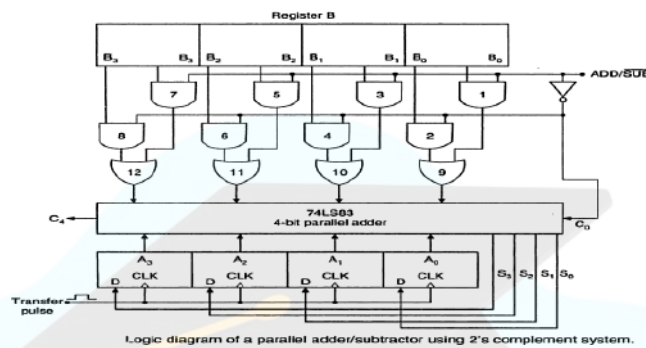1. AND gates 1,3,5 and 7 are disabled, allowing  $B_0, B_1, B_2$  and  $B_3$  from reaching the OR gates 9,10,11,12. AND gates 2,4,6 and 8 are enabled, blocking  $B_0', B_1', B_2',$  and  $B_3'$  from reaching the OR gates.



- The two levels  $B_0'$  to  $B_3'$  pass through the O' gates to the 4-bit parallel adder, to be added to the bits  $A_0$  to  $A_3$ . The  $C_0$  is now 1. thus the number in register B is converted to its 2's complement form.
- The difference appears at the output  $S_0$  to  $S_3$ .

Adders/Subtractors used for adding and subtracting signed binary numbers. In computers, the output is transferred into the register A (accumulator) so that the result of the addition or subtraction always end up stored in the register A. This is accomplished by applying a transfer pulse to the CLK inputs of register A.




## Serial Adder:

A serial adder is used to add binary numbers in serial form. The two binary numbers to be added serially are stored in two shift registers A and B. Bits are added one pair at a time through a single full adder (FA) circuit as shown. The carry out of the full-adder is transferred to a D flip-flop. The output of this flip-flop is then used as the carry input for the next pair of significant bits. The sum bit from the S output of the full-adder could be transferred to a third shift register. By shifting the sum into A while the bits of A are shifted out, it is possible to use one register for storing both augend and the sum bits. The serial input register B can be used to transfer a new binary number while the addend bits are shifted out during the addition.

The operation of the serial adder is:

Initially register A holds the augend, register B holds the addend and the carry flip-flop is cleared to 0. The outputs (SO) of A and B provide a pair of significant bits for the full-adder at x and y. The shift control enables both registers and carry flip-flop, so, at the clock pulse both registers are shifted once to the right, the sum bit from S enters the left most flip-flop of A, and the output carry is transferred into flip-flop Q. The shift control enables the registers for a number of clock pulses equal to the number of bits of the registers. For each succeeding clock pulse a new sum bit is transferred to A, a new carry is transferred to Q, and both registers are shifted once to the right. This process continues until the shift control is disabled. Thus the addition is accomplished by passing each pair of bits together with the previous carry through a single full adder circuit and transferring the sum, one bit at a time, into register A.

Initially, register A and the carry flip-flop are cleared to 0 and then the first number is added from B. While B is shifted through the full adder, a second number is transferred to it through its serial input. The second number is then added to the content of register A while a third number is transferred serially into register B. This can be repeated to form the addition of two, three, or more numbers and accumulate their sum in register A.

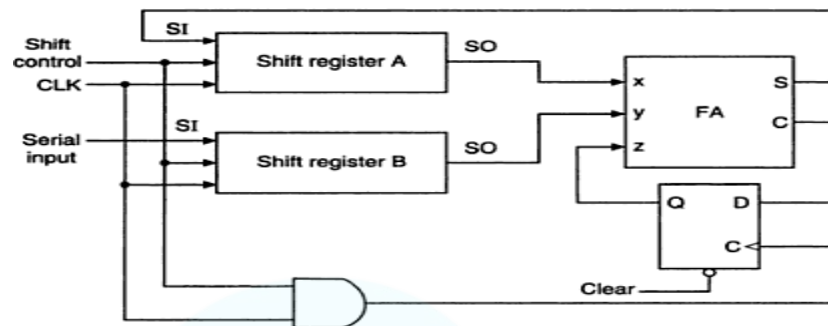

Logic diagram of a serial adder.

### Difference between Serial and Parallel Adders:

The parallel adder registers with parallel load, whereas the serial adder uses shift registers. The number of full adder circuits in the parallel adder is equal to the number of bits in the binary numbers, whereas the serial adder requires only one full adder circuit and a carry flip-flop. Excluding the registers, the parallel adder is a combinational circuit, whereas the serial adder is a sequential circuit. The sequential circuit in the serial adder consists of a full-adder and a flip-flop that stores the output carry.

### BCD Adder:

The BCD addition process:

1. Add the 4-bit BCD code groups for each decimal digit position using ordinary binary addition.
2. For those positions where the sum is 9 or less, the sum is in proper BCD form and no correction is needed.
3. When the sum of two digits is greater than 9, a correction of 0110 should be added to that sum, to produce the proper BCD result. This will produce a carry to be added to the next decimal position.

A BCD adder circuit must be able to operate in accordance with the above steps. In other words, the circuit must be able to do the following:

1. Add two 4-bit BCD code groups, using straight binary addition.



- Determine, if the sum of this addition is greater than 1101 (decimal 9); if it is, add 0110 (decimal 6) to this sum and generate a carry to the next decimal position.

The first requirement is easily met by using a 4-bit binary parallel adder such as the 74LS83 IC. For example, if the two BCD code groups  $A_3A_2A_1A_0$  and  $B_3B_2B_1B_0$  are applied to a 4-bit parallel adder, the adder will output  $S_4S_3S_2S_1S_0$ , where  $S_4$  is actually  $C_4$ , the carry-out of the MSB bits.

The sum outputs  $S_4S_3S_2S_1S_0$  can range anywhere from 00000 to 100109 when both the BCD code groups are 1001 (=9). The circuitry for a BCD adder must include the logic needed to detect whenever the sum is greater than 01001, so that the correction can be added in. Those cases, where the sum is greater than 1001 are listed as:

$S_4$	$S_3$	$S_2$	$S_1$	$S_0$	Decimal number
0	1	0	1	0	10
0	1	0	1	1	11
0	1	1	0	0	12
0	1	1	0	1	13
0	1	1	1	0	14
0	1	1	1	1	15
1	0	0	0	0	16
1	0	0	0	1	17
1	0	0	1	0	18

Let us define a logic output X that will go HIGH only when the sum is greater than 01001 (i.e., for the cases in table). If examine these cases, see that X will be HIGH for either of the following conditions:

- Whenever  $S_4=1$  (sum greater than 15)
- Whenever  $S_3=1$  and either  $S_2$  or  $S_1$  or both are 1 (sum 10 to 15)


This condition can be expressed as

$$X = S_4 + S_3(S_2 + S_1)$$

Whenever  $X=1$ , it is necessary to add the correction factor 0110 to the sum bits, and to generate a carry. The circuit consists of three basic parts. The two BCD code groups  $A_3A_2A_1A_0$  and  $B_3B_2B_1B_0$  are added together in the upper 4-bit adder, to produce the sum  $S_4S_3S_2S_1S_0$ . The logic gates shown implement the expression for X. The lower 4-bit adder will add the correction 0110 to the sum bits, only when  $X=1$ , producing the final BCD sum output represented by  $\sum_3\sum_2\sum_1\sum_0$ . The X is also the carry-out that is produced when the sum is greater than 01001. When  $X=0$ , there is no carry and no addition of 0110. In such cases,  $\sum_3\sum_2\sum_1\sum_0 = S_3S_2S_1S_0$ .



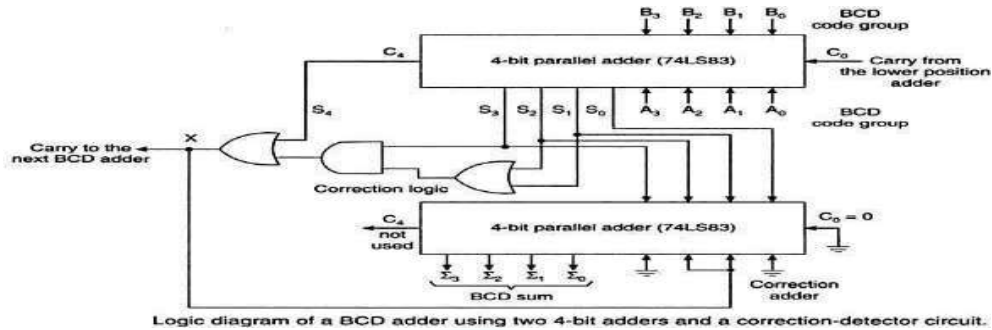Two or more BCD adders can be connected in cascade when two or more digit decimal numbers are to be added. The carry-out of the first BCD adder is connected as the carry-in of the second BCD adder, the carry-out of the second BCD adder is connected as the carry-in of the third BCD adder and so on.



### EXCESS-3(XS-3) ADDER:

To perform Excess-3 additions,

1. Add two xs-3 codegroups
2. If carry=1, add 0011(3) to the sum of those two codegroups  
If carry =0, subtract 0011(3) i.e., add 1101 (13 in decimal) to the sum of those two code groups.

Ex: Add 9 and 5

	1100	9 in Xs-3
	+1000	5 in xs-3
	-----	
1	0100	there is a carry
+0011	0011	add 3 to each group
	-----	
0100	0111	14 in xs-3
(1)	(4)	

**EX:**

(b)	0 1 1 1	4 in XS-3
	+ 0 1 1 0	3 in XS-3
	-----	
	1 1 0 1	no carry
	+ 1 1 0 1	Subtract 3 (i.e. add 13)
	-----	
Ignore carry	1 1 0 1 0	7 in XS-3
	(7)	

Implementation of xs-3 adder using 4-bit binary adders is shown. The augend ( $A_3 A_2 A_1 A_0$ ) and addend ( $B_3 B_2 B_1 B_0$ ) in xs-3 are added using the 4-bit parallel adder. If the carry is a 1, then 0011(3) is added to the sum bits  $S_3 S_2 S_1 S_0$  of the upper adder in the lower 4-bit parallel

adder. If the carry is a 0, then 1101(3) is added to the sum bits (This is equivalent to subtracting 0011(3) from the sum bits. The correct sum in xs-3 is obtained

### Excess-3 (XS-3) Subtractor:

To perform Excess-3 subtraction,

1. Complement the subtrahend
2. Add the complemented subtrahend to the minuend.
3. If carry = 1, result is positive. Add 3 and end around carry to the result. If carry = 0, the result is negative. Subtract 3, i.e., and take the 1's complement of the result.

Ex: Perform 9-4

1100	9 in xs-3
+1000	Complement of 4 in Xs-3
-----	
(1) 0100	There is a carry
+0011	Add 0011(3)
-----	
0111	
1	End around carry
-----	
1000	5 in xs-3

The minuend and the 1's complement of the subtrahend in xs-3 are added in the upper 4-bit parallel adder. If the carry-out from the upper adder is a 0, then 1101 is added to the sum bits of the upper adder in the lower adder and the sum bits of the lower adder are complemented to get the result. If the carry-out from the upper adder is a 1, then 3=0011 is added to the sum bits of the lower adder and the sum bits of the lower adder give the result.

### Binary Multipliers:

In binary multiplication by the paper and pencil method, is modified somewhat in digital machines because a binary adder can add only two binary numbers at a time. In a binary multiplier, instead of adding all the partial products at the end, they are added two at a time and their sum accumulated in a register (the accumulator register). In addition, when the multiplier bit is a 0, 0s are not written down and added because it does not affect the final result. Instead, the multiplicand is shifted left by one bit.

The multiplication of 1110 by 1001 using this process is

Multiplicand 1110

Multiplier 1001

1110

The LSB of the multiplier is a 1; write down the multiplicand; shift the multiplicand one position to the left (1 1 1 0 0)

1110

The second multiplier bit is a 0; write down the previous result 1110; shift the multiplicand to the left again (1 1 1 0

0 0)





+1110000

The fourth multiplier bit is a 1 write down the new multiplicand add it to the first partial product to obtain the final product.

1111110

This multiplication process can be performed by the serial multiplier circuit, which multiplies two 4-bit numbers to produce an 8-bit product. The circuit consists of following elements

**X register:** A 4-bit shift register that stores the multiplier --- it will shift right on the falling edge of the clock. Note that 0s are shifted in from the left.

**B register:** An 8-bit register that stores the multiplicand; it will shift left on the falling edge of the clock. Note that 0s are shifted in from the right.

**A register:** An 8-bit register, i.e., the accumulator that accumulates the partial products.

**Adder:** An 8-bit parallel adder that produces the sum of A and B registers. The adder outputs  $S_7$  through  $S_0$  are connected to the D inputs of the accumulator so that the sum can be transferred to the accumulator only when a clock pulse gets through the AND gate.

The circuit operation can be described by going through each step in the multiplication of 1110 by 1001. The complete process requires 4 clock cycles.

**1. Before the first clock pulse:** Prior to the occurrence of the first clock pulse, the register A is loaded with 00000000, the register B with the multiplicand 00001110, and the register X with the multiplier 1001. Assume that each of these registers is loaded using its asynchronous inputs (i.e., PRESET and CLEAR). The output of the adder will be the sum of A and B, i.e., 00001110.

**2. First Clock pulse:** Since the LSB of the multiplier ( $X_0$ ) is a 1, the first clock pulse gets through the AND gate and its positive going transition transfers the sum outputs into the accumulator. The subsequent negative going transition causes the X and B registers to shift right and left, respectively. This produces a new sum of A and B.

**3. Second Clock Pulse:** The second bit of the original multiplier is now in  $X_0$ . Since this bit is a 0, the second clock pulse is inhibited from reaching the accumulator. Thus, the sum outputs are not transferred into the accumulator and the number in the accumulator does not change. The negative going transition of the clock pulse will again shift the X and B registers. Again a new sum is produced.

**4. Third Clock Pulse:** The third bit of the original multiplier is now in  $X_0$ ; since this bit is a 0, the third clock pulse is inhibited from reaching the accumulator. Thus, the sum outputs are not transferred into the accumulator and the number in the accumulator does not change. The negative going transition of the clock pulse will again shift the X and B registers. Again a new sum is produced.

**5. Fourth Clock Pulse:** The last bit of the original multiplier is now in  $X_0$ , and since it is a 1, the positive going transition of the fourth pulse transfers the sum into the accumulator. The accumulator now holds the final product. The negative going transition of the clock pulse shifts X and B again. Note that, X is now 0000, since all the multiplier bits have been shifted out.

## Code converters:

The availability of a large variety of codes for the same discrete elements of information results in the use of different codes by different digital systems. It is sometimes necessary to use the output of one system as the input to another. A conversion circuit must be

inserted between the two systems if each uses different codes for the same information. Thus a code converter is a logic circuit whose inputs are bit patterns representing numbers (or character) in one code and whose outputs are the corresponding representation in a different code. Code converters are usually multiple output circuits.

To convert from binary code A to binary code B, the input lines must supply the bit combination of elements as specified by code A and the output lines must generate the corresponding bit combination of code B. A combinational circuit performs this transformation by means of logic gates.

For example, a binary-to-gray code converter has four binary input lines  $B_4, B_3, B_2, B_1$  and four gray code output lines  $G_4, G_3, G_2, G_1$ . When the input is 0010, for instance, the output should be 0011 and so forth. To design a code converter, we use a code table treating it as a truth table to express each output as a Boolean algebraic function of all the inputs.

In this example, of binary-to-gray code conversion, we can treat the binary to the gray code table as four truth tables to derive expressions for  $G_4, G_3, G_2,$  and  $G_1$ . Each of these four expressions would, in general, contain all the four input variables  $B_4, B_3, B_2,$  and  $B_1$ . Thus, this code converter is actually equivalent to four logic circuits, one for each of the truth tables.


The logic expression derived for the code converter can be simplified using the usual techniques, including 'don't cares' if present. Even if the input is an unweighted code, the same cell numbering method which we used earlier can be used, but the cell numbers -- must correspond to the input combinations as if they were an 8-4-2-1 weighted code. s

### Design of a 4-bit binary to gray code converter:

$$\begin{aligned}
 G_4 &= \sum m(8, 9, 10, 11, 12, 13, 14, 15) & G_4 &= B_4 \\
 G_3 &= \sum m(4, 5, 6, 7, 8, 9, 10, 11) & G_3 &= \bar{B}_4 B_3 + B_4 \bar{B}_3 = B_4 \oplus B_3 \\
 G_2 &= \sum m(2, 3, 4, 5, 10, 11, 12, 13) & G_2 &= \bar{B}_3 B_2 + B_3 \bar{B}_2 = B_3 \oplus B_2 \\
 G_1 &= \sum m(1, 2, 5, 6, 9, 10, 13, 14) & G_1 &= \bar{B}_2 B_1 + B_2 \bar{B}_1 = B_2 \oplus B_1
 \end{aligned}$$


4-bit binary				4-bit Gray			
$B_4$	$B_3$	$B_2$	$B_1$	$G_4$	$G_3$	$G_2$	$G_1$
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	1
0	0	1	1	0	0	1	0
0	1	0	0	0	1	1	0
0	1	0	1	0	1	1	1
0	1	1	0	0	1	0	1
0	1	1	1	0	1	0	0
1	0	0	0	1	1	0	0
1	0	0	1	1	1	0	1
1	0	1	0	1	1	1	1
1	0	1	1	1	1	1	0
1	1	0	0	1	0	1	0
1	1	0	1	1	0	1	1
1	1	1	0	1	0	0	1
1	1	1	1	1	0	0	0

(a) Conversion table

 

(c) Logic diagram

4-bit binary-to-Gray code converter

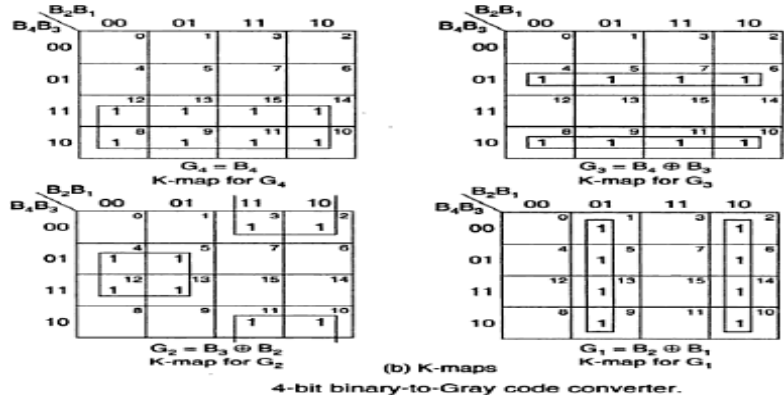

(b) K-maps  
4-bit binary-to-Gray code converter.


Design of a 4-bit gray to Binary code converter:

$$\begin{aligned}
 B_4 &= \Sigma m(12, 13, 15, 14, 10, 11, 9, 8) = \Sigma m(8, 9, 10, 11, 12, 13, 14, 15) \\
 B_3 &= \Sigma m(6, 7, 5, 4, 10, 11, 9, 8) = \Sigma m(4, 5, 6, 7, 8, 9, 10, 11) \\
 B_2 &= \Sigma m(3, 2, 5, 4, 15, 14, 9, 8) = \Sigma m(2, 3, 4, 5, 8, 9, 14, 15) \\
 B_1 &= \Sigma m(1, 2, 7, 4, 13, 14, 11, 8) = \Sigma m(1, 2, 4, 7, 8, 11, 13, 14)
 \end{aligned}$$


$$\begin{aligned}
 B_4 &= G_4 \\
 B_3 &= \bar{G}_4 G_3 + G_4 \bar{G}_3 = G_4 \oplus G_3 \\
 B_2 &= \bar{G}_4 G_3 \bar{G}_2 + \bar{G}_4 \bar{G}_3 G_2 + G_4 \bar{G}_3 \bar{G}_2 + G_4 G_3 G_2 \\
 &= \bar{G}_4 (G_3 \oplus G_2) + G_4 (\bar{G}_3 \oplus \bar{G}_2) = G_4 \oplus G_3 \oplus G_2 = B_3 \oplus G_2 \\
 B_1 &= \bar{G}_4 \bar{G}_3 \bar{G}_2 G_1 + \bar{G}_4 \bar{G}_3 G_2 \bar{G}_1 + \bar{G}_4 G_3 G_2 G_1 + \bar{G}_4 G_3 \bar{G}_2 \bar{G}_1 + G_4 G_3 \bar{G}_2 G_1 \\
 &\quad + G_4 G_3 G_2 \bar{G}_1 + G_4 \bar{G}_3 G_2 G_1 + G_4 \bar{G}_3 \bar{G}_2 \bar{G}_1 \\
 &= \bar{G}_4 \bar{G}_3 (G_2 \oplus G_1) + G_4 G_3 (G_2 \oplus G_1) + \bar{G}_4 G_3 (\bar{G}_2 \oplus \bar{G}_1) + G_4 \bar{G}_3 (\bar{G}_2 \oplus \bar{G}_1) \\
 &= (G_2 \oplus G_1) (\bar{G}_4 \oplus G_3) + (\bar{G}_2 \oplus \bar{G}_1) (G_4 \oplus G_3) \\
 &= G_4 \oplus G_3 \oplus G_2 \oplus G_1
 \end{aligned}$$

4-bit Gray				4-bit binary			
G <sub>4</sub>	G <sub>3</sub>	G <sub>2</sub>	G <sub>1</sub>	B <sub>4</sub>	B <sub>3</sub>	B <sub>2</sub>	B <sub>1</sub>
0	0	0	0	0	0	0	0
0	0	0	1	0	0	1	0
0	0	1	1	0	0	1	1
0	1	1	1	0	1	1	0
0	1	1	0	0	1	1	1
0	1	0	0	0	1	0	1
1	1	0	1	1	0	0	1
1	1	1	1	1	0	1	0
1	1	1	0	1	0	1	1
1	0	1	1	1	1	0	1
1	0	0	1	1	1	1	0
1	0	0	0	1	1	1	1


(a) Conversion table

 


(c) Logic diagram

 

 B<sub>4</sub> = G<sub>4</sub>  
K-map for B<sub>4</sub>



 B<sub>3</sub> = G<sub>4</sub> XOR G<sub>3</sub>  
K-map for B<sub>3</sub>



(b) K-maps  
4-bit Gray-to-binary code converter.

Design of a 4-bit BCD to XS-3 code converter:


8421 code				XS-3 code			
B <sub>4</sub>	B <sub>3</sub>	B <sub>2</sub>	B <sub>1</sub>	X <sub>4</sub>	X <sub>3</sub>	X <sub>2</sub>	X <sub>1</sub>
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0

(a) Conversion table

$X_4 = \sum m(5, 6, 7, 8, 9) + d(10, 11, 12, 13, 14, 15)$   
 $X_3 = \sum m(1, 2, 3, 4, 9) + d(10, 11, 12, 13, 14, 15)$   
 $X_2 = \sum m(0, 3, 4, 7, 8) + d(10, 11, 12, 13, 14, 15)$   
 $X_1 = \sum m(0, 2, 4, 6, 8) + d(10, 11, 12, 13, 14, 15)$   
 The minimal expressions are  
 $X_4 = B_4 + B_3B_2 + B_3B_1$   
 $X_3 = B_3\bar{B}_2\bar{B}_1 + \bar{B}_3B_1 + B_3B_2$   
 $X_2 = \bar{B}_2\bar{B}_1 + B_2B_1$   
 $X_1 = \bar{B}_1$

(b) Minimal expressions

4-bit BCD-to-XS-3 code converter

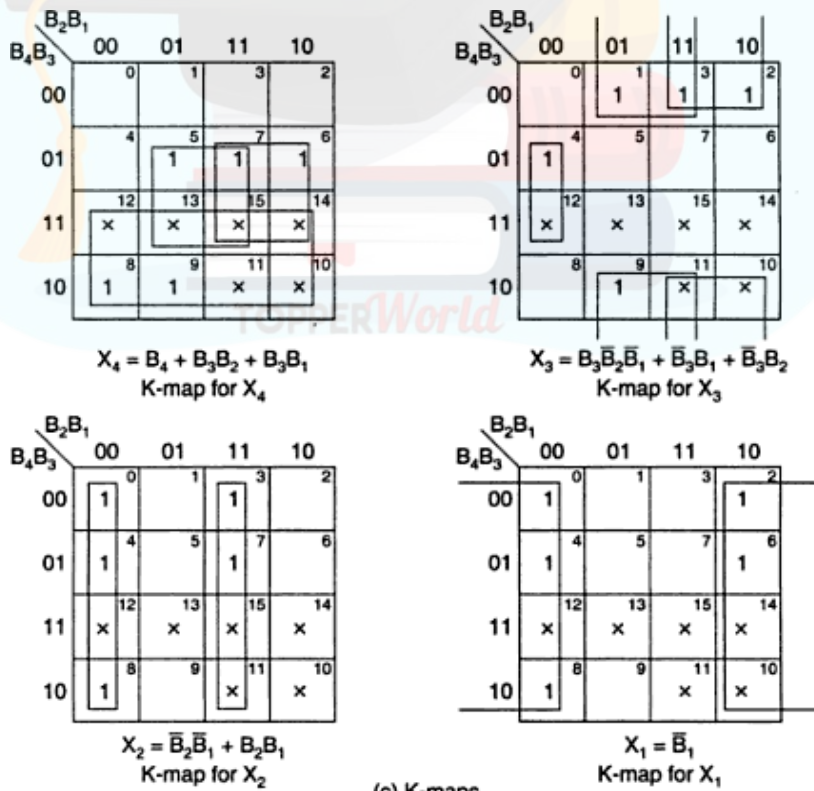


(c) K-maps

4-bit BCD-to-XS-3 code converter.

Design of a BCD to gray code converter:

BCD code				Gray code			
B <sub>3</sub>	B <sub>2</sub>	B <sub>1</sub>	B <sub>0</sub>	G <sub>3</sub>	G <sub>2</sub>	G <sub>1</sub>	G <sub>0</sub>
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	1
0	0	1	1	0	0	1	0
0	1	0	0	0	1	1	0
0	1	1	0	0	1	0	1
0	1	1	1	0	1	0	0
1	0	0	0	1	1	0	0
1	0	0	1	1	1	0	1

(a) BCD-to-Gray code conversion table

 

(b) Logic diagram

BCD-to-Gray code converter.




K-maps for a BCD-to-Gray code converter.


Design of a SOP circuit to Detect the Decimal numbers 5 through 12 in a 4-bit gray code Input:

Decimal number	4-bit Gray code				Output
	A	B	C	D	f
0	0	0	0	0	0
1	0	0	0	1	0
2	0	0	1	1	0
3	0	0	1	0	0
4	0	1	1	0	0
5	0	1	1	1	1
6	0	1	0	1	1
7	0	1	0	0	1
8	1	1	0	0	1
9	1	1	0	1	1
10	1	1	1	1	1
11	1	1	1	0	1
12	1	0	1	0	1
13	1	0	1	1	0
14	1	0	0	1	0
15	1	0	0	0	0

(a) Truth table

 

(b) K-map

 


(c) NAND logic

Truth table, K-map and logic diagram for the SOP circuit.


Design of a SOP circuit to detect the decimal numbers 0,2,4,6,8 in a 4-bit 5211 BCDcode input:

Decimal number	5211 code				Output
	A	B	C	D	f
0	0	0	0	0	1
1	0	0	0	1	0
2	0	0	1	1	1
3	0	1	0	1	0
4	0	1	1	1	1
5	1	0	0	0	0
6	1	0	1	0	1
7	1	1	0	0	0
8	1	1	1	0	1
9	1	1	1	1	0

(a) Truth table

 

(b) K-map

 

(c) Logic diagram


Truth table, K-map and logic diagram for the SOP circuit.

Design of a Combinational circuit to produce the 2's complement of a 4-bit binary number:

Input				Output			
A	B	C	D	E	F	G	H
0	0	0	0	0	0	0	0
0	0	0	1	1	1	1	1
0	0	1	0	1	1	1	0
0	0	1	1	1	1	0	1
0	1	0	0	1	1	0	0
0	1	0	1	1	0	1	1
0	1	1	0	1	0	1	0
0	1	1	1	1	0	0	1
1	0	0	0	1	0	0	0
1	0	0	1	0	1	1	1
1	0	1	0	0	1	1	0
1	0	1	1	0	1	0	1
1	1	0	0	0	1	0	0
1	1	0	1	0	0	1	1
1	1	1	0	0	0	1	0
1	1	1	1	0	0	0	1

 (a) Conversion table

Conversion table and K-maps for the circuit




(a) Seven-segment display



$$f_{min} = B + CD + \bar{C}D$$


(b) K-map

 

 (c) Logic diagram

Comparators:

$$\text{EQUALITY} = (A_3 \odot B_3)(A_2 \odot B_2)(A_1 \odot B_1)(A_0 \odot B_0)$$



Block diagram of a 1-bit comparator.

The logic for a 1-bit magnitude comparator: Let the 1-bit numbers be  $A = A_0$  and  $B = B_0$ .  
If  $A_0 = 1$  and  $B_0 = 0$ , then  $A > B$ .

Therefore,

$$A > B: G = A_0 \bar{B}_0$$

If  $A_0 = 0$  and  $B_0 = 1$ , then  $A < B$ .

Therefore,

$$A < B: L = \bar{A}_0 B_0$$


If  $A_0$  and  $B_0$  coincide, i.e.  $A_0 = B_0 = 0$  or if  $A_0 = B_0 = 1$ , then  $A = B$ .

Therefore,

$$A = B: E = A_0 \odot B_0$$

$A_0$	$B_0$	L	E	G
0	0	0	1	0
0	1	1	0	0
1	0	0	0	1
1	1	0	1	0

(a) Truth table

 

(b) Logic diagram  
1-bit comparator.

## 1. Magnitude Comparator:

### 1-bit Magnitude Comparator:

The logic for a 2-bit magnitude comparator: Let the two 2-bit numbers be  $A = A_1 A_0$  and  $B = B_1 B_0$ .

1. If  $A_1 = 1$  and  $B_1 = 0$ , then  $A > B$  or

2. If  $A_1$  and  $B_1$  coincide and  $A_0 = 1$  and  $B_0 = 0$ , then  $A > B$ . So the logic expression for  $A > B$  is

$$A > B: G = A_1 \bar{B}_1 + (A_1 \odot B_1) A_0 \bar{B}_0$$


1. If  $A_1 = 0$  and  $B_1 = 1$ , then  $A < B$  or

2. If  $A_1$  and  $B_1$  coincide and  $A_0 = 0$  and  $B_0 = 1$ , then  $A < B$ . So the expression for  $A < B$  is

$$A < B: L = \bar{A}_1 B_1 + (A_1 \odot B_1) \bar{A}_0 B_0$$

If  $A_1$  and  $B_1$  coincide and if  $A_0$  and  $B_0$  coincide then  $A = B$ . So the expression for  $A = B$  is
 
$$A = B: E = (A_1 \odot B_1)(A_0 \odot B_0)$$



Logic diagram of a 2-bit magnitude comparator.

#### 4- Bit Magnitude Comparator:

The logic for a 4-bit magnitude comparator: Let the two 4-bit numbers be  $A = A_3A_2A_1A_0$  and  $B = B_3B_2B_1B_0$ .

1. If  $A_3 = 1$  and  $B_3 = 0$ , then  $A > B$ . Or
2. If  $A_3$  and  $B_3$  coincide, and if  $A_2 = 1$  and  $B_2 = 0$ , then  $A > B$ . Or
3. If  $A_3$  and  $B_3$  coincide, and if  $A_2$  and  $B_2$  coincide, and if  $A_1 = 1$  and  $B_1 = 0$ , then  $A > B$ . Or
4. If  $A_3$  and  $B_3$  coincide, and if  $A_2$  and  $B_2$  coincide, and if  $A_1$  and  $B_1$  coincide, and if  $A_0 = 1$  and  $B_0 = 0$ , then  $A > B$ .

From these statements, we see that the logic expression for  $A > B$  can be written as

$$(A > B) = A_3\bar{B}_3 + (A_3 \odot B_3)A_2\bar{B}_2 + (A_3 \odot B_3)(A_2 \odot B_2)A_1\bar{B}_1 + (A_3 \odot B_3)(A_2 \odot B_2)(A_1 \odot B_1)A_0\bar{B}_0$$


Similarly, the logic expression for  $A < B$  can be written as

$$A < B = \bar{A}_3B_3 + (A_3 \odot B_3)\bar{A}_2B_2 + (A_3 \odot B_3)(A_2 \odot B_2)\bar{A}_1B_1 + (A_3 \odot B_3)(A_2 \odot B_2)(A_1 \odot B_1)\bar{A}_0B_0$$

If  $A_3$  and  $B_3$  coincide and if  $A_2$  and  $B_2$  coincide and if  $A_1$  and  $B_1$  coincide and if  $A_0$  and  $B_0$  coincide, then  $A = B$ .


So the expression for  $A = B$  can be written as
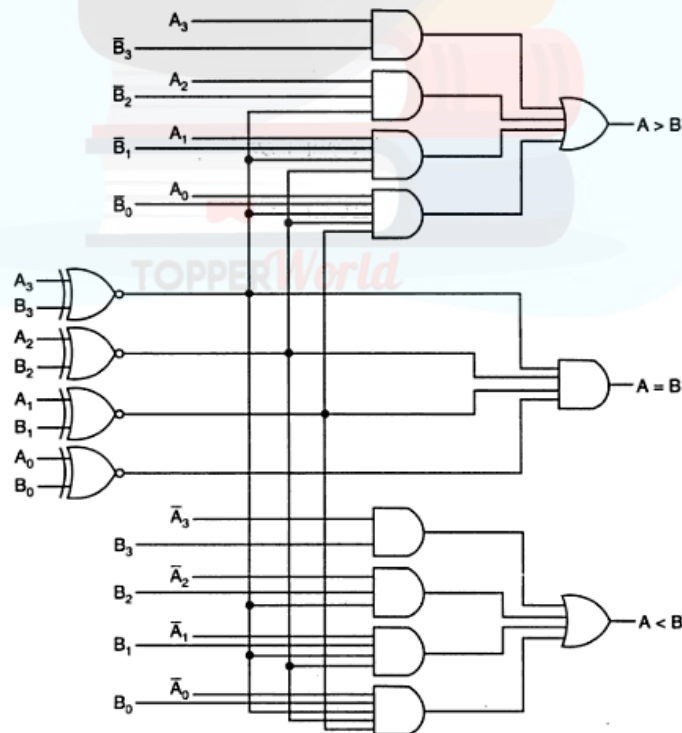
$$(A = B) = (A_3 \odot B_3)(A_2 \odot B_2)(A_1 \odot B_1)(A_0 \odot B_0)$$






## IC Comparator:

 


(a) Pin diagram of 7485

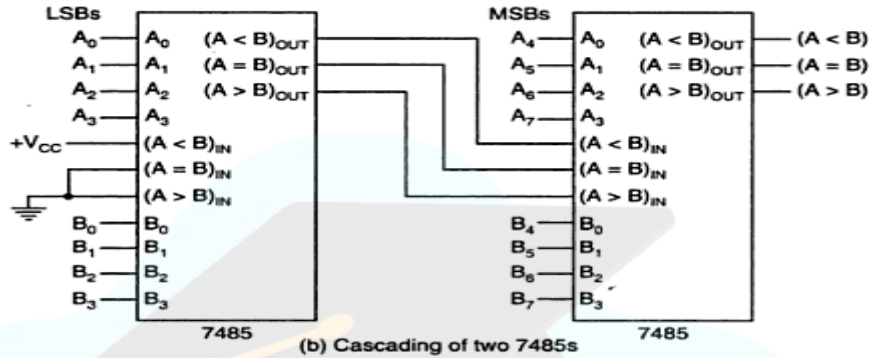


(b) Cascading of two 7485s

Pin diagram and cascading of 7485 4-bit comparators.

## ENCODERS:

 

Use of 7485 as a 5-bit comparator.

 


Block diagram of encoder.

## Octal to Binary Encoder:

Octal digits	Binary		
	A <sub>2</sub>	A <sub>1</sub>	A <sub>0</sub>
D <sub>0</sub>	0	0	0
D <sub>1</sub>	0	0	1
D <sub>2</sub>	0	1	0
D <sub>3</sub>	0	1	1
D <sub>4</sub>	1	0	0
D <sub>5</sub>	1	0	1
D <sub>6</sub>	1	1	0
D <sub>7</sub>	1	1	1


(a) Truth table

 

(b) Logic diagram

Octal-to-binary encoder.

## Decimal to BCD Encoder:

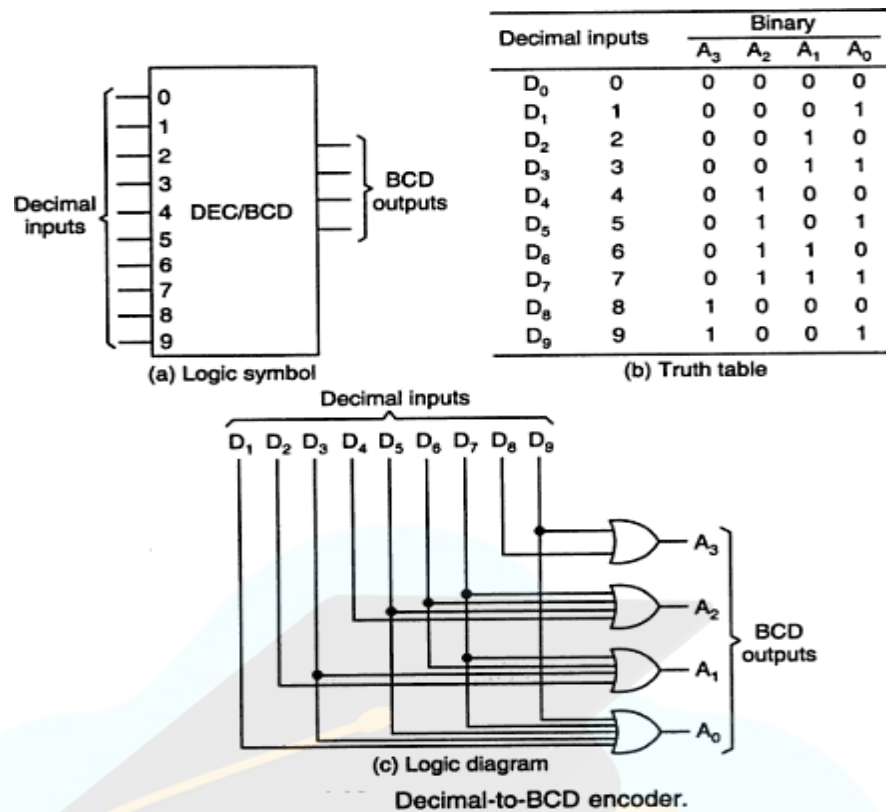


## Tristate bus system:

In digital electronics **three-state**, **tri-state**, or **3-state** logic allows an output port to assume a high impedance state in addition to the 0 and 1 logic levels, effectively removing the output from the circuit.

This allows multiple circuits to share the same output line or lines (such as a bus which cannot listen to more than one device at a time).

Three-state outputs are implemented in many registers, bus drivers, and flip-flops in the 7400 and 4000 series as well as in other types, but also internally in many integrated circuits. Other typical uses are internal and external buses in microprocessors, computer memory, and peripherals. Many devices are controlled by an active-low input called OE (Output Enable) which dictates whether the outputs should be held in a high-impedance state or drive their respective loads (to either 0- or 1-level).

 

INPUT		OUTPUT
A	B	C
0	1	0
1	1	1
X	0	Z (high impedance)

## UNIT-IV

### SEQUENTIAL CIRCUITS

#### The Basic Latch



- **Basic latch** is a feedback connection of two NOR gates or two NAND gates
- It can store one bit of information

It can be set to 1 using the  $S$  input and reset to 0 using the  $R$  input

#### The Gated Latch

- **Gated latch** is a basic latch that includes input gating and a control signal
- The latch retains its existing state when the control input is equal to 0
- Its state may be changed when the control signal is equal to 1. In our discussion we referred to the control input as the clock
- We consider two types of gated latches:
  - **Gated SR latch** uses the  $S$  and  $R$  inputs to set the latch to 1 or reset it to 0, respectively.
  - **Gated D latch** uses the  $D$  input to force the latch into a state that has the same logic value as the  $D$  input.

#### Gated S/R Latch

  


(c) Timing diagram



(d) Graphical symbol


## Gated D Latch

 


(a) Circuit

Clk	D	$Q(t+1)$
0	x	$Q(t)$
1	0	0
1	1	1

(b) Characteristic table

 

(c) Graphical symbol

 

(d) Timing diagram

## Setup and Hold Times

### ● Setup Time $t_{su}$

The minimum time that the input signal must be stable prior to the edge of the clock signal.

### ● Hold Time $t_h$



The minimum time that the input signal must be stable after the edge of the clock signal.

## Flip-Flops


- A **flip-flop** is a storage element based on the gated latch principle
- It can have its output state changed only on the edge of the controlling clock signal
- We consider two types:

- **Edge-triggered flip-flop** is affected only by the input values present when the active edge of the clock occurs
- **Master-slave flip-flop** is built with two gated latches
- The master stage is active during half of the clock cycle, and the slave stage is active during the other half.
- The output value of the flip-flop changes on the edge of the clock that activates the transfer into the slave stage.



### Master-Slave D Flip-Flop

  
 
### A Positive-Edge-Triggered D Flip-Flop



  
## Master-Slave D Flip-Flop with *Clear* and *Preset*




(a) Circuit

J	K	Q(t+1)
0	0	Q(t)
0	1	0
1	0	1
1	1	Q-bar(t)

 


(b) Characteristic table (c) Graphical symbol

## T Flip-Flop

 


(a) Circuit

T	Q(t+1)
0	Q(t)
1	Q-bar(t)

 

 (b) Characteristic table (c) Graphical symbol



(d) Timing diagram

## Excitation Tables

Previous State -> Present State	D
0 -> 0	0
0 -> 1	1
1 -> 0	0
1 -> 1	1

Previous State -> Present State	J	K
0 -> 0	0	X
0 -> 1	1	X
1 -> 0	X	1
1 -> 1	X	0

Previous State -> Present State	S	R
0 -> 0	0	X
0 -> 1	1	0
1 -> 0	0	1
1 -> 1	X	0

Previous State -> Present State	T
0 -> 0	0
0 -> 1	1
1 -> 0	1
1 -> 1	0

## Conversions of flip-flops

### Example: Use JK-FF to realize D-FF


- 1) Start transition table for D-FF
- 2) Create K-maps to express J and K as functions of inputs (D, Q)
- 3) Fill in K-maps with appropriate values for J and K to cause the same state transition as in the D-FF transition table

D	Q	Q <sup>+</sup>	J	K
0	0	0	0	X
0	1	0	X	1
1	0	1	1	X
1	1	1	X	0

State-Table



e.g.  
when D=Q=0, then Q<sup>+</sup>=0  
the same transition Q<sup>-</sup>→Q<sup>+</sup>  
is realized with J=0, K=X

Q	Q <sup>+</sup>	R	S	J	K	T	D
0	0	X	0	0	X	0	0
0	1	0	1	1	X	1	1
1	0	1	0	X	1	1	0
1	1	0	X	X	0	0	1

 


### Example: Implement JK-FF using a D-FF

J	K	Q	Q <sup>+</sup>	D	T
0	0	0	0	0	0
0	0	1	1	1	0
0	1	0	0	0	0
0	1	1	0	0	1
1	0	0	1	1	1
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	1

  

$$d = jQ + Kq$$

 

$$t = jQ + kq$$




## Sequential Circuit Design

- Steps in the design process for sequential circuits
- State Diagrams and State Tables □ Examples
- Steps in Design of a Sequential Circuit
  - 1. Specification – A description of the sequential circuit. Should include a detailing of the inputs, the outputs, and the operation. Possibly assumes that you have knowledge of digital system basics.
  - 2. Formulation: Generate a state diagram and/or a state table from the statement of the problem.
  - 3. State Assignment: From a state table assign binary codes to the states.
  - 4. Flip-flop Input Equation Generation: Select the type of flip-flop for the circuit and generate the needed input for the required state transitions
  - 5. Output Equation Generation: Derive output logic equations for generation of the output from the inputs and current state.
  - 6. Optimization: Optimize the input and output equations. Today, CAD systems are typically used for this in real systems.
  - 7. Technology Mapping: Generate a logic diagram of the circuit using ANDs, ORs, Inverters, and F/Fs.
  - 8. Verification: Use a HDL to verify the design

## Registers and Counters

- An  $n$ -bit register is a cascade of  $n$  flip-flops and can store an  $n$ -bit binary data
- A counter can count occurrences of events and can generate timing intervals for control purposes

## A Simple Shift Register

 


(a) Circuit

	In	Q <sub>1</sub>	Q <sub>2</sub>	Q <sub>3</sub>	Q <sub>4</sub> = Out
$t_0$	1	0	0	0	0
$t_1$	0	1	0	0	0
$t_2$	1	0	1	0	0
$t_3$	1	1	0	1	0
$t_4$	1	1	1	0	1
$t_5$	0	1	1	1	0
$t_6$	0	0	1	1	1
$t_7$	0	0	0	1	1

(b) A sample sequence

## Parallel-Access Shift Register

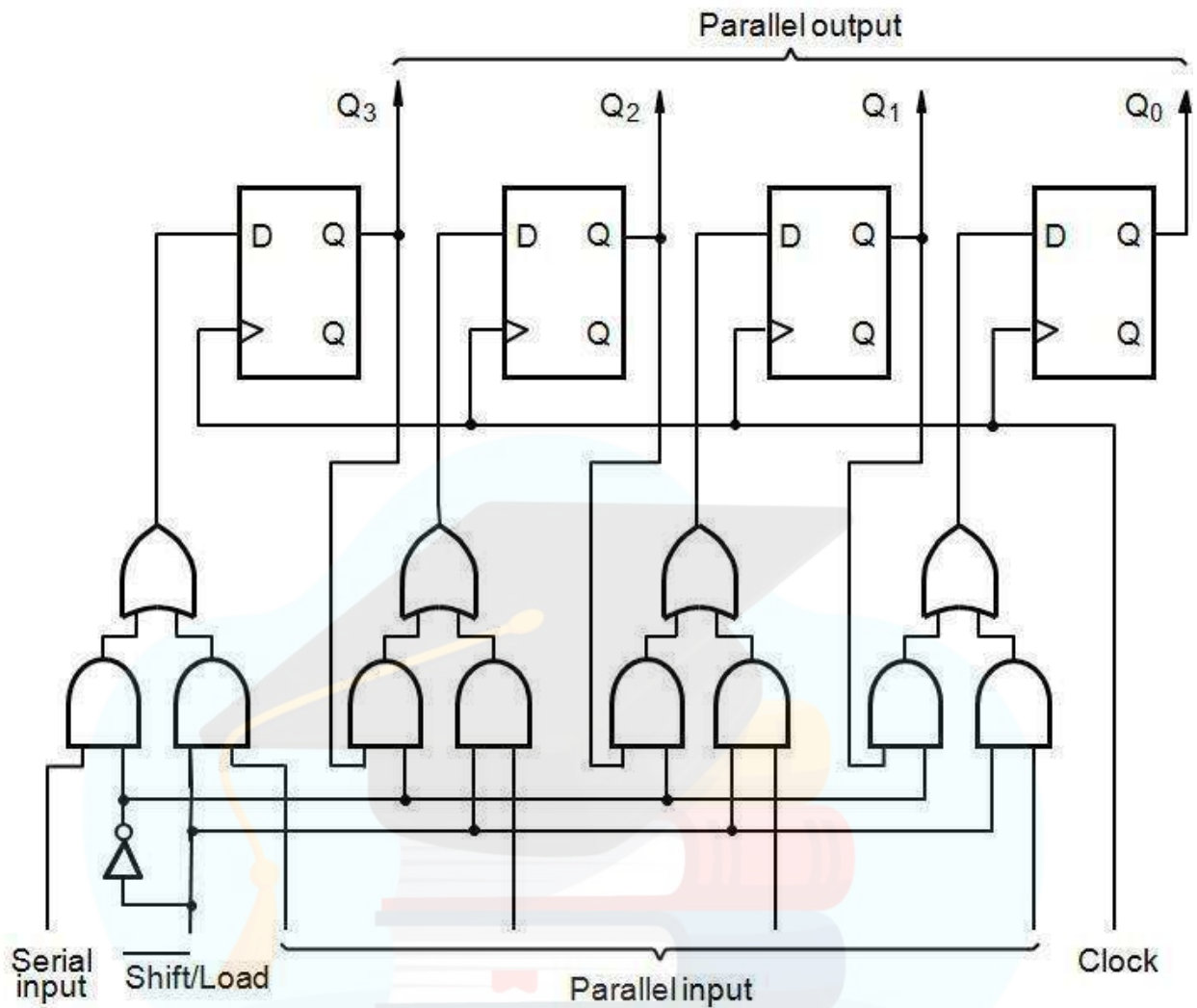

## Counters

- Counters are a specific type of sequential circuit.
- Like registers, the state, or the flip-flop values themselves, serves as the “output.”
- The output value increases by one on each clock cycle.
- After the largest value, the output “wraps around” back to 0.
- Using two bits, we’d get something like this:



Present State		Next State	
A	B	A	B
0	0	0	1
0	1	1	0
1	0	1	1
1	1	0	0

### Benefits of counters



- Counters can act as simple clocks to keep track of “time.” •  
 You may need to record how many times something has happened.
  - How many bits have been sent or received?
  - How many steps have been performed in some computation?
- All processors contain a program counter, or PC.
  - Programs consist of a list of instructions that are to be executed one after another (for the most part).
  - The PC keeps track of the instruction currently being executed.
  - The PC increments once on each clock cycle, and the next program instruction is then executed.
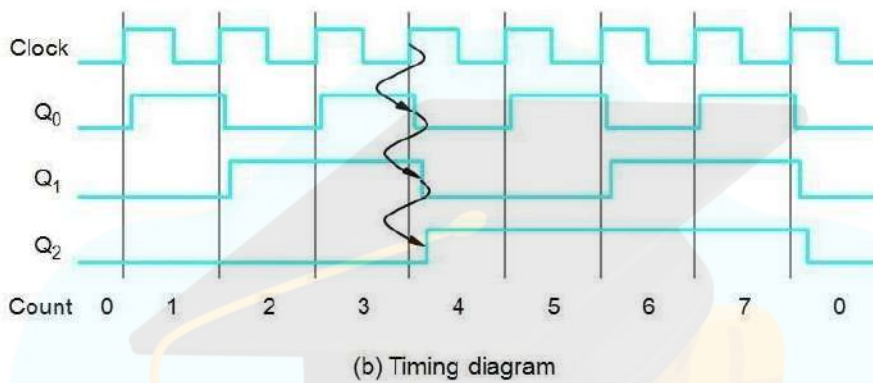 
### A Three-Bit Up-Counter

- $Q_1$  is connected to clk,  $Q_2$  and  $Q_3$  are clocked by  $Q'$  of the preceding stage (hence called asynchronous or ripple counter)



### A Three-Bit Down-Counter

  

### Shift registers:


In digital circuits, a **shift register** is a cascade of flip-flops sharing the same clock, in which the output of each flip-flop is connected to the "data" input of the next flip-flop in the chain, resulting in a circuit that shifts by one position the "bit array" stored in it, *shifting in* the data present at its input and *shifting out* the last bit in the array, at each transition of the clock input. More generally, a **shift register** may be multidimensional, such that its "data in" and stage outputs are themselves bit arrays: this is implemented simply by running several shift registers of the same bit-length in parallel.

Shift registers can have both parallel and serial inputs and outputs. These are often configured as **serial-in, parallel-out (SIPO)** or as **parallel-in, serial-out (PISO)**. There are also types that have both serial and parallel input and types with serial and parallel output. There are also **bi-directional** shift registers which allow shifting in both directions: L→R or R→L. The serial input and last output of a shift register can also be connected to create a **circular shift register**

Shift registers are a type of logic circuits closely related to counters. They are basically for the storage and transfer of digital data.

### Buffer register:

The buffer register is the simple set of registers. It simply stores the binary word. The buffer may be controlled buffer. Most of the buffer registers used D Flip-flops.

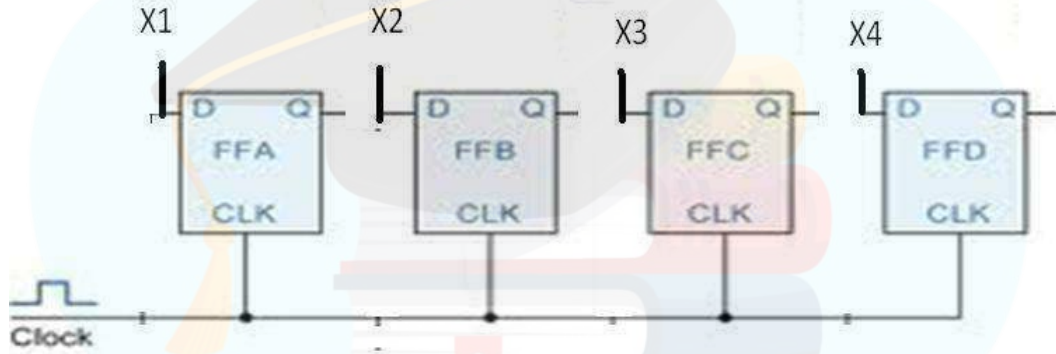

**Figure: logic diagram of 4-bit buffer register**

The figure shows a 4-bit buffer register. The binary word to be stored is applied to the data terminals. On the application of clock pulse, the output word becomes the same as the word applied at the terminals. i.e., the input word is loaded into the register by the application of clock pulse.

When the positive clock edge arrives, the stored word becomes:

$$Q_4Q_3Q_2Q_1 = X_4X_3X_2X_1$$
$$Q = X$$

### Controlled buffer register:


If goes LOW, all the FFs are RESET and the output becomes,  $Q = 0000$ .

When is HIGH, the register is ready for action. LOAD is the control input. When LOAD is HIGH, the data bits X can reach the D inputs of FF's.


$$Q_4Q_3Q_2Q_1 = X_4X_3X_2X_1$$
$$Q = X$$

→ when load is low, the ↓ bits cannot reach the FF's.


## Data transmission in shift registers:

 

 
Serial-in, serial-out shift register with 4-stages



 Parallel-in, parallel-out shift register with 4-stages



 Serial-in, parallel-out shift register with 4-stages




Parallel-in, serial-out shift register with 4-stages

A number of ff's connected together such that data may be shifted into and shifted out of them is called shift register. data may be shifted into or out of the register in serial form or in parallel form. There are four basic types of shift registers.

1. Serial in, serial out, shift right, shift registers
2. Serial in, serial out, shift left, shift registers
3. Parallel in, serial out shift registers
4. Parallel in, parallel out shift registers

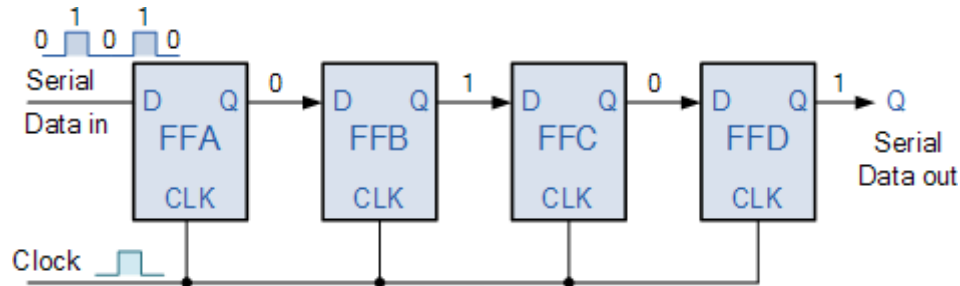
### Serial IN, serial OUT, shift right, shift left register:

The logic diagram of 4-bit serial in serial out, right shift register with four stages. The register can store four bits of data. Serial data is applied at the input D of the first FF. The Q output of the first FF is connected to the D input of another FF. The data is outputted from the Q terminal of the last FF.



When serial data is transferred into a register, each new bit is clocked into the first FF at the positive going edge of each clock pulse. The bit that was previously stored by the first FF is transferred to the second FF. The bit that was stored by the second FF is transferred to the third FF.

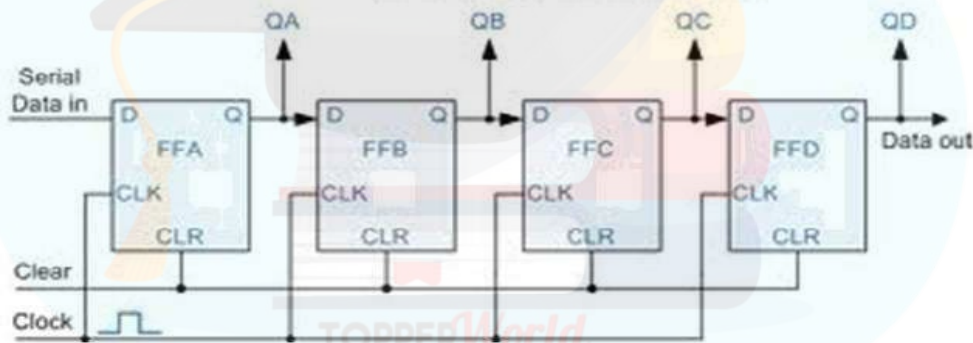
### Serial-in, parallel-out, shift register:



In this type of register, the data bits are entered into the register serially, but the data stored in the register is shifted out in parallel form.

Once the data bits are stored, each bit appears on its respective output line and all bits are available simultaneously, rather than on a bit-by-bit basis with the serial output. The serial-in, parallel out, shift register can be used as serial-in, serial out, shift register if the output is taken from the Q terminal of the last FF.

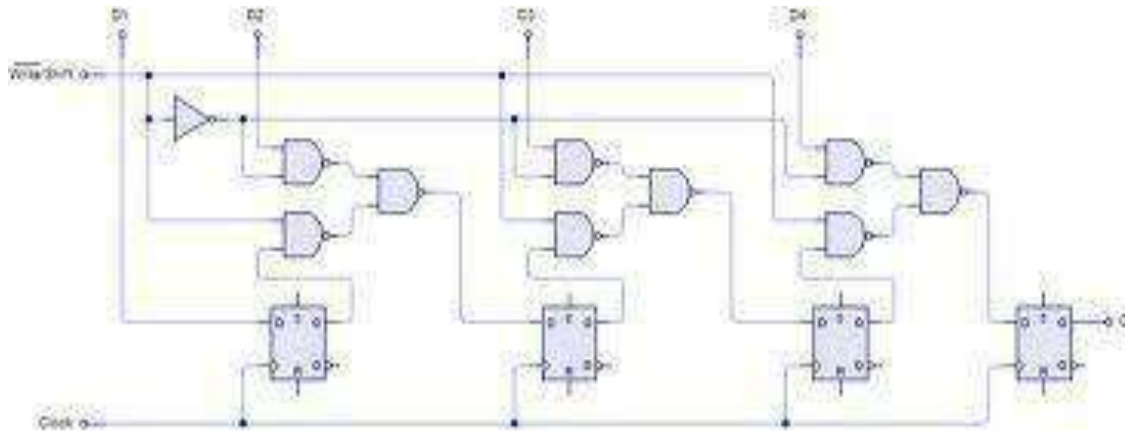
### Parallel-in, serial-out, shift register:



For a parallel-in, serial out, shift register, the data bits are entered simultaneously into their respective stages on parallel lines, rather than on a bit-by-bit basis on one line as with serial data bits are transferred out of the register serially. On a bit-by-bit basis over a single line.

There are four data lines A,B,C,D through which the data is entered into the register in parallel form. The signal shift/ load allows the data to be entered in parallel form into the register and the data is shifted out serially from terminal Q4
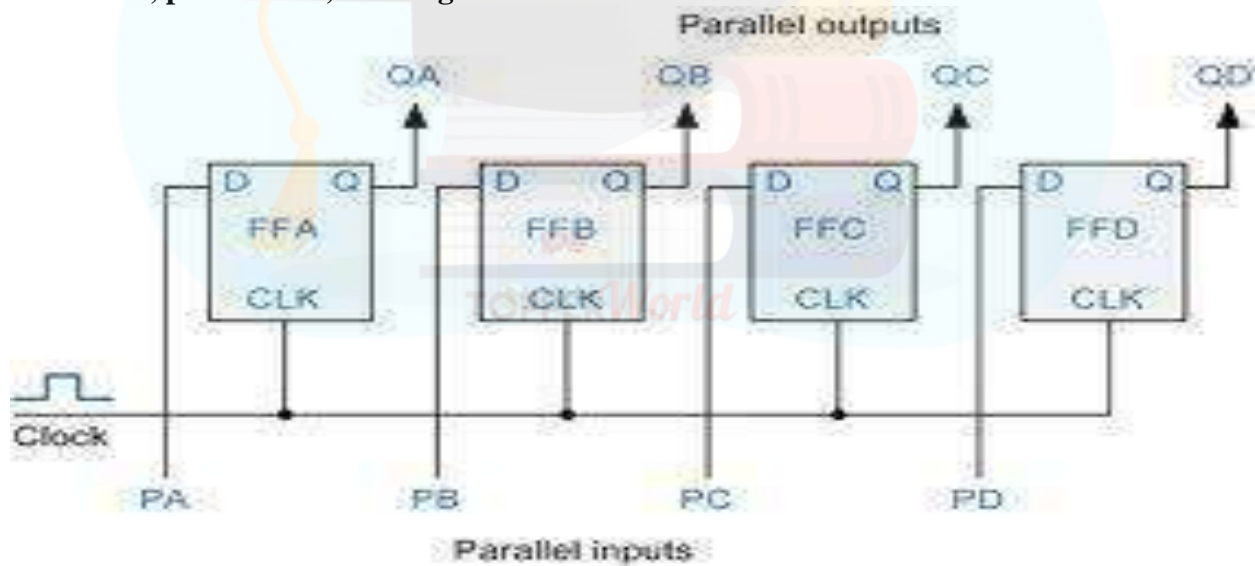
### Parallel-in, parallel-out, shift register



In a parallel-in, parallel-out shift register, the data is entered into the register in parallel form, and also the data is taken out of the register in parallel form. Data is applied to the D input terminals of the FF's. When a clock pulse is applied, at the positive going edge of the pulse, the D inputs are shifted into the Q outputs of the FFs. The register now stores the data. The stored data is available instantaneously for shifting out in parallel form.



### Bidirectional shift register:

A bidirectional shift register is one which the data bits can be shifted from left to right or from right to left. A fig shows the logic diagram of a 4-bit serial-in, serial out, bidirectional shift register. Right/left is the mode signal, when right /left is a 1, the logic circuit works as a shift-register. the bidirectional operation is achieved by using the mode signal and two NAND gates and one OR gate for each stage.

A HIGH on the right/left control input enables the AND gates G1, G2, G3 and G4 and disables the AND gates G5, G6, G7 and G8, and the state of Q output of each FF is passed through the gate to the D input of the following FF. when a clock pulse occurs, the data bits are then effectively shifted one place to the right. A LOW on the right/left control inputs enables the AND gates G5, G6, G7 and G8 and disables the And gates G1, G2, G3 and G4 and the Q output of each FF is passed to the D input of the preceding FF. when a clock pulse occurs, the data bits are then effectively shifted one place to the left. Hence, the circuit works as a bidirectional shift register

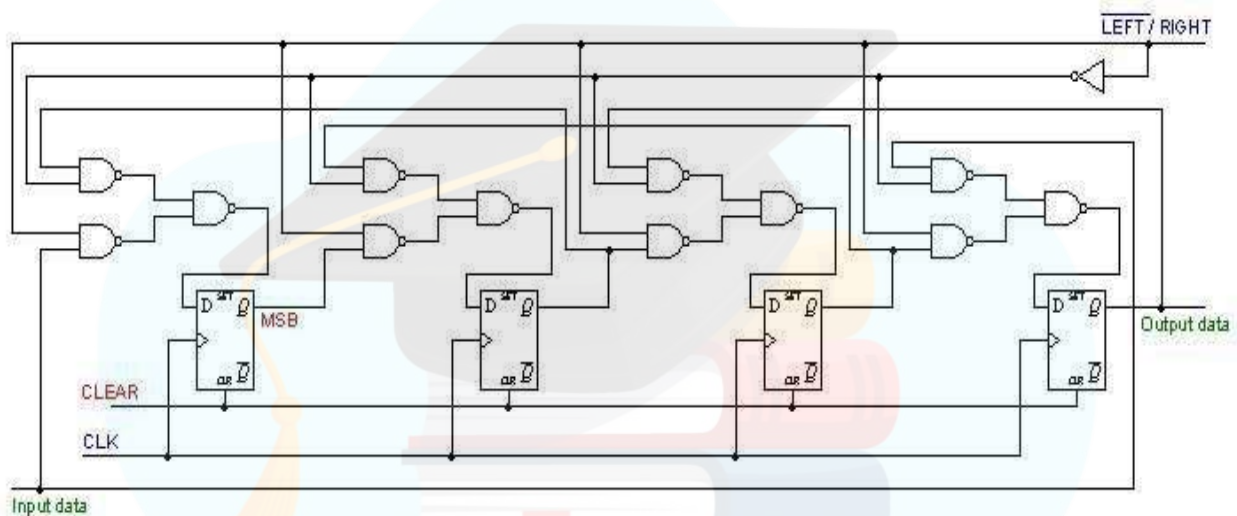


Figure: logic diagram of a 4-bit bidirectional shift register

### Universal shift register:

A register is capable of shifting in one direction only is a unidirectional shift register. One that can shift both directions is a bidirectional shift register. If the register has both shifts and parallel load capabilities, it is referred to as a universal shift registers. Universal shift register is a bidirectional register, whose input can be either in serial form or in parallel form and whose output also can be in serial form or I parallel form.

The most general shift register has the following capabilities.

1. A clear control to clear the register to 0
2. A clock input to synchronize the operations
3. A shift-right control to enable the shift-right operation and serial input and output lines associated with the shift-right

4. A shift-left control to enable the shift-left operation and serial input and output lines associated with the shift-left
5. A parallel loads control to enable a parallel transfer and the n input lines associated with the parallel transfer
6. N parallel output lines
7. A control state that leaves the information in the register unchanged in the presence of the clock.

A universal shift register can be realized using multiplexers. The below fig shows the logic diagram of a 4-bit universal shift register that has all capabilities. It consists of 4 D flip-flops and four multiplexers. The four multiplexers have two common selection inputs  $s_1$  and  $s_0$ . Input 0 in each multiplexer is selected when  $S_1S_0=00$ , input 1 is selected when  $S_1S_0=01$  and input 2 is selected when  $S_1S_0=10$  and input 4 is selected when  $S_1S_0=11$ . The selection inputs control the mode of operation of the register according to the functions entries. When  $S_1S_0=0$ , the present value of the register is applied to the D inputs of flip-flops. The condition forms a path from the output of each flip-flop into the input of the same flip-flop. The next clock edge transfers into each flip-flop the binary value it held previously, and no change of state occurs. When  $S_1S_0=01$ , terminal 1 of the multiplexer inputs have a path to the D inputs of the flip-flop. This causes a shift-right operation, with serial input transferred into flip-flop  $A_4$ . When  $S_1S_0=10$ , a shift left operation results with the other serial input going into flip-flop  $A_1$ . Finally when  $S_1S_0=11$ , the binary information on the parallel input lines is transferred into the register simultaneously during the next clock cycle

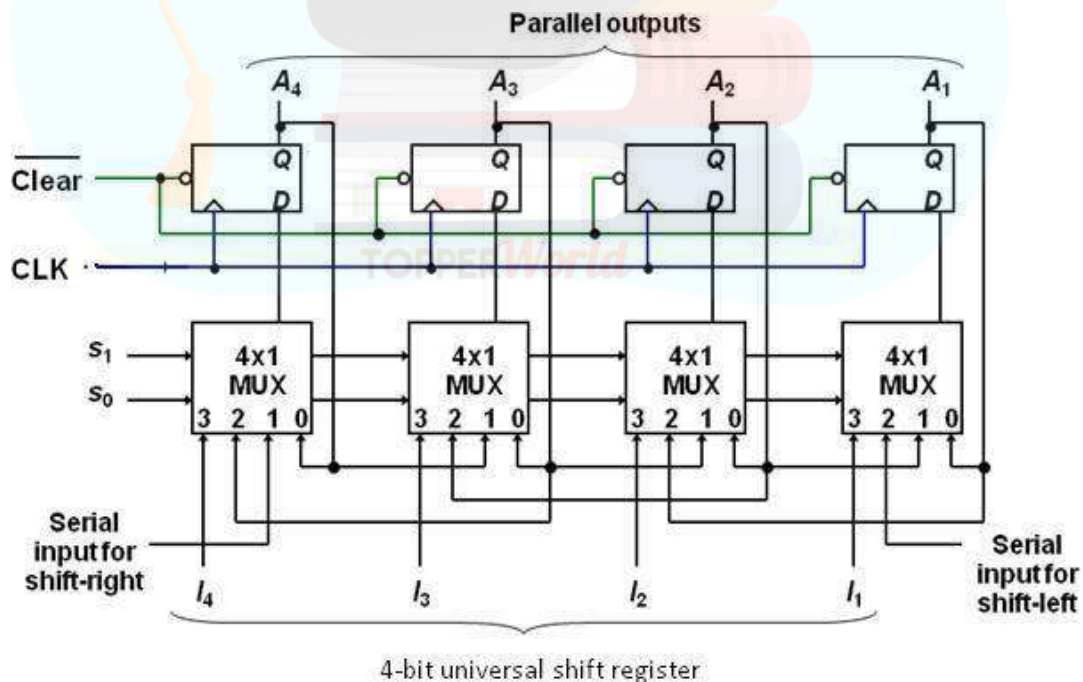


Figure: logic diagram 4-bit universal shift register

### Function table for the register

mode control		
S0	S1	register operation
0	0	No change
0	1	Shift Right
1	0	Shift left
1	1	Parallel load

### Counters:

**Counter** is a device which stores (and sometimes displays) the number of times particular event or process has occurred, often in relationship to a clock signal. A Digital counter is a set of flip flops whose state change in response to pulses applied at the input to the counter. Counters may be asynchronous counters or synchronous counters. Asynchronous counters are also called ripple counters

In electronics counters can be implemented quite easily using register-type circuits such as the flip-flops and a wide variety of classifications exist:

- Asynchronous (ripple) counter – changing state bits are used as clocks to subsequent state flip-flops
- Synchronous counter – all state bits change under control of a single clock
- Decade counter – counts through ten states per stage
- Up/down counter – counts both up and down, under command of a control input
- Ring counter – formed by a shift register with feedback connection in a ring
- Johnson counter – a *twisted* ring counter
- Cascaded counter
- Modulus counter.

Each is useful for different applications. Usually, counter circuits are digital in nature, and count in natural binary. Many types of counter circuits are available as digital building blocks, for example a number of chips in the 4000 series implement different counters.

Occasionally there are advantages to using a counting sequence other than the natural binary sequence such as the binary coded decimal counter, a linear feed-back shift register counter, or a gray-code counter.

Counters are useful for digital clocks and timers, and in oven timers, VCR clocks, etc.


## Asynchronous counters:


An asynchronous (ripple) counter is a single [JK-type flip-flop](#), with its J (data) input fed from its own inverted output. This circuit can store one bit, and hence can count from zero to one before it overflows (starts over from 0). This counter will increment once for every clock cycle and takes two clock cycles to overflow, so every cycle it will alternate between a transition from 0 to 1 and a transition from 1 to 0. Notice that this creates a new clock with a 50% [duty cycle](#) at exactly half the frequency of the input clock. If this output is then used as the clock signal for a similarly arranged D flip-flop (remembering to invert the output to the input), one will get another 1 bit counter that counts half as fast. Putting them together yields a two-bit counter:
 
### Two-bit ripple up-counter using negative edge triggered flip flop:


Two bit ripple counter used two flip-flops. There are four possible states from 2 – bit up-counting I.e. 00, 01, 10 and 11.

- The counter is initially assumed to be at a state 00 where the outputs of the two flip-flops are noted as  $Q_1Q_0$ . Where  $Q_1$  forms the MSB and  $Q_0$  forms the LSB.
- For the negative edge of the first clock pulse, output of the first flip-flop  $FF_1$  toggles its state. Thus  $Q_1$  remains at 0 and  $Q_0$  toggles to 1 and the counter state are now read as 01.
- During the next negative edge of the input clock pulse  $FF_1$  toggles and  $Q_0 = 0$ . The output  $Q_0$  being a clock signal for the second flip-flop  $FF_2$  and the present transition acts as a negative edge for  $FF_2$  thus toggles its state  $Q_1 = 1$ . The counter state is now read as 10.
- For the next negative edge of the input clock to  $FF_1$  output  $Q_0$  toggles to 1. But this transition from 0 to 1 being a positive edge for  $FF_2$  output  $Q_1$  remains at 1. The counter state is now read as 11.
- For the next negative edge of the input clock,  $Q_0$  toggles to 0. This transition from 1 to 0 acts as a negative edge clock for  $FF_2$  and its output  $Q_1$  toggles to 0. Thus the starting state 00 is attained. Figure shown below



 

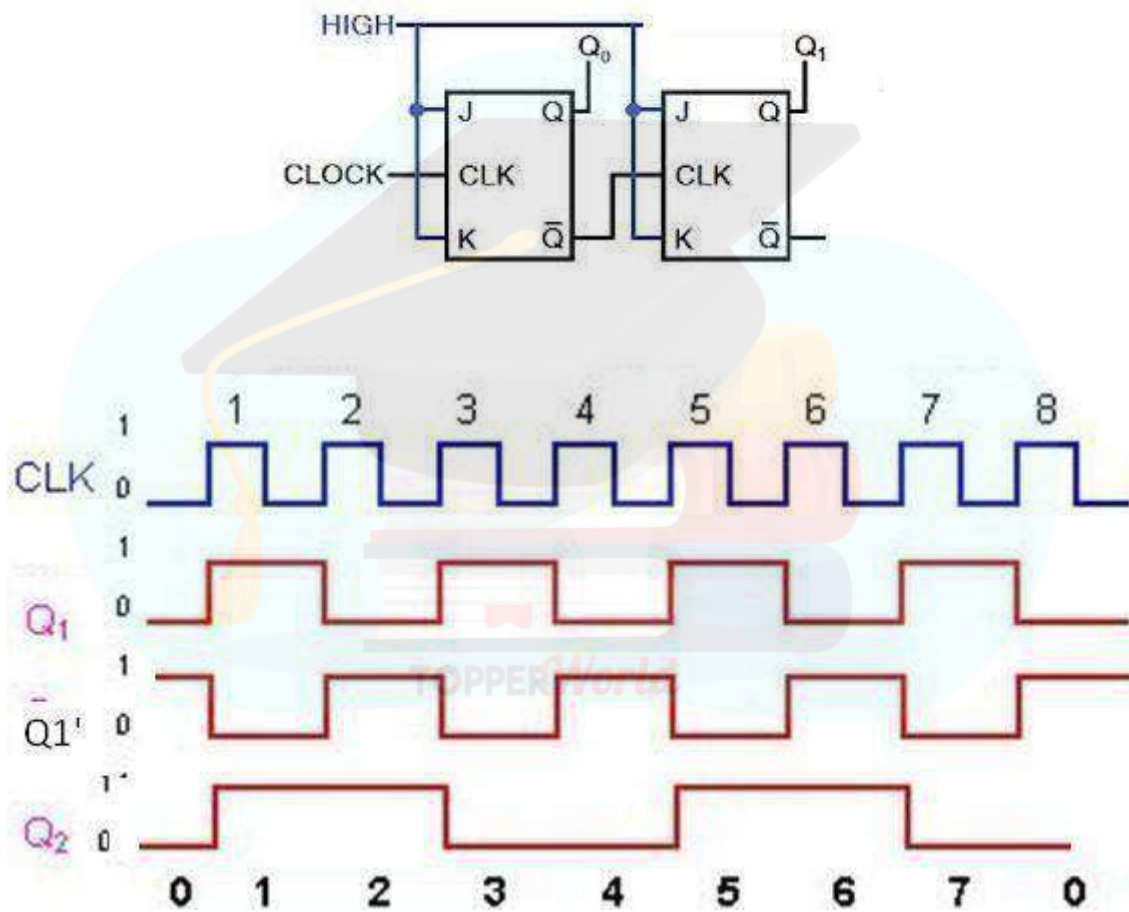Two-bit ripple down-counter using negative edge triggered flip flop:




A 2-bit down-counter counts in the order 0,3,2,1,0,1.....,i.e, 00,11,10,01,00,11 .....etc. the above fig. shows ripple down counter, using negative edge triggered J-K FFs and its timing diagram.

- For down counting, Q<sub>1</sub>' of FF1 is connected to the clock of Ff2. Let initially all the FF1 toggles, so, Q<sub>1</sub> goes from a 0 to a 1 and Q<sub>1</sub>' goes from a 1 to a 0.

- The negative-going signal at  $Q_1'$  is applied to the clock input of FF2, toggles FF2 and, therefore,  $Q_2$  goes from a 0 to a 1. so, after one clock pulse  $Q_2=1$  and  $Q_1=1$ , I.e., the state of the counter is 11.
- At the negative-going edge of the second clock pulse,  $Q_1$  changes from a 1 to a 0 and  $Q_1'$  from a 0 to a 1.
- This positive-going signal at  $Q_1'$  does not affect FF2 and, therefore,  $Q_2$  remains at a 1. Hence, the state of the counter after second clock pulse is 10
- At the negative going edge of the third clock pulse, FF1 toggles. So  $Q_1$ , goes from a 0 to a 1 and  $Q_1'$  from 1 to 0. This negative going signal at  $Q_1'$  toggles FF2 and, so,  $Q_2$  changes from 1 to 0, hence, the state of the counter after the third clock pulse is 01.
- At the negative going edge of the fourth clock pulse, FF1 toggles. So  $Q_1$ , goes from a 1 to a 0 and  $Q_1'$  from 0 to 1. . This positive going signal at  $Q_1'$  does not affect FF2 and, so,  $Q_2$  remains at 0, hence, the state of the counter after the fourth clock pulse is 00.

#### Two-bit ripple up-down counter using negative edge triggered flip flop:

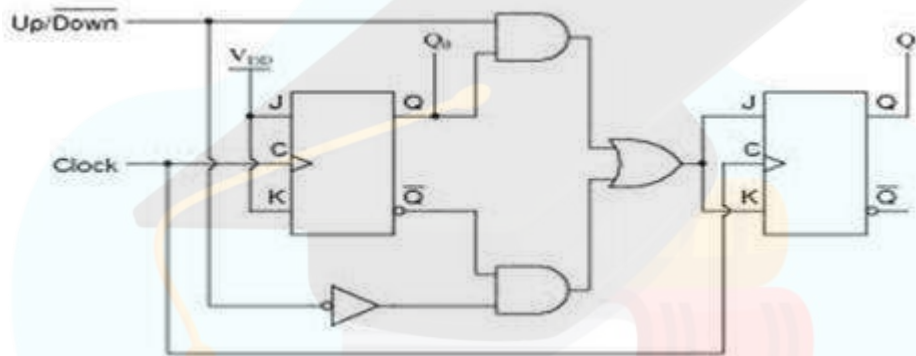

**Figure: asynchronous 2-bit ripple up-down counter using negative edge triggered flip flop:**



- As the name indicates an up-down counter is a counter which can count both in upward and downward directions. An up-down counter is also called a forward/backward counter or a bidirectional counter. So, a control signal or a mode signal  $M$  is required to choose the direction of count. When  $M=1$  for up counting,  $Q_1$  is transmitted to clock of FF2 and when  $M=0$  for down counting,  $Q_1'$  is transmitted to clock of FF2. This is achieved by using two AND gates and one OR gates. The external clock signal is applied to FF1.
- Clock signal to FF2 =  $(Q_1 \cdot \text{Up}) + (Q_1' \cdot \text{Down}) = Q_1 M + Q_1' M'$

#### Design of Asynchronous counters:

To design a asynchronous counter, first we write the sequence, then tabulate the values of reset signal  $R$  for various states of the counter and obtain the minimal expression for  $R$  and  $R'$  using K-Map or any other method. Provide a feedback such that  $R$  and  $R'$  resets all the FF's after the desired count
 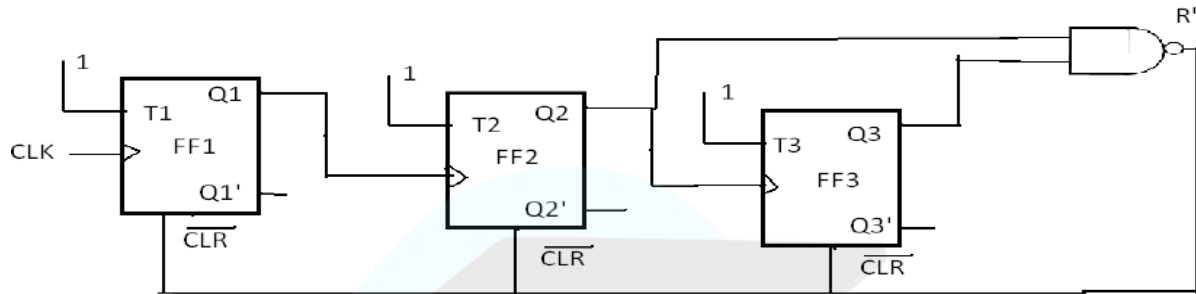
### Design of a Mod-6 asynchronous counter using T FFs:

A mod-6 counter has six stable states 000, 001, 010, 011, 100, and 101. When the sixth clock pulse is applied, the counter temporarily goes to 110 state, but immediately resets to 000 because of the feedback provided. It is a divide-by-6 counter, in the sense that it divides the input clock frequency by 6. It requires three FFs, because the smallest value of  $n$  satisfying the condition  $N \leq 2^n$  is  $n=3$ ; three FFs can have 8 possible states, out of which only six are utilized and the remaining two states 110 and 111, are invalid. If initially the counter is in 000 state, then after the sixth clock pulse, it goes to 001, after the second clock pulse, it goes to 010, and so on.



After sixth clock pulse it goes to 000. For the design, write the truth table with present state outputs  $Q_3$ ,  $Q_2$  and  $Q_1$  as the variables, and reset  $R$  as the output and obtain an expression for  $R$  in terms of  $Q_3$ ,  $Q_2$ , and  $Q_1$  that decides the feedback into to be provided. From the truth table,  $R = Q_3Q_2$ . For active-low Reset,  $R'$  is used. The reset pulse is of very short duration, of the order of nanoseconds and it is equal to the propagation delay time of the NAND gate used. The expression for  $R$  can also be determined as follows.

$$R=0 \text{ for } 000 \text{ to } 101, R=1 \text{ for } 110, \text{ and } R=X \text{ for } 111$$

Therefore,

$$R = Q_3Q_2Q_1' + Q_3Q_2Q_1 = Q_3Q_2$$


The logic diagram and timing diagram of Mod-6 counter is shown in the above fig.

The truth table is as shown in below.

After pulses	States			
	Q3	Q2	Q1	R
0	0	0	0	0
1	0	0	1	0
2	0	1	0	0
3	0	1	1	0
4	1	0	0	0
5	1	0	1	0
6	1	1	0	1
	↓	↓	↓	
	0	0	0	0
7	0	0	0	0
 
### Design of a mod-10 asynchronous counter using T-flip-flops:

A mod-10 counter is a decade counter. It is also called a BCD counter or a divide-by-10 counter. It requires four flip-flops (condition  $10 \leq 2^n$  is  $n=4$ ). So, there are 16 possible states, out of which ten are valid and remaining six are invalid. The counter has ten stable states, 0000 through 1001, i.e., it counts from 0 to 9. The initial state is 0000 and after nine clock pulses it goes to 1001. When the tenth clock pulse is applied, the counter goes to state 1010 temporarily, but because of the feedback provided, it resets to initial state 0000. So, there will be a glitch in the waveform of Q2. The state 1010 is a temporary state for which the reset signal  $R=1$ ,  $R=0$  for 0000 to 1001, and  $R=C$  for 1011 to 1111.



The count table and the K-Map for reset are shown in fig. from the K-Map  $R=Q4Q2$ . So, feedback is provided from second and fourth FFs. For active-HIGH reset,  $Q4Q2$  is applied to the clear terminal. For active-LOW reset  $\overline{Q4Q2}$  is connected to all flip-flops.




		Q2Q1			
		00	01	11	10
Q4Q3	00				
	01				
	11	X	X	X	X
	10		X	X	1

After pulses	Count			
	Q4	Q3	Q2	Q1
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	0	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	0	1	0	1
10	0	0	0	0
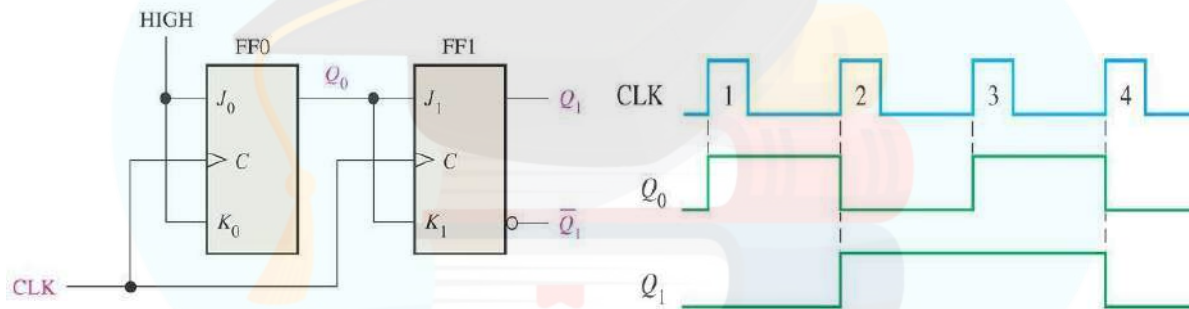
### Synchronous counters:

Asynchronous counters are serial counters. They are slow because each FF can change state only if all the preceding FFs have changed their state. If the clock frequency is very high, the asynchronous counter may skip some of the states. This problem is overcome in synchronous counters or parallel counters. Synchronous counters are counters in which all the flip-flops are triggered simultaneously by the clock pulses. Synchronous counters have a common clock pulse applied simultaneously to all flip-flops. □ A 2-Bit Synchronous Binary Counter



### Design of synchronous counters: TOPPERWorld

For a systematic design of synchronous counters. The following procedure is used.

**Step 1:** State Diagram: draw the state diagram showing all the possible states state diagram which also be called nth transition diagrams, is a graphical means of depicting the sequence of states through which the counter progresses.

**Step 2:** number of flip-flops: based on the description of the problem, determine the required number n of the flip-flops- the smallest value of n is such that the number of states  $N \leq 2^n$ --- and the desired counting sequence.

**Step 3:** choice of flip-flops excitation table: select the type of flip-flop to be used and write the excitation table. An excitation table is a table that lists the present state (ps) , the next state(ns) and required excitations.

**Step4:** minimal expressions for excitations: obtain the minimal expressions for the excitations of the FF using K-maps drawn for the excitation of the flip-flops in terms of the present states and inputs.

**Step5:** logic diagram: draw a logic diagram based on the minimal expressions

**Design of a synchronous 3-bit up-down counter using JK flip-flops:**

**Step1:** determine the number of flip-flops required. A 3-bit counter requires three FFs. It has 8 states (000,001,010,011,101,110,111) and all the states are valid. Hence no don't cares. For selecting up and down modes, a control or mode signal M is required. When the mode signal M=1 and counts down when M=0. The clock signal is applied to all the FFs simultaneously.

**Step2:** draw the state diagrams: the state diagram of the 3-bit up-down counter is drawn as


**Step3:** select the type of flip flop and draw the excitation table: JK flip-flops are selected and the excitation table of a 3-bit up-down counter using JK flip-flops is drawn as shown in fig.

PS			mode	NS			required excitations					
Q3	Q2	Q1	M	Q3	Q2	Q1	J3	K3	J2	K2	J1	K1
0	0	0	0	1	1	1	1	x	1	x	1	x
0	0	0	1	0	0	1	0	x	0	x	1	x
0	0	1	0	0	0	0	0	x	0	x	x	1
0	0	1	1	0	1	0	0	x	1	x	x	1
0	1	0	0	0	0	1	0	x	x	1	1	x
0	1	0	1	0	1	1	0	x	x	0	1	x
0	1	1	0	0	1	0	0	x	x	0	x	1
0	1	1	1	1	0	0	1	x	x	1	x	1
1	0	0	0	0	1	1	x	1	1	x	1	x
1	0	0	1	1	0	1	x	0	0	x	1	x
1	0	1	0	1	0	0	x	0	0	x	x	1
1	0	1	1	1	1	0	x	0	1	x	x	1
1	1	0	0	1	0	1	x	0	x	1	1	x
1	1	0	1	1	1	1	x	0	x	0	1	x
1	1	1	0	1	1	0	x	0	x	0	x	1
1	1	1	1	0	0	0	x	1	x	1	x	1

**Step4:** obtain the minimal expressions: From the excitation table we can conclude that J1=1 and K1=1, because all the entries for J1 and K1 are either X or 1. The K-maps for J3, K3, J2 and K2 based on the excitation table and the minimal expression obtained from them are shown in fig.

	00	01	11	10
Q3Q2	1			
Q1M			1	
	X	X	X	X
	X	X	X	X

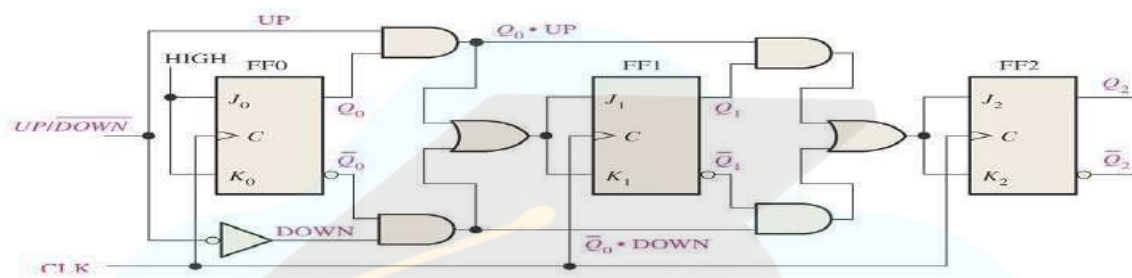
**Step5:** draw the logic diagram: a logic diagram using those minimal expressions can be drawn as shown in fig.


 
### Design of a synchronous modulo-6 gray cod counter:

**Step 1:** the number of flip-flops: we know that the counting sequence for a modulo-6 gray code counter is 000, 001, 011, 010, 110, and 111. It requires  $n=3$  FFs ( $N \leq 2^n$ , i.e.,  $6 \leq 2^3$ ). 3 FFs can have 8 states. So the remaining two states 101 and 100 are invalid. The entries for excitation corresponding to invalid states are don't cares.


**Step2:** the state diagram: the state diagram of the mod-6 gray code converter is drawn as shown in fig.




**Step3:** type of flip-flop and the excitation table: T flip-flops are selected and the excitation table of the mod-6 gray code counter using T-flip-flops is written as shown in fig.

PS			NS			required excitations		
Q3	Q2	Q1	Q3	Q2	Q1	T3	T2	T1
0	0	0	0	0	1	0	0	1
0	0	1	0	1	1	0	1	0
0	1	1	0	1	0	0	0	1
0	1	0	1	1	0	1	0	0
1	1	0	1	1	1	0	0	1
1	1	1	0	0	0	1	1	1

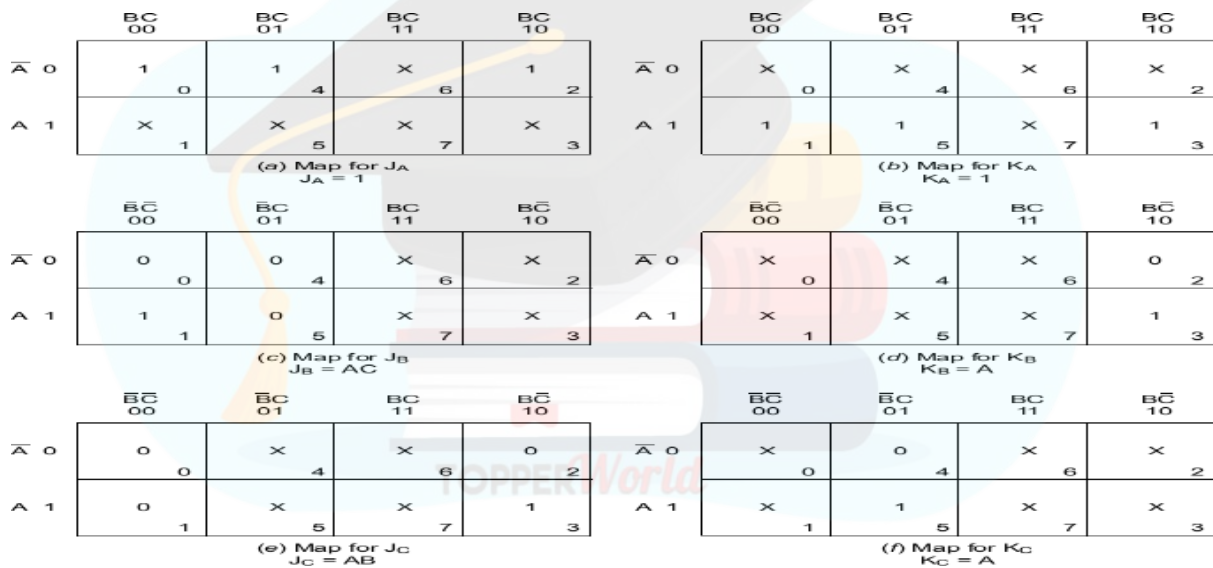**Step4:** The minimal expressions: the K-maps for excitations of FFs T3,T2,and T1 in terms of outputs of FFs Q3,Q2, and Q1, their minimization and the minimal expressions for excitations obtained from them are shown if fig



 **Step5:** the logic diagram: the logic diagram based on those minimal expressions is drawn as shown in fig.



### Design of a synchronous BCD Up-Down counter using FFs:

**Step1:** the number of flip-flops: a BCD counter is a mod-10 counter has 10 states (0000 through 1001) and so it requires  $n=4\text{FFs}(N \leq 2^n, \text{ i.e., } 10 \leq 2^4)$ . 4 FFS can have 16 states. So out of 16 states, six states (1010 through 1111) are invalid. For selecting up and down mode, a control or mode signal M is required. , it counts up when  $M=1$  and counts down when  $M=0$ . The clock signal is applied to all FFs.

**Step2:** the state diagram: The state diagram of the mod-10 up-down counter is drawn as shown in fig.

**Step3:** types of flip-flops and excitation table: T flip-flops are selected and the excitation table of the modulo-10 up down counter using T flip-flops is drawn as shown in fig.

The remaining minterms are don't cares ( $\sum d(20,21,22,23,24,25,26,27,28,29,30,31)$ ) from the excitation table we can see that  $T1=1$  and the expression for  $T4, T3, T2$  are as follows.

$$T4 = \sum m(0,15,16,19) + d(20,21,22,23,24,25,26,27,28,29,30,31)$$

$$T3 = \sum m(7,15,16,8) + d(20,21,22,23,24,25,26,27,28,29,30,31)$$


$$T2 = \sum m(3,4,7,8,11,12,15,16) + d(20,21,22,23,24,25,26,27,28,29,30,31)$$

PS				mode	NS				required excitations			
Q4	Q3	Q2	Q1		Q4	Q3	Q2	Q1	T4	T3	T2	T1
0	0	0	0	0	1	0	0	1	1	0	0	1
0	0	0	0	1	0	0	0	1	0	0	0	1
0	0	0	1	0	0	0	0	0	0	0	0	1
0	0	0	1	1	0	0	1	0	0	0	1	1
0	0	1	0	0	0	0	0	1	0	0	1	1
0	0	1	0	1	0	0	1	1	0	0	0	1
0	0	1	1	0	0	0	1	0	0	0	0	1
0	0	1	1	1	0	1	0	0	0	1	1	1
0	1	0	0	0	0	0	1	1	0	1	1	1
0	1	0	0	1	0	1	0	1	0	0	0	1
0	1	0	1	0	0	1	0	0	0	0	0	1
0	1	0	1	1	0	1	1	0	0	0	1	1
0	1	1	0	0	0	1	0	1	0	0	1	1
0	1	1	0	1	0	1	1	1	0	0	0	1
0	1	1	1	0	0	1	1	0	0	0	0	1
0	1	1	1	1	1	0	0	0	1	1	1	1
1	0	0	0	0	0	1	1	1	1	1	1	1
1	0	0	0	1	1	0	0	1	0	0	0	1
1	0	0	1	0	1	0	0	0	0	0	0	1
1	0	0	1	1	0	0	0	0	1	0	0	1

**Step4:** The minimal expression: since there are 4 state variables and a mode signal, we require 5 variable kmaps. 20 conditions of  $Q_4Q_3Q_2Q_1M$  are valid and the remaining 12 combinations are invalid. So the entries for excitations corresponding to those invalid combinations are don't cares. Minimizing K-maps for T2 we get

$$T_2 = Q_4Q_1'M + Q_4'Q_1M + Q_2Q_1'M' + Q_3Q_1'M'$$

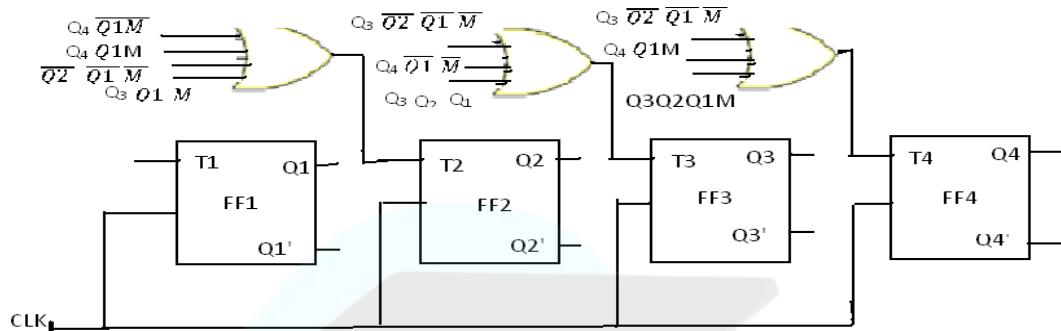
**Step5:** the logic diagram: the logic diagram based on the above equation is shown in fig.



### Shift register counters:

One of the applications of shift register is that they can be arranged to form several types of counters. The most widely used shift register counter is ring counter as well as the twisted ring counter.

**Ring counter:** this is the simplest shift register counter. The basic ring counter using D flip-flops is shown in fig. the realization of this counter using JK FFs. The Q output of each stage is connected to the D flip-flop connected back to the ring counter.

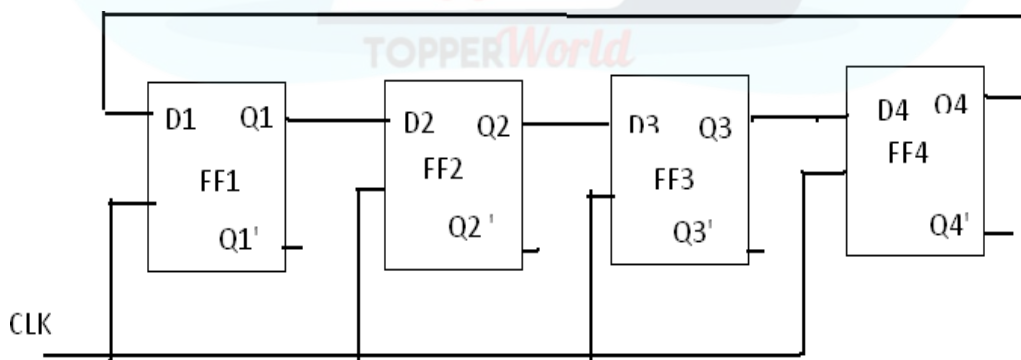


**FIGURE: logic diagram of 4-bit ring counter using D flip-flops**

 Only a single 1 is in the register and is made to circulate around the register as long as clock pulses are applied. Initially the first FF is present to a 1. So, the initial state is 1000, i.e.,  $Q_1=1, Q_2=0, Q_3=0, Q_4=0$ . After each clock pulse, the contents of the register are shifted to the right by one bit and  $Q_4$  is shifted back to  $Q_1$ . The sequence repeats after four clock pulses. The number

of distinct states in the ring counter, i.e., the mod of the ring counter is equal to number of FFs used in the counter. An n-bit ring counter can count only n bits, whereas n-bit ripple counter can count  $2^n$  bits. So, the ring counter is uneconomical compared to a ripple counter but has advantage of requiring no decoder, since we can read the count by simply noting which FF is set. Since it is entirely a synchronous operation and requires no gates external FFs, it has the further advantage of being very fast.

**Timing diagram:**



**Twisted Ring counter (Johnson counter):**

This counter is obtained from a serial-in, serial-out shift register by providing feedback from the inverted output of the last FF to the D input of the first FF. The Q output of each is connected to the D input of the next stage, but the Q' output of the last stage is connected to the D input of the first stage, therefore, the name twisted ring counter. This feedback arrangement produces a unique sequence of states.

The logic diagram of a 4-bit Johnson counter using D FF is shown in fig. the realization of the same using J-K FFs is shown in fig.. The state diagram and the sequence table are shown in figure. The timing diagram of a Johnson counter is shown in figure.

Let initially all the FFs be reset, i.e., the state of the counter be 0000. After each clock pulse, the level of Q1 is shifted to Q2, the level of Q2 to Q3, Q3 to Q4 and the level of Q4' to Q1 and the sequences given in fig.

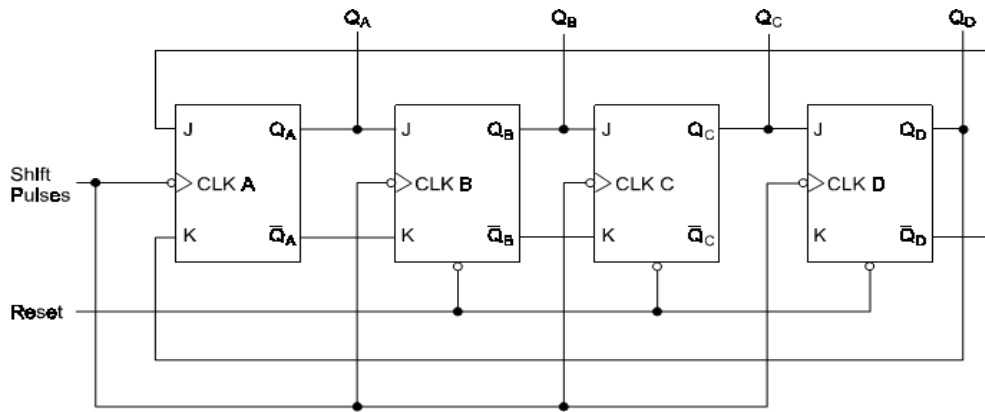


Figure: Johnson counter with JK flip-flops

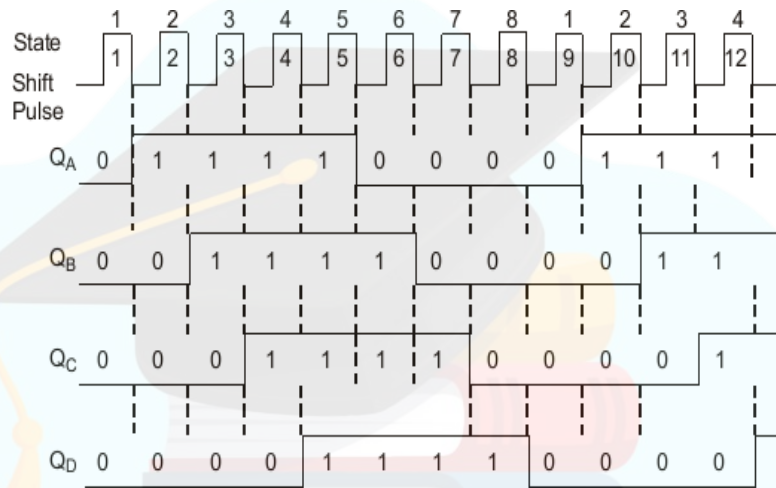


Figure: timing diagram

TOPPERWorld



## UNIT- V

### MEMORY

Memory structures are crucial in digital design. – ROM, PROM, EPROM, RAM, SRAM, (S)DRAM, RDRAM,...

- All memory structures have an address bus and a data bus – Possibly other control signals to control output etc. •E.g. 4 Bit Address bus with 5 Bit Data Bus ADDR DOUT
- There are two types of memories that are used in digital systems:
  - Random-access memory(RAM): perform both the write and read operations.
  - Read-only memory(ROM): perform only the readoperation.
- The read-only memory is a programmable logic device. Other such units are the programmable logic array(PLA), the programmable array logic(PAL), and the field-programmable gatearray(FPGA).

#### Random-Access Memory:

- A memory unit stores binary information in groups of bits called words.
  - byte = 8 bits
  - word = 2 bytes
- The communication between a memory and its environment is achieved through data input and output lines, address selection lines, and control lines that specify the direction of transfer.

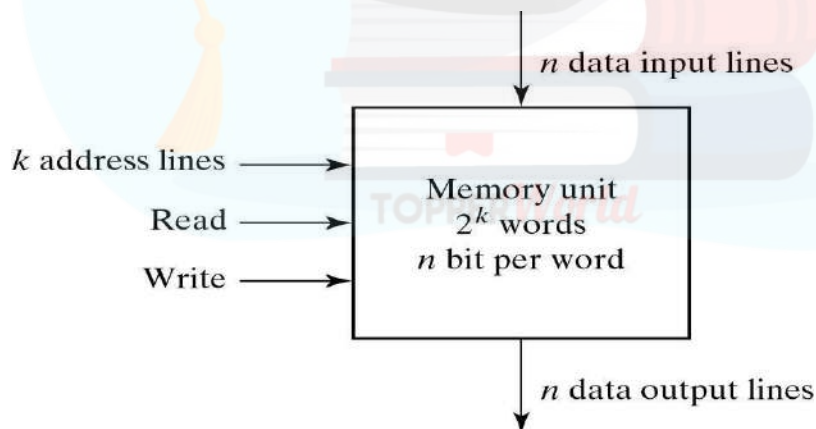


Fig. 7-2 Block Diagram of a Memory Unit

- In random-access memory, the word locations may be thought of as being separated in space, with each word occupying one particular location.
- In sequential-access memory, the information stored in some medium is not immediately accessible, but is available only certain intervals of time. A magnetic disk or tape unit is of this type.
- In a random-access memory, the access time is always the same regardless of the particular location of the word.


- ❑ In a sequential-access memory, the time it takes to access a word depends on the position of the word with respect to the reading head position; therefore, the access time is variable.

## **Static RAM**


- ❑ SRAM consists essentially of internal latches that store the binary information.
- ❑ The stored information remains valid as long as power is applied to the unit.
- ❑ SRAM is easier to use and has shorter read and write cycles.
- ❑ Low density, low capacity, high cost, high speed, high power consumption.
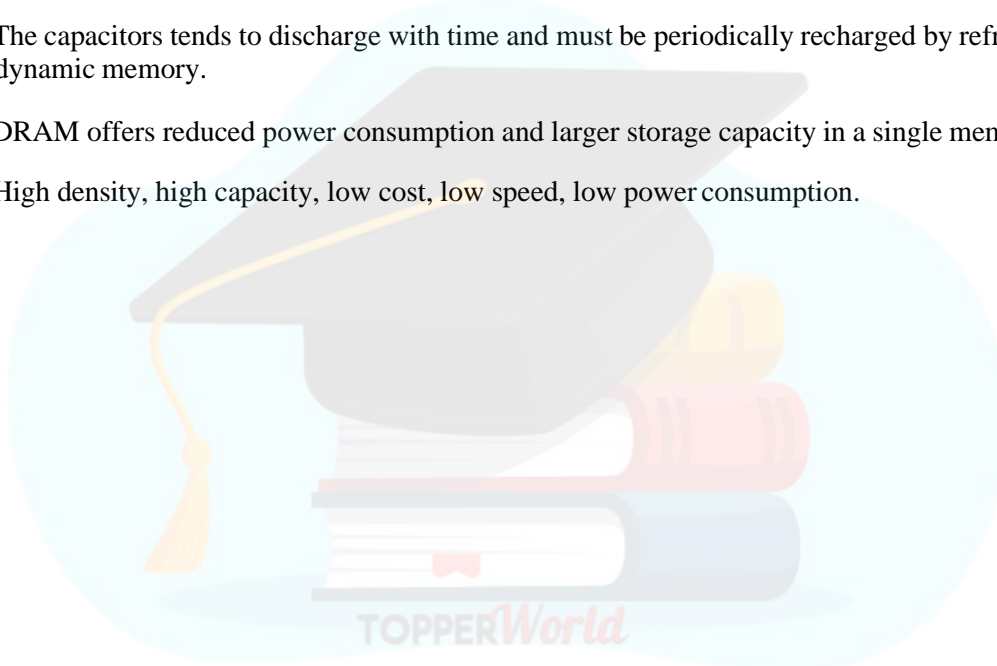
## **Dynamic RAM**

- ❑ DRAM stores the binary information in the form of electric charges on capacitors.
- ❑ The capacitors are provided inside the chip by MOS transistors.
- ❑ The capacitors tend to discharge with time and must be periodically recharged by refreshing the dynamic memory.
- ❑ DRAM offers reduced power consumption and larger storage capacity in a single memory chip.
- ❑ High density, high capacity, low cost, low speed, low power consumption.



MEMORY DECODING:

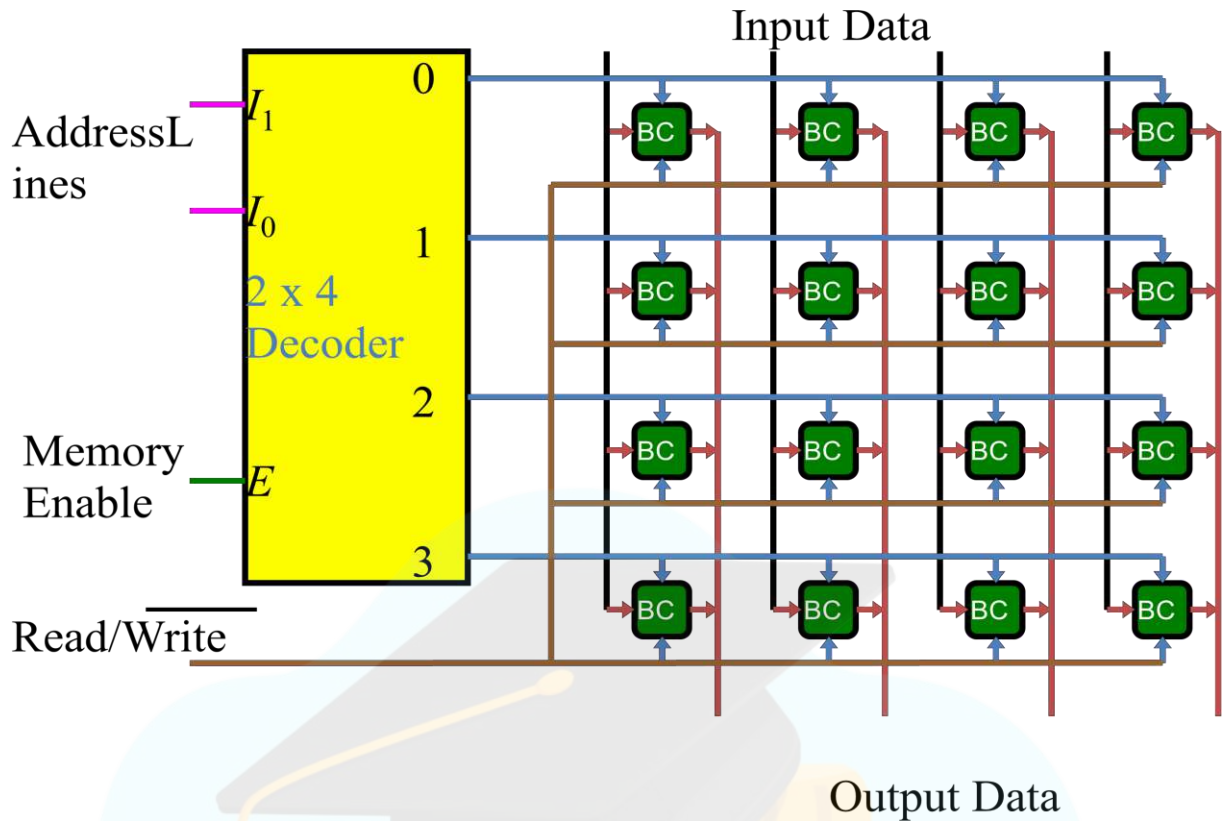

- The equivalent logic of a binary cell that stores one bit of information is shown below.
  - Read/Write = 0, select = 1, input data to S-R latch
  - Read/Write = 1, select = 1, output data from S-R latch

 


Fig. 7-5 Memory Cell

## Programmable Logic Array:

- The decoder in PROM is replaced by an array of AND gates that can be programmed to generate any product term of the input variables.
- The product terms are then connected to OR gates to provide the sum of products for the required Boolean functions.
- The output is inverted when the XOR input is connected to 1 (since  $x \oplus 1 = x'$ ). The output doesn't change and connect to 0 (since  $x \oplus 0 = x$ ).

F1 =

$$AB' + AC + A'BC'$$

$$F2 = (AC + BC)'$$

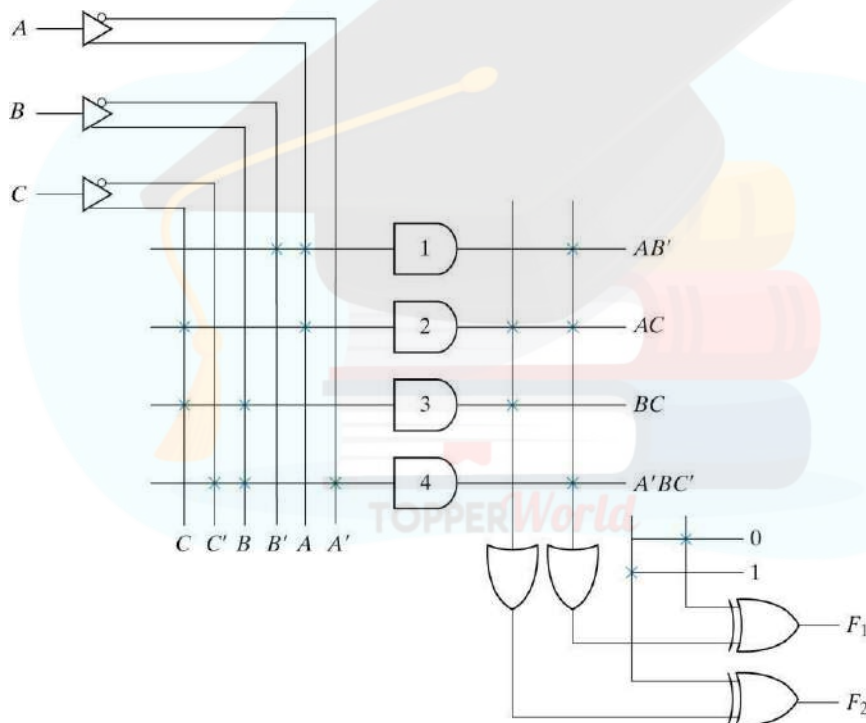


Fig. 7-14 PLA with 3 Inputs, 4 Product Terms, and 2 Outputs

**Table 7-5**  
**PLA Programming Table**

Product Term		Inputs			Outputs	
		A	B	C	(T)	(C)
					$F_1$	$F_2$
$AB'$	1	1	0	-	1	-
$AC$	2	1	-	1	1	1
$BC$	3	-	1	1	-	1
$A'BC'$	4	0	1	0	1	-

□ Implement the following two Boolean functions with a PLA:

- $F_1(A, B, C) = \sum(0, 1, 2, 4)$
- $F_2(A, B, C) = \sum(0, 5, 6, 7)$

		BC			
		00	01	11	10
A	0	1	1	0	1
	1	1	0	0	0

$C$

$$F_1 = A'B' + A'C' + B'C'$$

$$F_1 = (AB + AC + BC)'$$

		BC			
		00	01	11	10
A	0	1	0	0	0
	1	0	1	1	1

$C$

$$F_2 = AB + AC + A'B'C'$$

$$F_2 = (A'C + A'B + AB'C)'$$

- Both the **true** and **complement** of the functions are simplified in **sum of products**.
- We can find the same terms from the group terms of the functions of  $F_1$ ,  $F_1'$ ,  $F_2$  and  $F_2'$  which will make the minimum terms.

$$F_1 = (AB + AC + BC)'$$

$$F_2 = AB + AC + A'B'C'$$

PLA programming table

	Product term	Inputs			Outputs	
		A	B	C	(C)	(T)
					$F_1$	$F_2$
$AB$	1	1	1	-	1	1
$AC$	2	1	-	1	1	1
$BC$	3	-	1	1	1	-
$A'B'C'$	4	0	0	0	-	1

Fig. 7-15 Solution to Example 7-2

