

Roll No. ....

Total Pages : 2

**BT-3/D-18**

**33113**

**DIGITAL ELECTRONICS AND LOGIC DESIGN**

**Paper : IT-207N**

**Time : Three Hours]**

**[Maximum Marks : 75**

**Note :** Attempt *five* questions in all, selecting at least *one* question from each unit.

**UNIT-I**

1. Express the following BCD numbers :
  - (i) Straight binary form and
  - (ii) Excess-3 code-10010011, 01100111. (15)
  
2. Simplify the Boolean function using K-Map  
$$F(W, X, Y, Z) = \sum (1, 3, 7, 11, 15) + d(0, 2, 5)$$
Also simplify the same using QMC method. (15)

TOPPERWorld

**UNIT-II**

3. What is Encoder? Explain with logic circuit. Also explain how encoders with decoders can be used as code converters. (15)
  
4. Explain BCD adder and subtractor in detail. (15)

33113/400/KD/2148

**[P.T.O.  
20/12**

### UNIT-III

5. What is different between JK flip-flop and JK master slave flip-flop? Which *one* is better and why? (15)
6. Explain synchronous and asynchronous counters. (15)

### UNIT-IV

7. Discuss D/A and A/D converter. (15)
8. What are programmable logic devices? Differentiate PLA and PAL. (15)

