

BT-3/D-21

43140

NETWORK THEORY

Paper-EC-213A


Time : Three Hours]

[Maximum Marks : 75

**Note :** Attempt *five* questions in all, selecting at least *one* question from each unit.

## UNIT-I

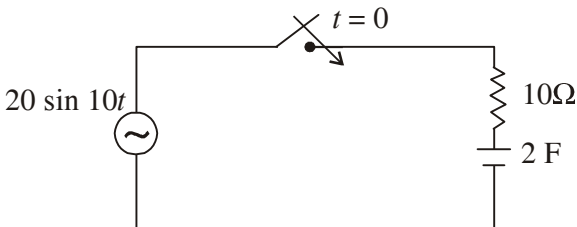1. (a) What is incidence matrix in network? Explain its properties.
- (b) Find the step response (by applying of a constant voltage source at the close of a switch) of a series RLC circuit.
2. (a) What are singularity functions? Give examples.
- (b) In the circuit shown in fig, find the transient current when the switch is closed at  $t = 0$ . Assume zero initial conditions.




## UNIT-II

- Derive the Transient Response in series R-C circuit with sinusoidal excitation for second order circuit. A step voltage of 10 V is applied at  $t = 0$  in a R-C series circuit where  $R = 2\Omega$ .  $C = 2F$ . The initial charge of the capacitor is nil. calculate  $i(t)$  using Laplace Transform.
- The Laplace transform of a voltage  $v(t)$  is  $V(s) = 4(s + 1)/(s + 2)(s + 3)$ . Draw poles and zeros of this function and determine  $v(t)$  using pole-zero plot.

## UNIT-III

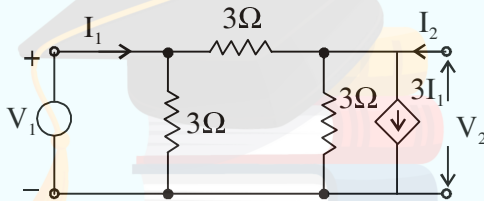- (a) Determine the  $y$ -parameters of the network shown in figure.



- (b) The Z-parameters of a two port network are  $Z_{11} = 15$ ,  $Z_{22} = 24$ ,  $Z_{12} = Z_{21} = 6$ .

Determine (i) ABCD parameters and (ii) Equivalent T network.

- (a) Derive the  $h$ -parameters of Two port networks. Also determine the condition of reciprocity and symmetry in  $h$ -parameter network.
- (b) Explain the parallel connection of Two port network.

## UNIT-IV

7. (a) Design a T and  $\pi$  section constant-K Low pass filter having a cut-off frequency of 2 kHz and nominal impedance  $R_0 = 600 \Omega$ . Obtain a) characteristics impedance and phase constant at 24 kHz when cut off frequency is 10 kHz.
- (b) List and explain the synthesis properties of R-L impedance functions.
8. (a) Design an  $m$  drive T section for high pass filter having cut off frequency 10 kHz, design impedance 600  $\Omega$  and frequency of infinite attenuation of 15 kHz.
- (b) Describe the criterion to determine whether a polynomial is Hurwitz polynomial or not.

